
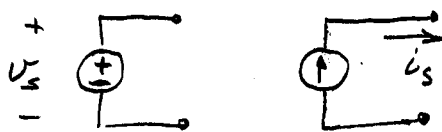
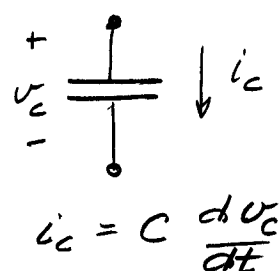
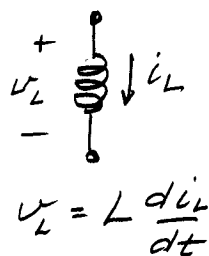


1.2 Analysis of Linear Circuits by Differential Equations 1.2.1



DC & L Chapt. 9

- The DE representation of a circuit is fundamental. It accommodates time variation and non-linearities, both of which present problems for transform methods.


The cast:

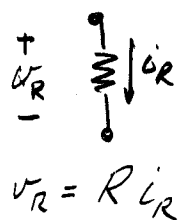

independent sources

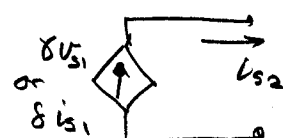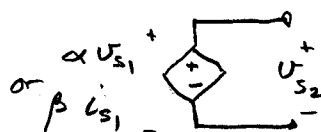


controlled sources

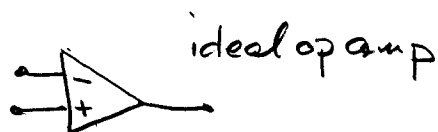

Why are these idealizations?


- From previous courses, you are familiar with use of node and loop equations (KCL, KVL) to obtain a DE relating a selected variable as output to the various inputs. We won't expand on the method in ENSC 320 — but you must know it.
- Instead, we will develop an alternative method based on "state equations."
 - convenient for numerical solution by computer
 - convenient for non linear circuits
 - link to control theory, system theory
 - link to linear algebra.

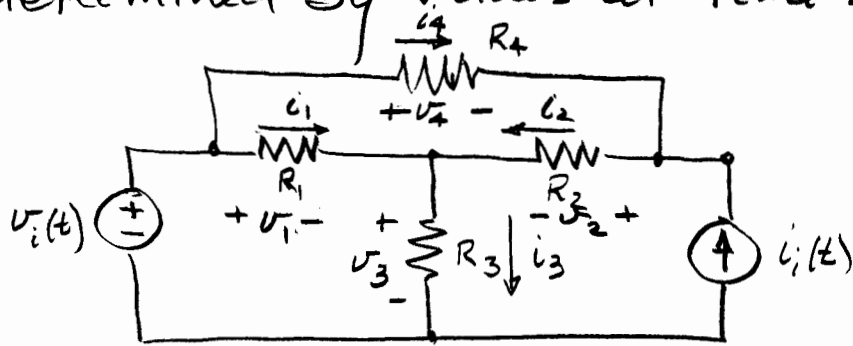- In a purely resistive circuit, the values at time t of every current and voltage are determined by values at time t of the inputs



memoryless

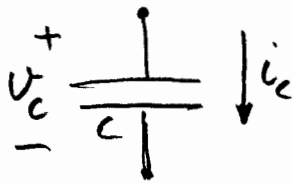
- But capacitors and inductors have memory:



$$i_c = C \frac{dv_c}{dt}$$

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(\alpha) d\alpha$$

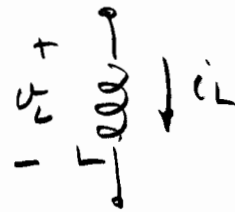cap voltage won't change instantaneously, even if sources do.




$$v_L = L \frac{di_L}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\alpha) d\alpha$$

inductor current won't change instantaneously, even if sources do

Capacitor voltages and inductor currents summarize the effect at time t of all past inputs.

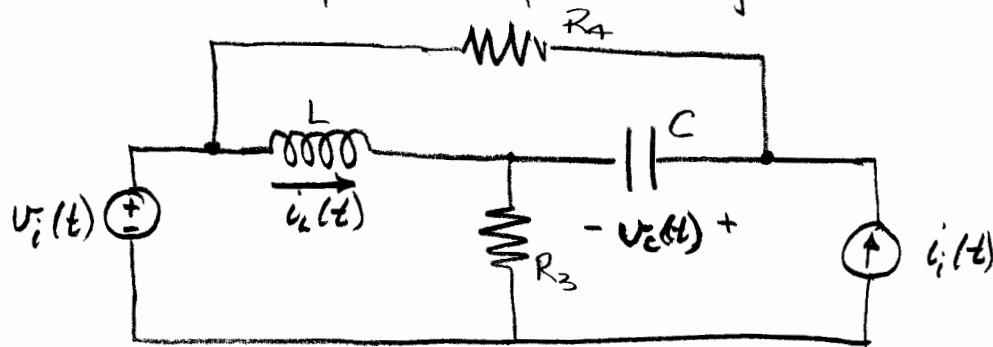- In an RLC circuit, the values at time t of every current and voltage are determined by the values at time t of the inputs, the cap voltages and inductor currents, 1.2.2 c




With inputs, cap voltages, inductor currents specified, you can calculate all other currents and voltages by loop & node equations, or circuit reduction (voltage dividers, current dividers, etc), or (for simple circuits) by inspection.

- So the response of the circuit is determined by the way the v_C 's and i_L 's respond; we need their derivatives $\frac{d}{dt} v_C(t)$, $\frac{d}{dt} i_L(t)$.

- The state equations express the derivatives of the cap voltages and inductor currents (the state variables) as functions only of
 - the inputs
 - the state variables themselves,
 not (e.g.) resistor voltages, or cap currents, or inductor voltages.

"Coupled 1st order D $\dot{E}$ s."

Example

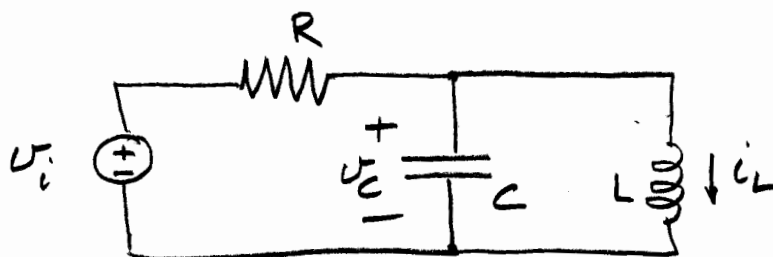

state variables $v_c(t)$, $i_L(t)$.

State equations:

$$\dot{v}_c = \frac{1}{C} i_C = \frac{1}{C} \left(\frac{v_i - v_c}{R} - i_L \right) \quad \text{KCL}$$

$$= -\frac{1}{RC} v_c - \frac{i_L}{C} + \frac{v_i}{RC} \quad (1)$$

and

$$\dot{i}_L = \frac{1}{L} v_L = \frac{1}{L} v_c \quad (2) \quad \text{KVL}$$

The v_c and i_L act rather like sources themselves in determining their derivatives.

- Link with linear algebra and with numerical solution.


1.2.2e

$$\begin{bmatrix} \dot{v}_c \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} & -\frac{1}{C} \\ \frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{RC} \\ 0 \end{bmatrix} v_i$$

- If we solve for $v_c(t)$ and $i_L(t)$, then other circuit quantities are determined — for

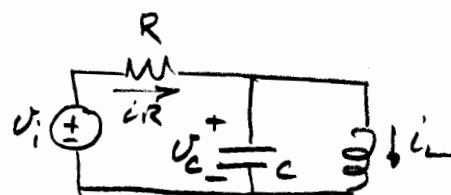example, $i_R = \frac{v_i - v_c}{R}$

$$= \begin{bmatrix} -\frac{1}{R} & 0 \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix} + \frac{1}{R} v_i$$



- General approach for state equations;

1. Write elementary DE for each state var.

$$\dot{v}_c = \frac{1}{C} i_c \quad \dot{i}_L = \frac{1}{L} v_L$$

2. Express RHS (i_c, v_L) in terms of inputs and state vars v_c, i_L only.

Note i_c, v_L are not state variables.

- Often, we are interested in one quantity, which we designate as an "output". We want a single higher order DE for it, instead of a collection of 1st order DEs.

- Suppose it's v_c , in example from p. 1.2.2.d.

- start from state eq'ns

$$\dot{v}_c = -\frac{1}{RC} v_c - \frac{1}{C} i_L + \frac{1}{RC} v_i \quad (1)$$

$$i_L = \frac{1}{L} v_L \quad (2)$$

- Eliminate i_L by differentiating (1),
subst (2):

$$\ddot{v}_c = -\frac{1}{RC} \dot{v}_c - \frac{1}{C} \dot{i}_L + \frac{1}{RC} \dot{v}_i \quad (1)$$

$$= -\frac{1}{RC} \dot{v}_c - \frac{1}{LC} v_c + \frac{1}{RC} v_i \quad \text{subst (2)}$$

Rearrange:

$$\ddot{v}_c + \frac{1}{RC} \dot{v}_c + \frac{1}{LC} v_c = \frac{1}{RC} v_i$$

General procedure DC & L 9.5

- It's a bit more complicated to obtain a DE in i_L , since ① has v_C on the right hand side. This way works well enough, since it's a simple circuit: 1.2.2g

$$\ddot{i}_L = \frac{1}{L} \dot{v}_C$$

$$= -\frac{1}{RLC} v_C - \frac{\dot{i}_L}{LC} + \frac{v_i}{RLC} \quad \text{subst ①}$$

$$= -\frac{\dot{i}_L}{RC} - \frac{\dot{i}_L}{LC} + \frac{v_i}{RLC} \quad \text{subst ②}$$

$$\boxed{\ddot{i}_L + \frac{1}{RC} \dot{i}_L + \frac{1}{LC} i_L = \frac{1}{RLC} v_i} \quad \text{rearranged}$$

- The systematic procedure of DC&L 9.5 treats differentiation like mult. by a constant. OK, since differentiation operator and "mult by a const" operator are linear and commute with themselves and each other.

$$\left(\frac{d}{dt} + \frac{1}{RC}\right) v_C + \frac{1}{C} i_L = \frac{1}{RC} v_i \quad \text{① (rewritten)}$$

$$\frac{1}{L} v_C - \frac{d}{dt} i_L = 0 \quad \text{② (rewritten)}$$

Eliminate v_C :

$$\text{first, } L\left(\frac{d}{dt} + \frac{1}{RC}\right)\text{②: } \left(\frac{d}{dt} + \frac{1}{RC}\right) v_C - L\left(\frac{d}{dt} + \frac{1}{RC}\right) \frac{d}{dt} i_L = 0 \quad \text{②}$$

$$\text{second, ①-②: } \frac{1}{C} i_L + L\left(\frac{d}{dt} + \frac{1}{RC}\right) \frac{d}{dt} i_L = \frac{1}{RC} v_i \quad \text{③}$$


$\frac{1}{L}\text{③}$, then rearrange:

$$\boxed{\ddot{i}_L + \frac{1}{RC} \dot{i}_L + \frac{1}{LC} i_L = \frac{1}{RLC} v_i}$$

This is easier with Laplace transforms.


- Response depends on
 - the input(s)
 - what the circuit was doing just before the input was applied (i.e., cap voltages, inductor currents).

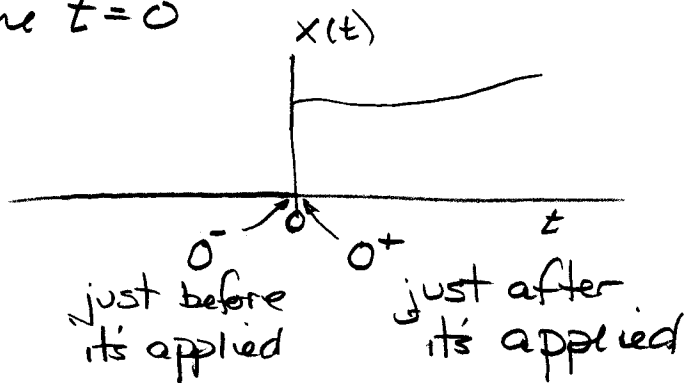- Consider inputs that are switched on at time $t=0$




This notation lets us distinguish initial conditions ($t=0^-$) from those just after input starts ($t=0^+$). Lets us account for discontinuities by transforming 0^- conditions to 0^+ conditions, the ones we use for fitting parameters.

- Example - series/parallel RLC again

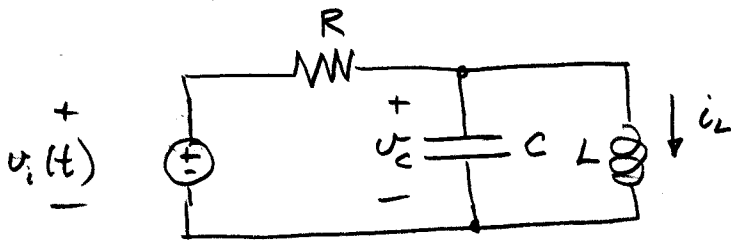

Suppose $v_c(0^-) = 0$ $i_L(0^-) = 0$ at rest
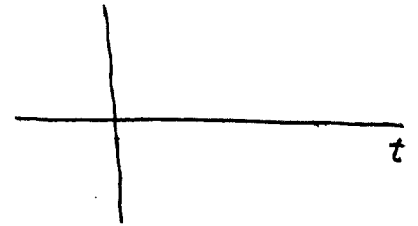
$$\text{and } v_i(t) = \begin{cases} V_i \cos(2\pi f_0 t) & t \geq 0 \\ 0 & t < 0 \end{cases}$$



What are $v_c(0^+)$, $i_L(0^+)$?


what are $\dot{v}_c(0^+)$, $\dot{i}_L(0^+)$?

$$\dot{v}_c(0^+) = \frac{1}{C} i_c(0^+) = \frac{1}{C} \left(\frac{v_i(0^+) - v_c(0^+)}{R} - i_L(0^+) \right)$$

=

$$\dot{i}_L(0^+) = \frac{1}{L} v_L(0^+) = \frac{1}{L} v_c(0^+) =$$

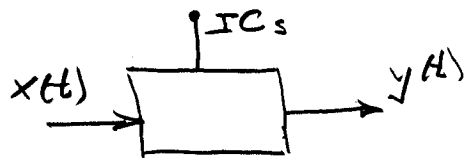- Generally, the response is the solution to



$$a_n y^{(n)} + a_{n-1} y^{(n-1)} + \dots + a_0 y = b_m x^{(m)} + \dots + b_0 x \quad (m \leq n)$$

with ICs $y^{(k)}(0^-) = C_k$

- Components of the solution

- A particular solution satisfies the DE

$$A[y_p(t)] = B[x(t)]$$

for the given $x(t)$, but does not necessarily satisfy the ICs

- A homogeneous solution satisfies

$$A[y_h(t)] = 0$$

but not necessarily the ICs. It depends only on the system internal dynamics, not the input.

- The sum of any particular and any homog. solution satisfies the DE, so total solution

$$y_t(t) = y_p(t) + y_h(t)$$

Since

$$\begin{aligned} A[y_t(t)] &= A[y_p(t)] + A[y_h(t)] \\ &= B[x(t)] \end{aligned}$$

— Reminiscent of linear equations

$$A \underline{y} = \underline{b}$$

If A is singular, then $A \underline{y}_h = \underline{0}$ where

$\underline{y}_h$ has number of params equal to degeneracy.

If $\underline{y}_p$ is any solution of $A \underline{y}_p = \underline{b}$, then

so is $\underline{y}_p + \underline{y}_h$ since

• From MATH 310

Homogeneous

Exponentials reproduce under differentiation, so substitute

$$\underline{y}_h(t) = K e^{st}$$

giving

$$(a_n s^n + a_{n-1} s^{n-1} + \dots + a_0) K e^{st} = 0$$

= 0

Get n solutions $s_i, i=1, \dots, n$ as real, or complex pairs and possibly repeated.

Hence

$$\underline{y}_h(t) = \sum_{i=1}^n K_i e^{s_i t}$$

$$= K_1 e^{s_1 t} + K_2 e^{s_2 t} + \dots + K_n e^{s_n t}$$

is the general form. Repeated roots give

$$\text{poly}(t) e^{s_i t}$$

where $\text{poly}(t)$ degree is one less than multiplicity of root.

Particular

From experience

$\underline{x}(t)$	$\underline{y}_p(t)$
X	Y (const)
$X_0 + X_1 t$	$Y_0 + Y_1 t$
$\cos(2\pi f_0 t)$	$Y_c \cos(2\pi f_0 t)$
or $\sin(2\pi f_0 t)$	$+ Y_s \sin(2\pi f_0 t)$


Substitute $\underline{y}_p(t)$ into DE and fit parameters so both sides match

- The total solution

$$y_t(t) = y_p(t) + \underbrace{y_h(t)}_{n \text{ params}}$$

must now be adjusted through choice of params to match the ICs. Fit them at what time??

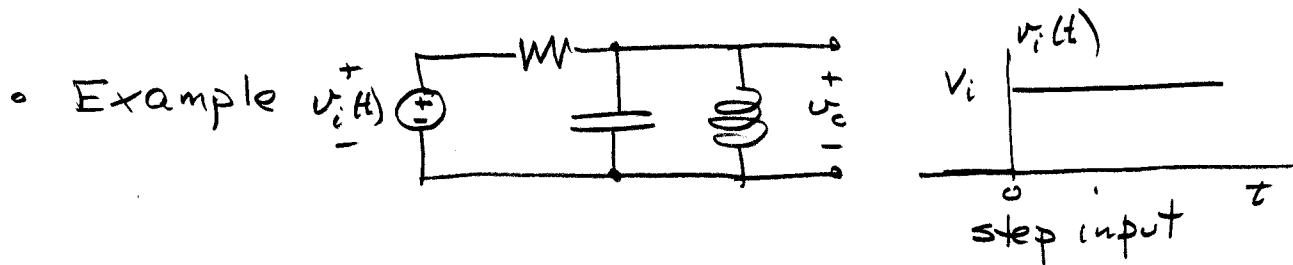Note $y_t(t)$ is continuous for $t > 0$, so fit at $t = 0^+$ to the conditions we transformed from those at $t = 0^-$.



Particular $v_{cp}(t) = V_c$ since input constant

$$\ddot{V}_c + \frac{1}{RC} \dot{V}_c + \frac{1}{LC} V_c = \underbrace{\frac{1}{RC} V_i}_0$$

$$\text{so } v_{cp}(t) = 0$$

on physical grounds, too

Homogeneous - find s values. Subst e^{st} into DE p. 1.2.2

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \quad s = -\frac{1}{2RC} \pm \frac{1}{2} \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}$$

$$v_{ch}(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

Total

$$v_c(t) = v_{cp}(t) + v_{ch}(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} \quad t > 0$$

And fit to ICs on p. 1.2.4.

$$v_c(0^+) = K_1 e^{s_1 0^+} + K_2 e^{s_2 0^+} = 0$$

$$K_1 + K_2 = 0$$

$$\dot{v}_c(0^+) = K_1 s_1 e^{s_1 0^+} + K_2 s_2 e^{s_2 0^+} = \frac{V_i}{RC}$$

$$K_1 s_1 + K_2 s_2 = \frac{V_i}{RC}$$

so $K_1 = \frac{V_i}{RC(s_1 - s_2)} \quad K_2 = -K_1$

or $= \frac{V_i}{RC \sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}} \quad K_2 = -K_1$ where $s_1 = -\frac{1}{2RC} + \frac{1}{2}\sqrt{\dots}$
 $s_2 = -\frac{1}{2RC} - \frac{1}{2}\sqrt{\dots}$


so
$$v_c(t) = \frac{V_i}{RC \sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}} e^{-t/2RC} \left(e^{\frac{t}{2}\sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}} - e^{-\frac{t}{2}\sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}} \right) \quad (1)$$

Looks as though we have a complete solution method. But what if the discriminant is negative (complex roots) or zero (repeated roots)?

A little more work is required (not much). Look at all three cases in detail: distinct real roots, repeated real roots, imaginary roots.


- Case 1: $\left(\frac{1}{RC}\right)^2 > \frac{4}{LC}$, distinct real roots

1.2.9

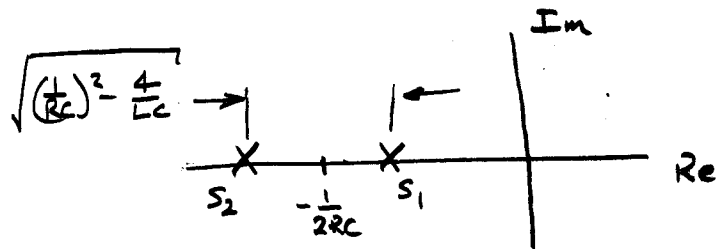

This is the solution labelled ① on P. 1.2.8. View it as $e^{-t/2RC}$ decaying exponential times a sinh function or, more productively, as
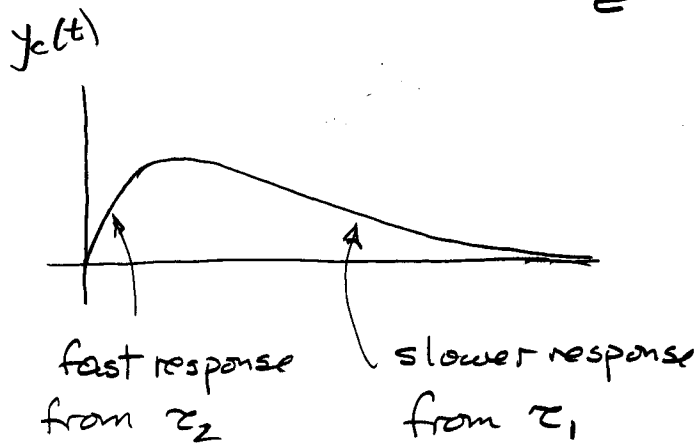
$$u_c(t) = \frac{V_i}{RC\sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}} \left(\underbrace{e^{t(-\frac{1}{2RC} + \frac{1}{2}\sqrt{\dots})}}_{e^{-t/\tau_1}} - \underbrace{e^{t(-\frac{1}{2RC} - \frac{1}{2}\sqrt{\dots})}}_{e^{-t/\tau_2}} \right)$$




$\tau_1 =$

$\tau_2 =$

The root closer to the origin contributes the more slowly decaying term. Generally true — real poles closer to origin have slower responses.

- Case 2: $\left(\frac{1}{RC}\right)^2 < \frac{4}{LC}$, complex roots
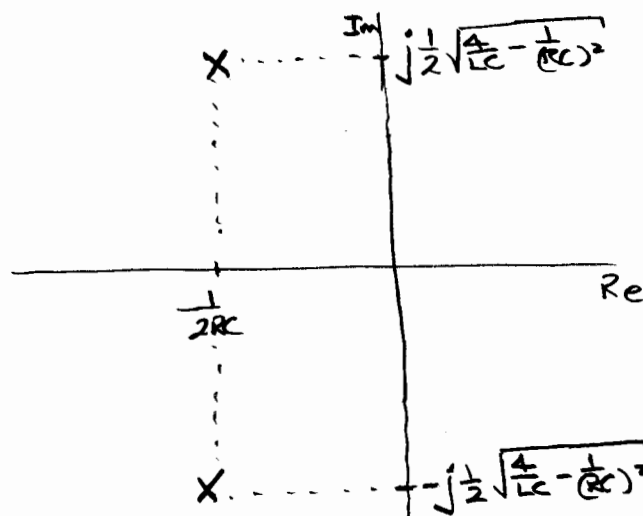
$$s_1 = -\frac{1}{2RC} + \frac{j}{2} \sqrt{\frac{4}{LC} - \left(\frac{1}{RC}\right)^2} \quad s_2 = -\frac{1}{2RC} - \frac{j}{2} \sqrt{\frac{4}{LC} - \left(\frac{1}{RC}\right)^2}$$




a
conjugate
pair

From ①, p 1.2.8

$$v_c(t) = \frac{V_i}{jRC \sqrt{\frac{4}{LC} - \left(\frac{1}{RC}\right)^2}} e^{-t/2RC} \left(e^{j\frac{t}{2} \sqrt{\frac{4}{LC} - \left(\frac{1}{RC}\right)^2}} - e^{-j\frac{t}{2} \sqrt{\frac{4}{LC} - \left(\frac{1}{RC}\right)^2}} \right)$$
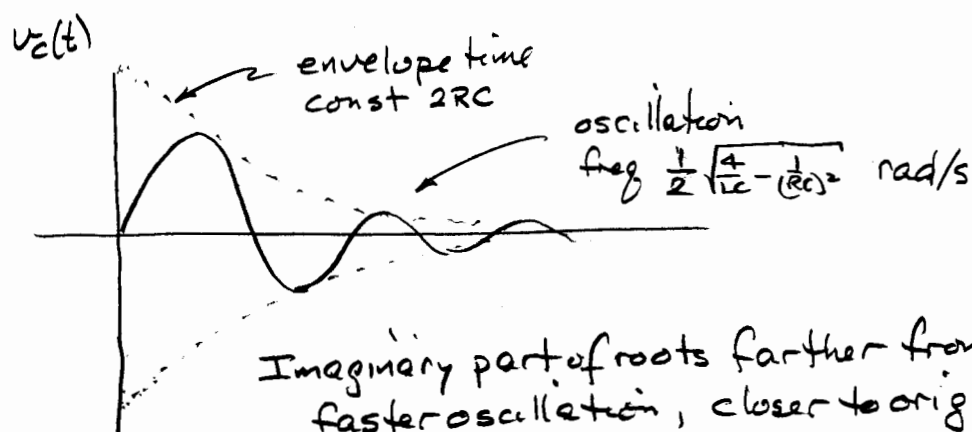
$$= \frac{2 V_i}{RC \sqrt{\frac{4}{LC} - \left(\frac{1}{RC}\right)^2}} e^{-t/2RC} \sin\left(\frac{1}{2} \sqrt{\frac{4}{LC} - \left(\frac{1}{RC}\right)^2} t\right)$$




Imaginary part of roots farther from origin gives faster oscillation, closer to origin is slower osc.

Real part farther from origin gives faster decay, closer to origin, slower decay.

- Case 3 (last one) $\left(\frac{1}{RC}\right)^2 = \frac{4}{LC}$ repeated roots

$$s_1 = s_2 = -\frac{1}{2RC}$$

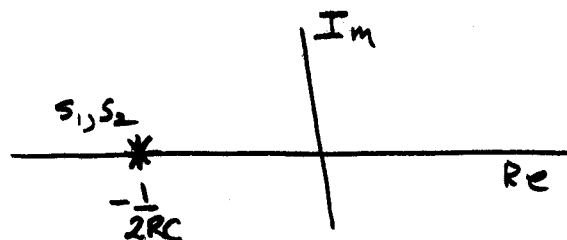

From ①, p 1.2.8, both numerator and denominator are zero! Two workarounds: (1) take limit of Case 1 or Case 2 as $s_1 - s_2 \rightarrow 0$ using L'Hopital's Rule, or (2) use the "canned" solution that results:

$$v_{ch}(t) = (F_1 + F_2 t) e^{s_c t} \quad (s_c \text{ is the common value of root})$$

so

$$v_c(t) = (F_1 + F_2 t) e^{s_c t}$$


Now fit to ICs as on p 1.2.8

$$v_c(0^+) = (F_1 + F_2 0^+) e^{s_c 0^+} = 0 \Rightarrow F_1 = 0$$

$$\dot{v}_c(0^+) = F_2 e^{s_c 0^+} + s_c (F_1 + F_2 0^+) e^{s_c 0^+} = \frac{V_i}{RC} \Rightarrow s_c F_2 = \frac{V_i}{RC}$$

so $F_1 = 0 \quad F_2 = \frac{V_i}{RC} =$

$$v_c(t) = \frac{V_i}{RC} t e^{-t/2RC}$$

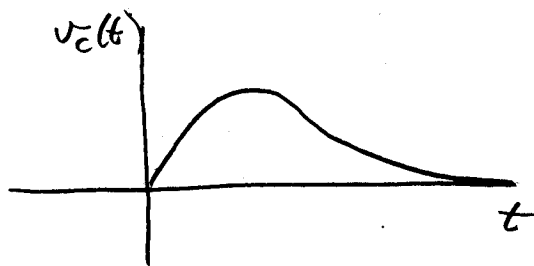

Faster response as pole pair moves out from origin.

- This lengthy example and its predecessors showed the full solution process:
 - obtain a single DE
 - convert ICs at 0^- to ICs at 0^+ for fitting parameters
 - the parameter fit
 - variations on the form of the response

It's easier with Laplace transforms!

- Why is this circuit useful?

View animations in "Poles, Zeros and System Response" on website.