

## 1.3 Additional Topics on Differential Eqn Solution <sup>1.3.1</sup>

- Section 1.2 described how to analyze simple electric circuits. Simple? No dependent sources, only one source. See DC&L for them.
- This section contains observations about the solution.

### 1.3.1 The Impulse Response

- We have seen how to calculate the response to a step, or a ramp, or a sinusoid. For ICs at  $t=0^+$ , we relied on continuity of cap voltages, inductor currents.
- Impulse response is tougher — it's just a homogeneous solution for  $t > 0$  (Why?), but impulses can cause jumps in  $v_c$  or  $i_L$ . What ICs at  $t=0^+$ ?

- How to obtain the impulse response:
  - the hard way – make subtle arguments about ICs before and after the impulse. See "How to Deal With Discontinuities" in Supplementary Notes and Demos on web site.
  - the easy way – calculate the step response  $q(t)$  and differentiate it:
 
$$h(t) = \frac{d}{dt} q(t)$$

### 1.3.2 Decomposition of Solution

- The response of a circuit can be split up in a few interesting ways
- You have seen

$$y_t(t) = y_p(t) + y_h(t)$$

with the  $n$  params of  $y_h(t)$  selected  
so  $y_t(t)$  fits ICs at  $t=0^+$

• Here's an important decomposition:

- zero input response : response to initial conditions only, with no input; it's a homogeneous sol'n with params selected to satisfy ICs (spec'd at  $0^-$ )
- zero state response : response of system to input if it had been at rest; homog plus particular, with params selected for ICs all zero at  $0^-$ .
- total solution :  $y_t(t) = y_{zs}(t) + y_{zi}(t)$

Proof:

$$A[y_t] = A[y_{zs} + y_{zi}] = A[y_{zs}] + A[y_{zi}] = B[x], \quad t > 0$$


and

$$y_t^{(k)}(0^-) = y_{zs}^{(k)}(0^-) + y_{zi}^{(k)}(0^-) = 0 + C_k = C_k, \quad k = 0 \dots n-1$$

so  $A[y_t] = B[x], \quad t > 0$

$$y_t^{(k)}(0^-) = C_k \quad k = 0 \dots n-1$$

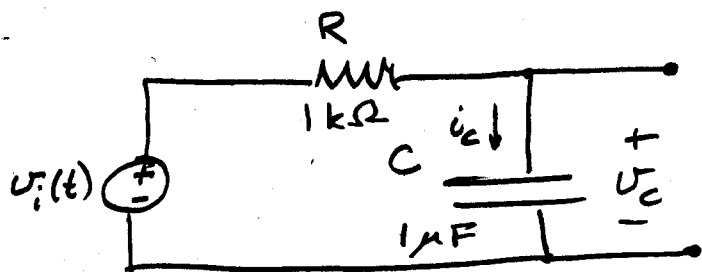- example: The circuit below has input, parameter values and IC's as shown. Find its voltage response as a sum of zero state and zero input responses, and verify that it satisfies the DE and IC's



$$v_c(0^-) = 5 \text{ volt.}$$

$$v_i(t) = 10 \text{ u(t)}$$

- The DE

$$\dot{v}_c = \frac{1}{C} i_c = \frac{1}{C} \left( \frac{v_i - v_c}{R} \right)$$

$$\dot{v}_c + \frac{1}{RC} v_c = \frac{1}{RC} v_i, \text{ with } v_c(0^-) = 5 \text{ volt, } v_i(t) = 10 \text{ u(t)}$$

- Zero input response (due to ICs alone)

$$\dot{v}_{zir} + \frac{1}{RC} v_{zir} = 0 \Rightarrow v_{zir}(t) = A e^{-t/RC} = A e^{-1000t}$$

a homogeneous solution

To get A, fit at  $t=0^+$ . With no input,

$$v_c(0^+) = v_c(0^-) = 5 \text{ V}; \quad v_{zir}(0^-) = A e^{-0/RC} = A$$

$$A = 5 \text{ V}$$

$$v_{zir}(t) = 5 e^{-1000t}, \quad t > 0$$

- zero state response (circuit at rest, then driven by input)

$$\dot{v}_{zsr}(t) + \frac{1}{RC} v_{zsr}(t) = \frac{10}{RC} u(t), \quad v_{zsr}(0^-) = 0 \text{ (at rest)}$$

particular solution for  $t > 0$ :  $u(t)$  is constant at 1, so

$$v_p(t) = 10$$

homog solution, as before,

$$v_h(t) = A e^{-t/RC} = A e^{-1000t}$$

- So the zsr is  $v_{zsr}(t) = 10 + A e^{-1000t}$ ,  $t > 0$
- Transform the IC: No impulses driving circuit, so cap voltage is continuous;  $v_{zsr}(0^+) = v_{zsr}(0^-) = 0$ .


$$10 + A e^{-1000 \cdot 0^+} = 0 \Rightarrow A = -10$$

$$v_{zsr}(t) = 10(1 - e^{-1000t}), t > 0$$

• Total response

$$v_c(t) = \underbrace{5 e^{-1000t}}_{zsr} + \underbrace{10(1 - e^{-1000t})}_{zsr}, t > 0$$

$$= 10 - 5 e^{-1000t}, t > 0$$

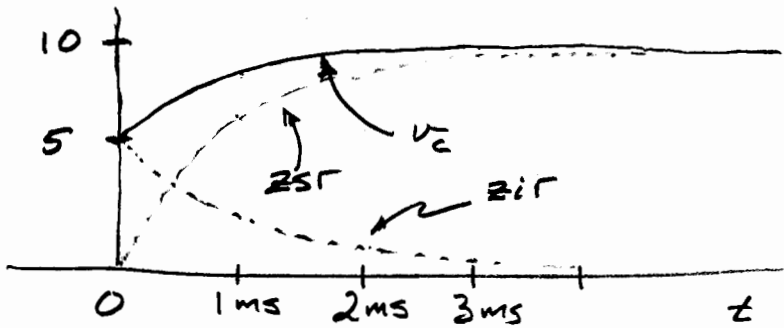


- Verify — substitute  $v_c(t) = 10 - 5 e^{-1000t}$  into the DE

$$\underbrace{5000 e^{-1000t}}_{\dot{v}_c} + \underbrace{1000 \cdot (10 - 5 e^{-1000t})}_{\frac{1}{RC} v_c} = \underbrace{1000 \cdot 10}_{\frac{1}{RC} V_i} \quad \checkmark$$


and IC?

$$v_c(0^+) = 10 - 5 e^{-1000 \cdot 0^+} = 5 \text{ V} \quad \checkmark$$

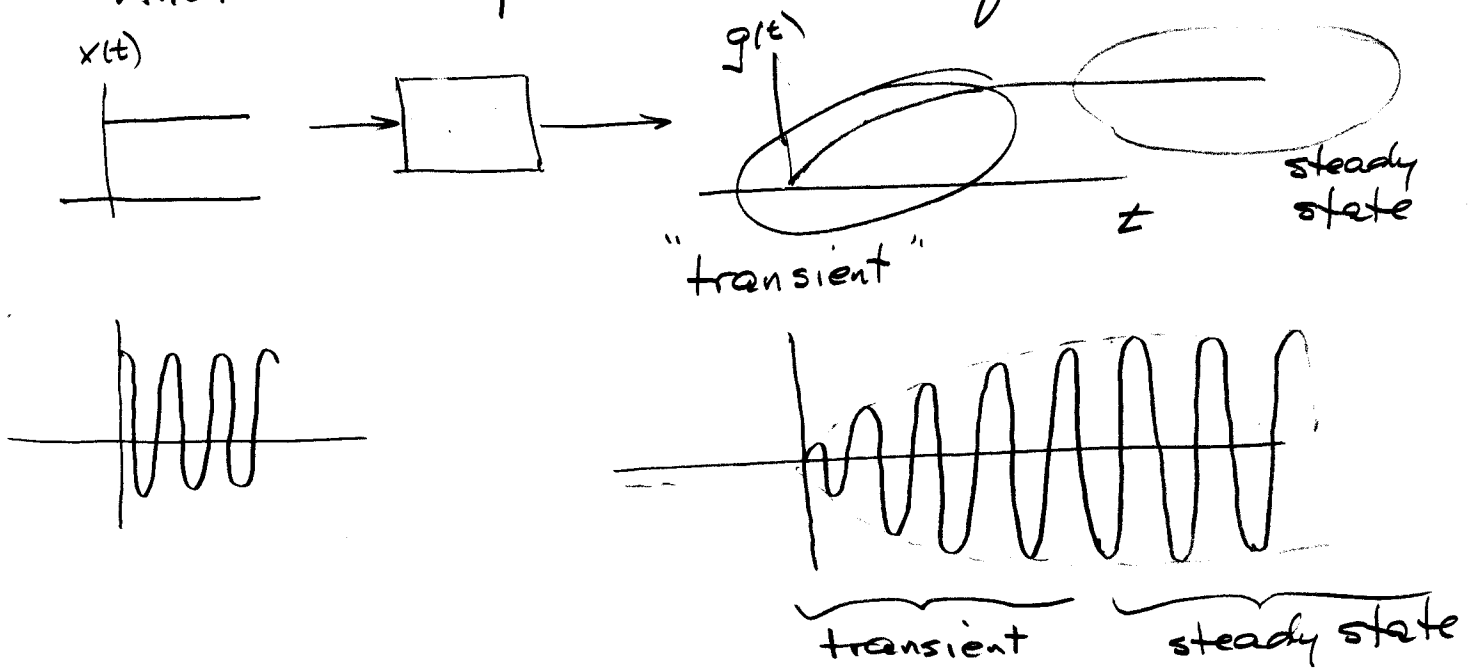- Another decomposition is more qualitative. 1.3.4



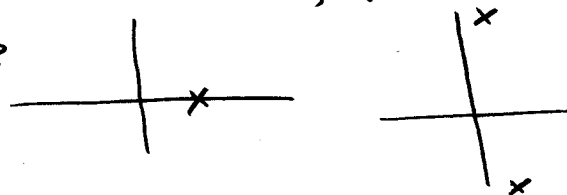- No sharp boundary
- Requires system to be stable, poles in LHP — not like




That way the homogeneous solution dies out (is transient) instead of growing exponentially.

- The steady state component is the particular solution.
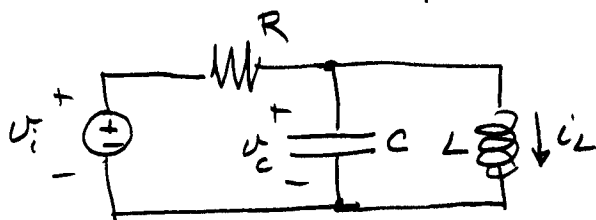
### 1.3.3 State Variables


- Capacitors and inductors are the dynamic portions of a circuit. Their voltages  $v_c$  and currents  $i_L$  are "state variables".
- Recall initial analysis as coupled first order DEs. Example p 1.2.2




$$\dot{v}_c = -\frac{1}{RC} v_c - \frac{i_L}{C} + \frac{v_i}{RC}$$

$$\dot{i}_L = \frac{1}{L} v_c$$

- Any selected output depends only on the input and the state variables.

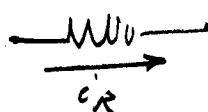e.g. resistor current 

$$i_R(t) = \frac{v_i(t) - v_c(t)}{R}$$

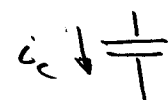e.g. cap current 

$$i_c(t) = i_R(t) - i_L(t) = -\frac{1}{R} v_c(t) - i_L(t) + \frac{1}{R} v_i(t)$$

- The evolution of the system response depends only on the input and the state variables, since the derivatives capture the instantaneous evolution


- The state (the collection of state variables) captures the entire past history of the circuit, since at any time

$$\dot{v}_c(t) = -\frac{1}{RC} v_c(t) - \frac{1}{L} i_L(t) + \frac{1}{RC} v_i(t)$$

$$\dot{i}_L(t) = \frac{1}{L} v_c(t)$$




It doesn't matter how the system came to particular values of  $v_c(t)$ ,  $i_L(t)$ .

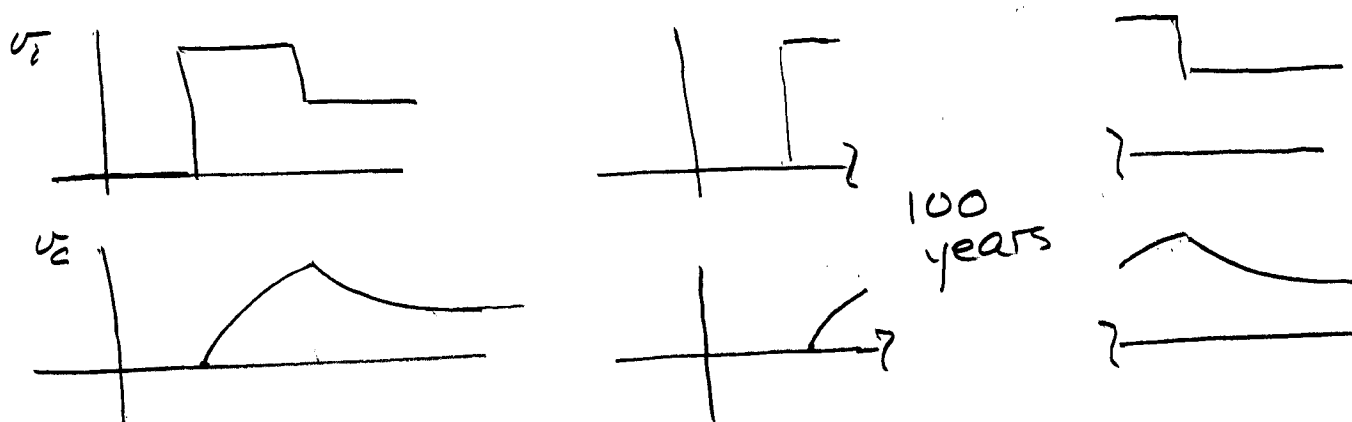- If we could save, then restore, the state, the system would be unaffected by the gap



- A similar concept applies to multitasking on a computer. The state is the set of values in all CPU registers, stack pointers and data areas of a program. Save them, then restore at some future time, and the program simply carries on.


- Similarly, mechanical systems

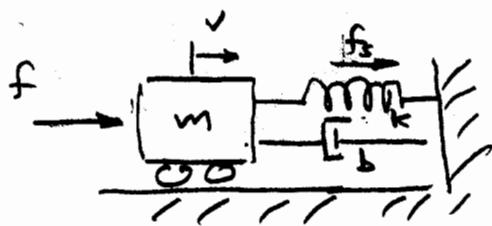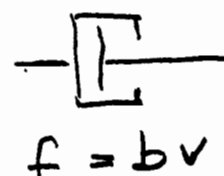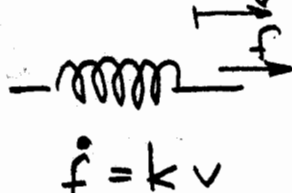

use as state variables



- velocities of masses
- forces in springs

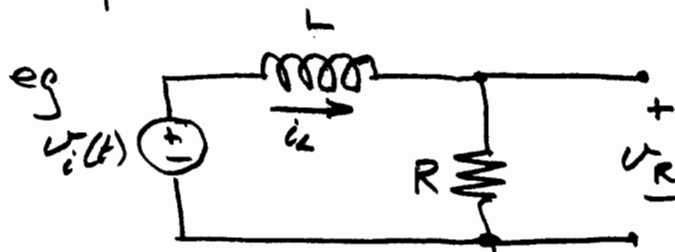- If the <sup>initial</sup> state is non-zero, then the output will be non zero, even with no input. This is "zero input response."
- If <sup>initial</sup> state is zero (all cap voltages, inductor currents zero), system is at rest. Response to input is "zero state response"





for step input  $V_i u(t)$   
and  
 $i_L(0^-) \neq 0$

zero input response

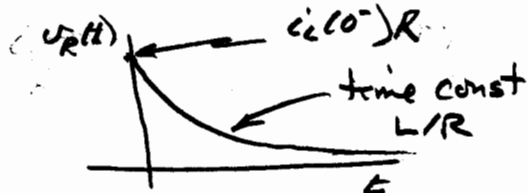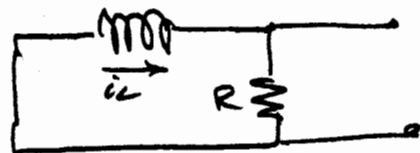


zero state response

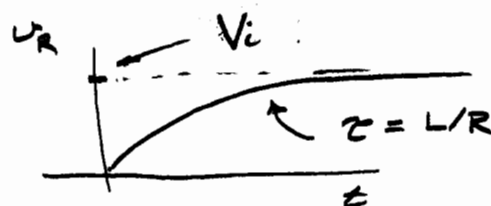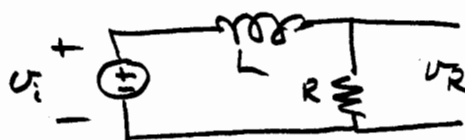

- The state variables can be stacked in a state vector, leading to the state equations

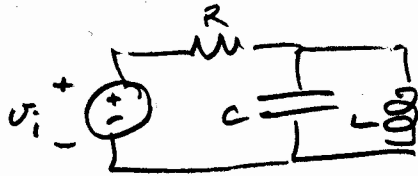example from p 1.3.5  $\begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} = \underline{x}(t)$



conventional notation  $\underline{x}$

$$\begin{bmatrix} \dot{v}_c(t) \\ \dot{i}_L(t) \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} & -\frac{1}{C} \\ \frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} 1/RC \\ 0 \end{bmatrix} v_i(t)$$

$$\dot{\underline{x}}(t) = A \underline{x}(t) + \underline{b} u(t)$$

conventional notation



If output is  $i_L$

$$i_L(t) = \begin{bmatrix} -\frac{1}{R} & 0 \end{bmatrix} \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} 1/R \end{bmatrix} v_i(t)$$

$$y(t) = C \underline{x}(t) + d u(t)$$

conventional

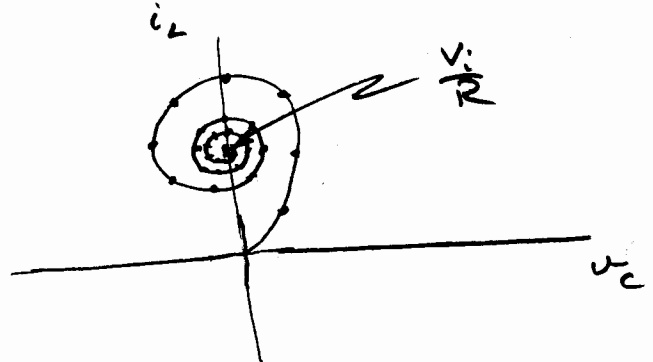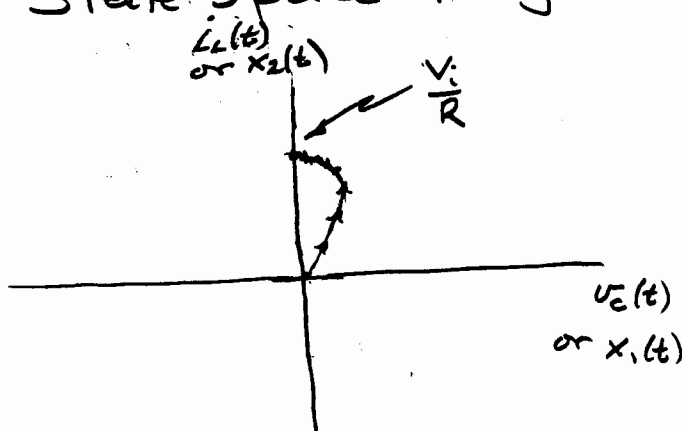- State space trajectories in response to step




### 1.3.4 Order of Derivation on Right Hand Side

1-3.9


- Consider a system  described by  $A[y(t)] = x(t)$

Typical step responses

1<sup>st</sup> order

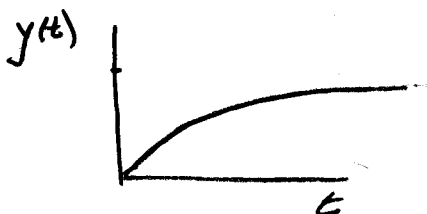



2<sup>nd</sup> order

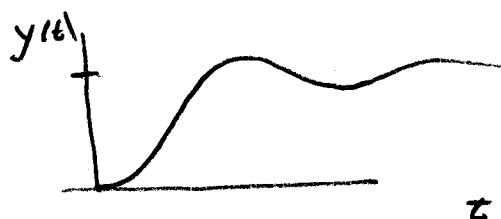

- If the RHS is replaced by  $\dot{x}(t)$ , the new system is described by


$$A[y(t)] = \dot{x}(t)$$

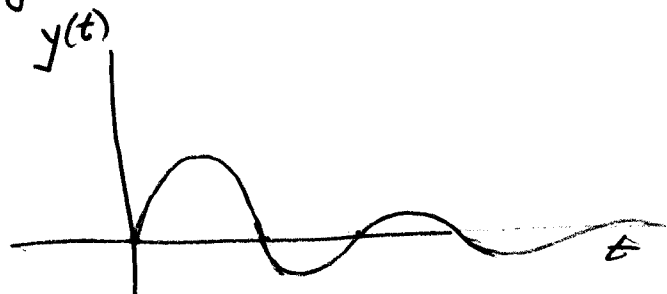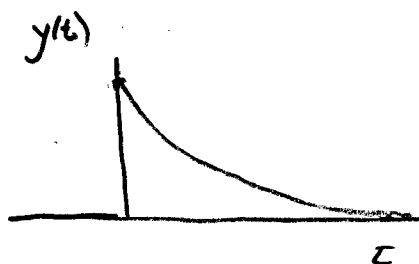In form, this is just like the original system but driven by an input  $\dot{x}(t)$ . Hence response of new system is just the deriv. of response of the original



And for second order with  $\ddot{x}(t)$  on RHS



Order of discontinuity increases.

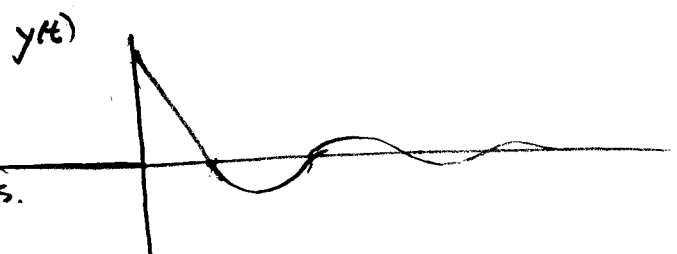

### 1.3.5 Standard Parameterization for Second Order

1.3.10

- Here are two second-order circuits

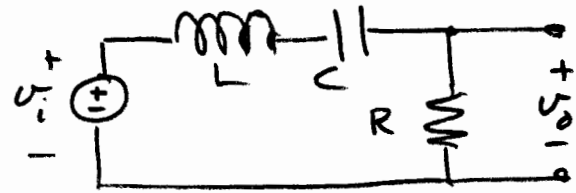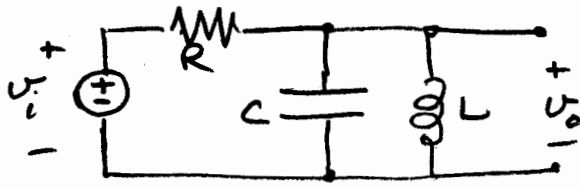

$$\ddot{v}_o + \frac{1}{RC} \dot{v}_o + \frac{1}{LC} v_o = \frac{1}{RC} \dot{v}_i \quad \ddot{v}_o + \frac{R}{L} \dot{v}_o + \frac{1}{LC} v_o = \frac{R}{L} \dot{v}_i$$

The coefficients of the homogeneous DE depend on component values in a way determined by the structure of the circuit.

- To study behaviour of 2<sup>nd</sup> order solutions in general, adopt this standard parameterization

$$\ddot{v}_o + 2\zeta\omega_0 \dot{v}_o + \omega_0^2 v_o = 0$$

$\zeta$  damping factor

The characteristic poly

$\omega_0$  natural frequency

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0$$

has roots

$$\begin{aligned} \begin{Bmatrix} s_1 \\ s_2 \end{Bmatrix} &= -\zeta\omega_0 \pm \frac{1}{2} \sqrt{(2\zeta\omega_0)^2 - 4\omega_0^2} \\ &= \omega_0 \left( -\zeta \pm \sqrt{\zeta^2 - 1} \right) \end{aligned}$$

The nature of the discriminant is set by  $\zeta$

• circuit 1

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

decr  $\omega$  incr  $R$


circuit 2

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

incr  $\omega$  incr  $R$

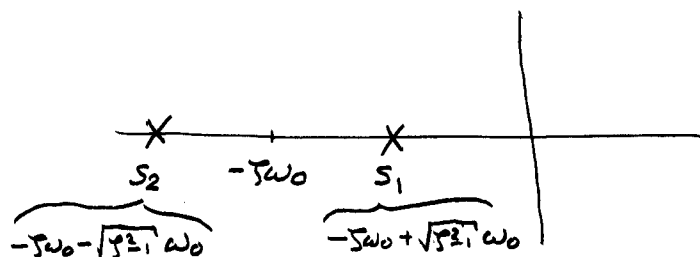• Case  $\zeta > 1$ , overdamped, distinct real roots



- Components of homog. sol'n.


$$e^{s_1 t} = e^{(-\zeta + \sqrt{\zeta^2 - 1}) \omega_0 t} = e^{-t/\tau_1}$$

$$\tau_1 = \frac{1}{\omega_0 (\zeta - \sqrt{\zeta^2 - 1})}$$

$$e^{s_2 t} = e^{(-\zeta - \sqrt{\zeta^2 - 1}) \omega_0 t} = e^{-t/\tau_2}$$

$$\tau_2 = \frac{1}{\omega_0 (\zeta + \sqrt{\zeta^2 - 1})}$$


- Step response

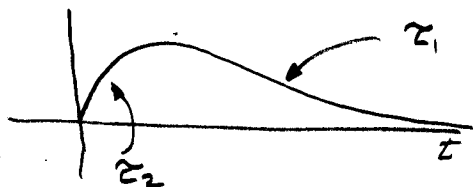


As  $\zeta$  increases,  $\tau_1$  increases, asympt  $\tau_1 \sim \frac{2\zeta}{\omega_0}$

$\tau_2$  decreases, asympt  $\tau_2 \sim \frac{1}{2\zeta\omega_0}$


- Extreme case, large  $\zeta$

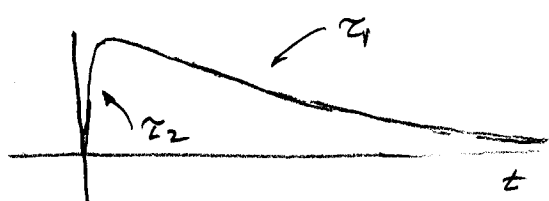

model  
as 1st  
order?

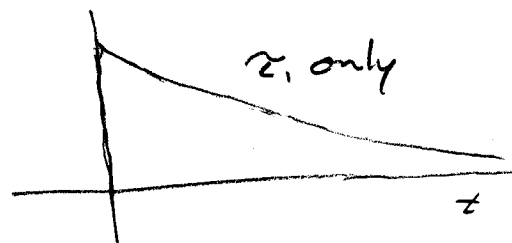

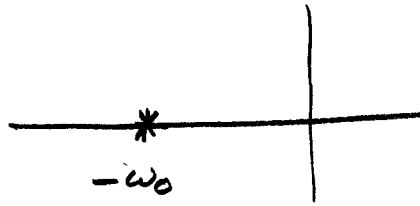- Case  $\zeta = 1$ , critically damped, repeated root 1.3.12




- Step response  $t e^{s_1 t} = t e^{s_2 t} = t e^{-\omega_0 t}$



- Case 3  $\zeta < 1$ , underdamped, complex roots
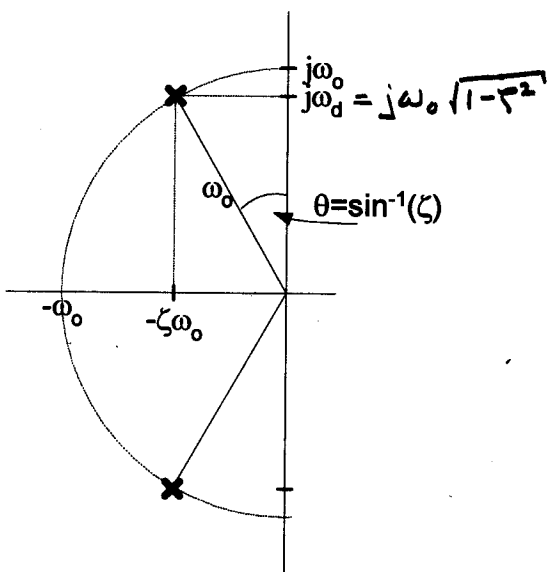
$$\begin{Bmatrix} s_1 \\ s_2 \end{Bmatrix} = \omega_0 (-\zeta \pm j \sqrt{1-\zeta^2})$$



$\omega_0$  natural freq, radius of the roots

$\zeta$  damping factor  
 $\zeta = \sin \theta$

$\omega_d$  damped natural freq,  $\omega_d = \omega_0 \sqrt{1-\zeta^2}$

- step response

$$G_1 e^{s_1 t} + G_2 e^{s_2 t}$$


$$= e^{-\gamma \omega_0 t} (G_1 e^{j \omega_d t} + G_2 e^{-j \omega_d t})$$

Note  $G_2 = G_1^*$  to give real sum. For illustration,

$$\text{look at } G_1 = -j \quad G_2 = j$$

step response
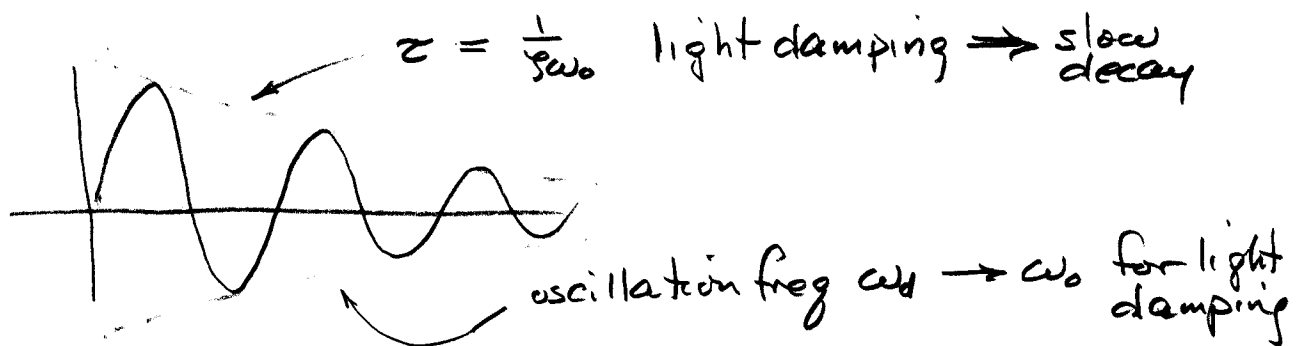
$$e^{-\gamma \omega_0 t} \sin(\omega_d t) = e^{-\gamma \omega_0 t} \sin(\sqrt{1-\gamma^2} \omega_0 t)$$




• In all three cases, we see from

$$e^{s_i t} = e^{(-\gamma \pm \sqrt{\gamma^2 - 1}) \omega_0 t}$$

that -  $\gamma$  sets the "shape" of the response

-  $\omega_0$  sets the time scale

• For

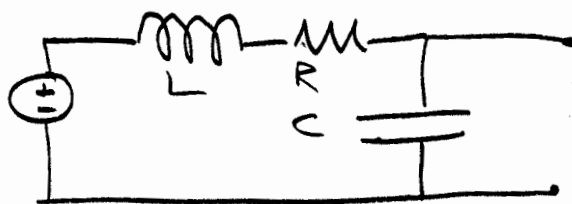

1.3.14  
or any other  
2<sup>nd</sup> order circuit

the step response clearly shows the effect of damping factor

