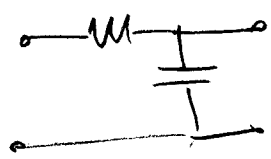




1.5 Useful Circuits Seen in the Time Domain

• In this section, we'll look at a few simple and useful circuits and interpret their action in the time domain





• First order low pass



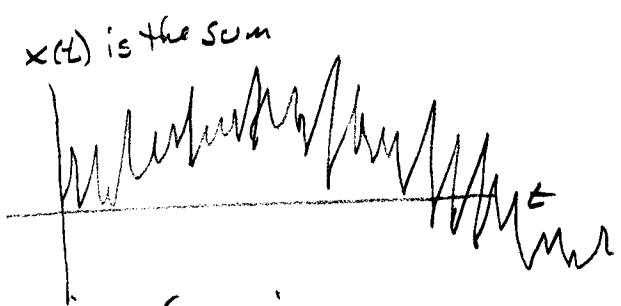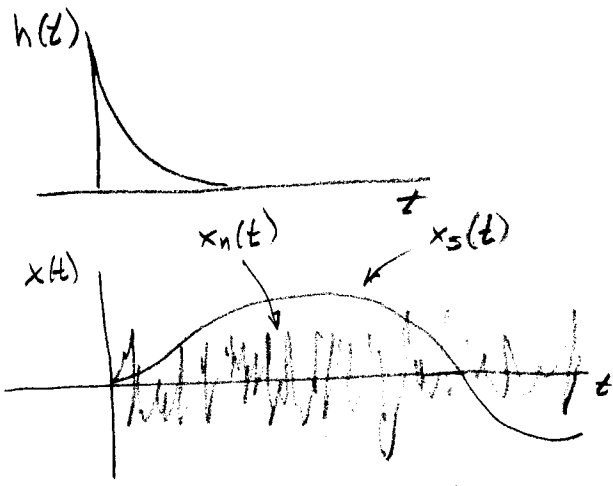lets slowly varying signal through without much damage, while suppressing rapidly varying noise.



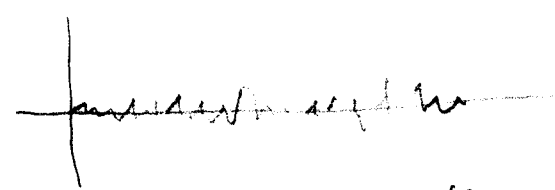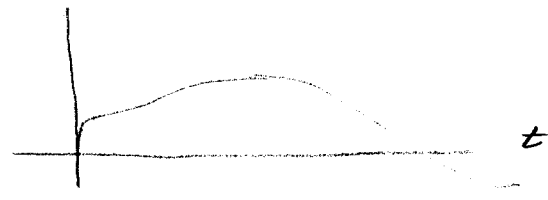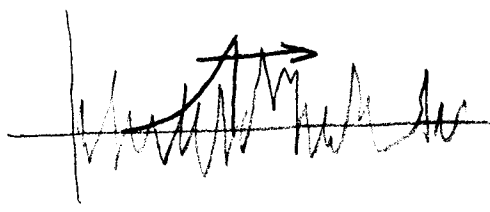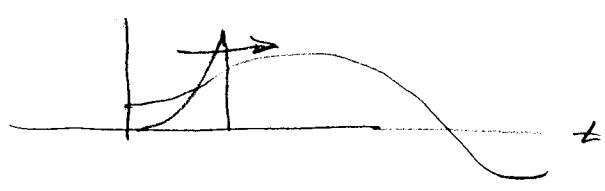Superposition - get sum of signal, noise responses





some distortion, less with very slow variation


noise is greatly reduced through averaging

- A first order "edge picker" gives a blip when the input changes suddenly.


1.5.2

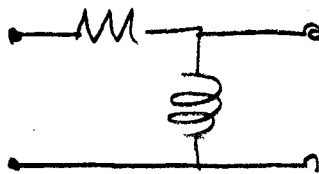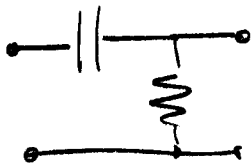

1st order
highpass

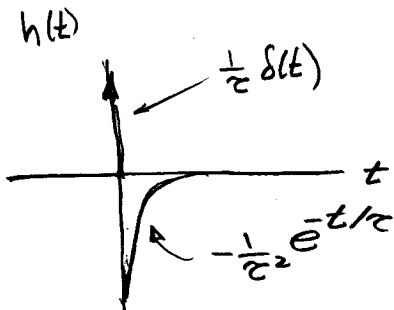


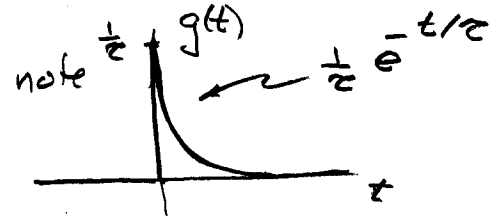
impulse and
exponential
have equal,
opposite areas








$$y(t) = h(t) \otimes x(t) = \frac{1}{\tau} \left(x(t) - \frac{1}{\tau} e^{-t/\tau} \otimes x(t) \right)$$

an exponentially-weighted short term average, lagging



or
 $\dot{x}(t) \otimes g(t)$

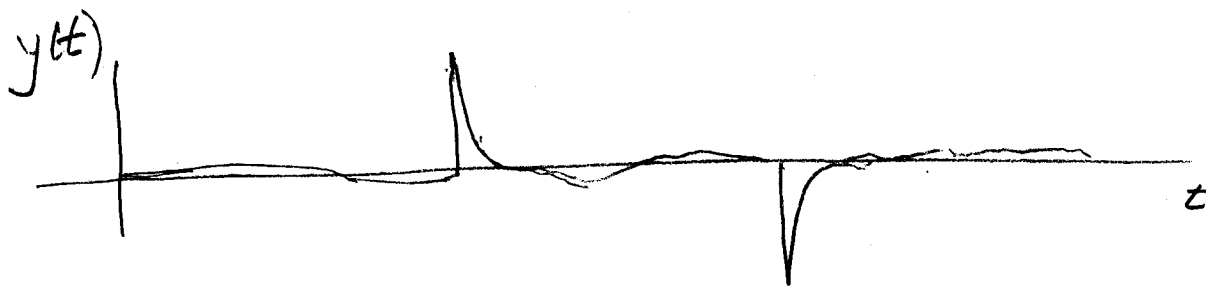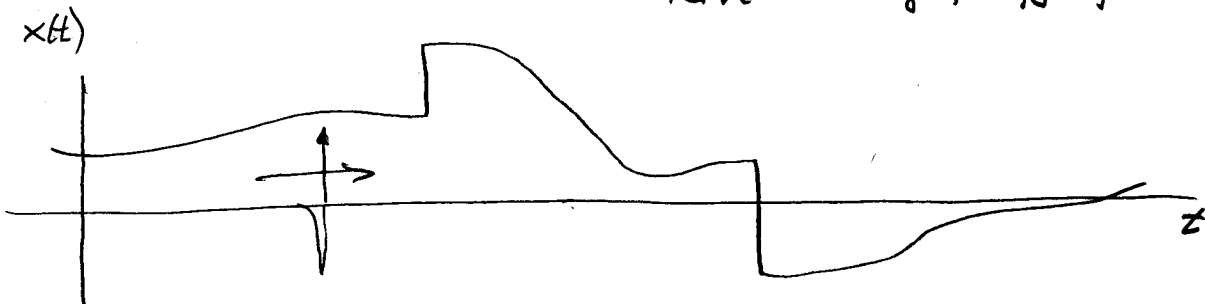

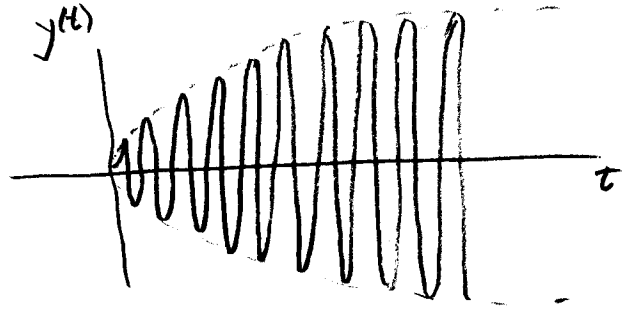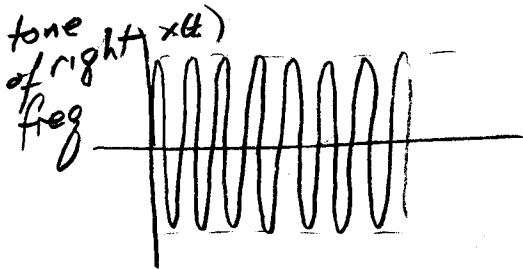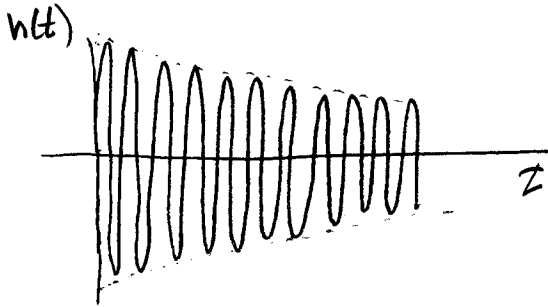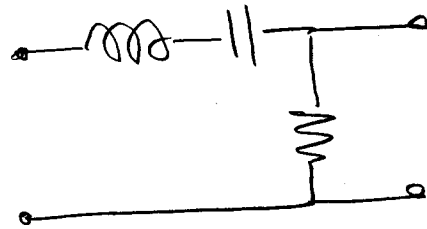
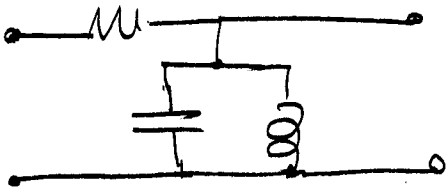
- A resonant circuit detects or tunes a radio station




low freq tone

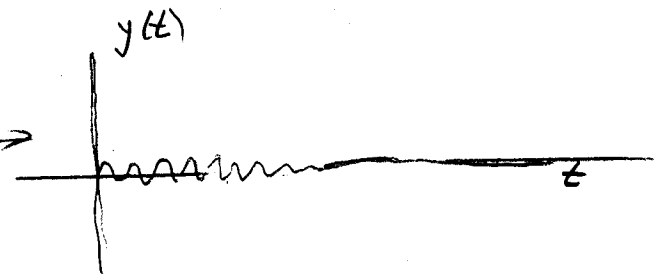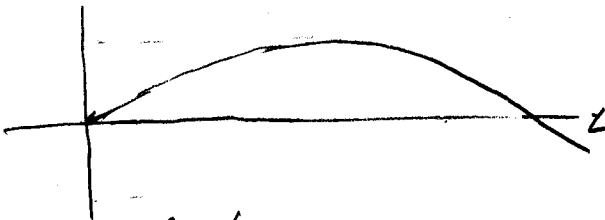

very high freq tone

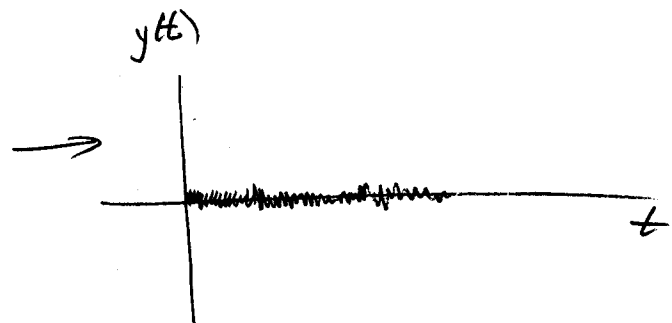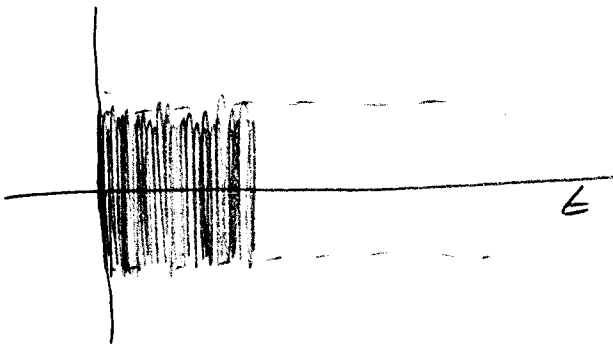


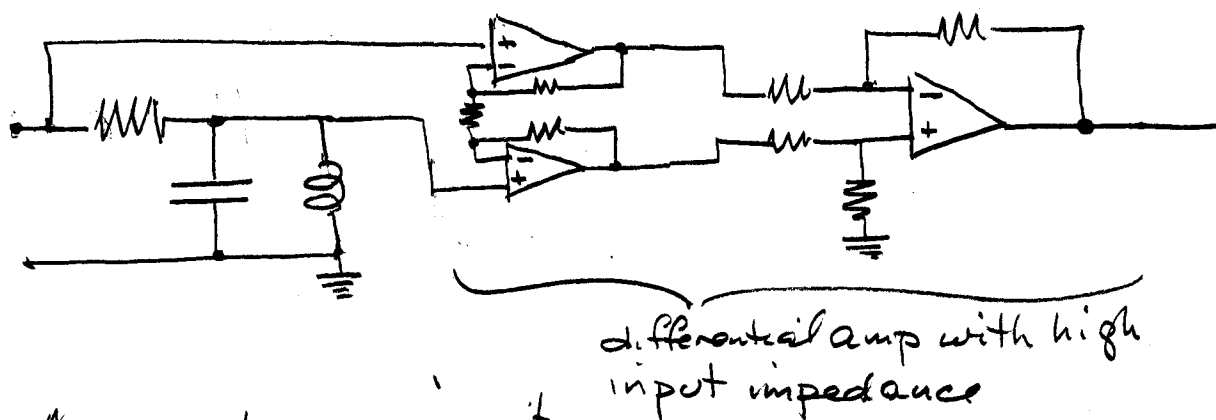- A notch eliminates single-tone interference



A very clumsy circuit.

h(t)

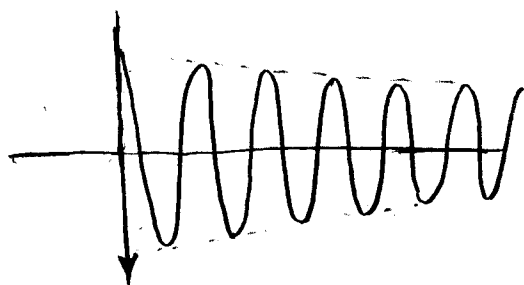

At resonance, the output of the tank circuit is in phase with the input and at the same amplitude. The " $-s(t)$ " branch subtracts the input, so response is zero

