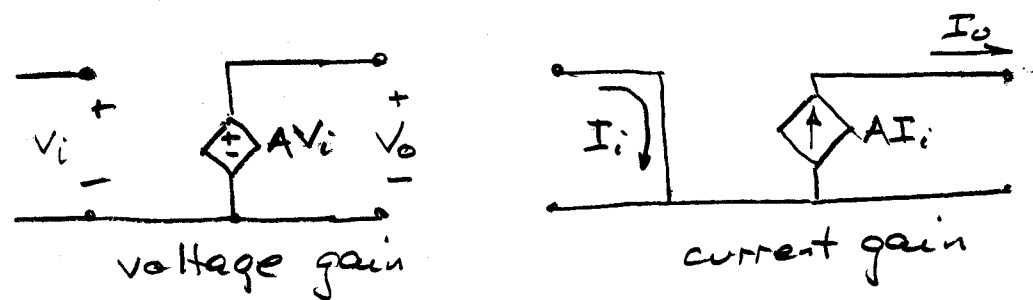


5.5 Sallen-Key and Related Active Filters


5.5.1

- Although passive filters are the best (or only) choice for some applications, their inductors are a nuisance for most purposes:
 - not completely linear
 - relatively expensive to make
 - bulky — very hard to put on an IC
- Active filters incorporate dependent sources — usually op amps, sometimes transistors — that allow complex poles with just R, C elements.
- The approach is similar to the way we do passive filters: select a normalized prototype of some structure, then scale it to your specs.


- Revisit impedance scaling with dependent sources.



dimensionless gains are unaffected

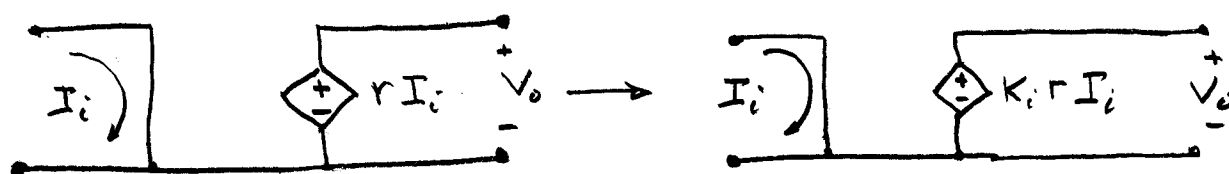

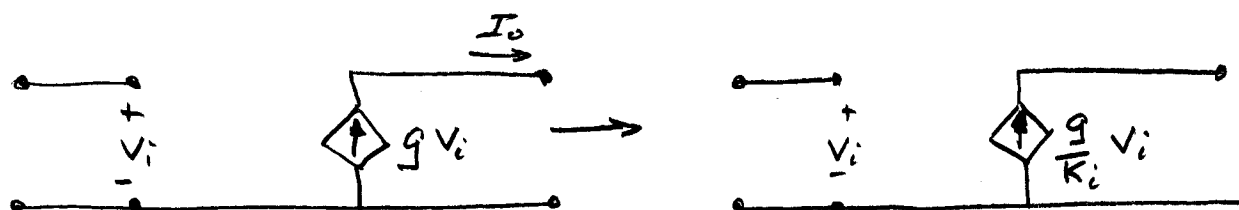
transresistance is scaled proportional to K_i



transconductance is scaled inversely proportional to K_i


• Sallen and Key designs DC + L 21.6

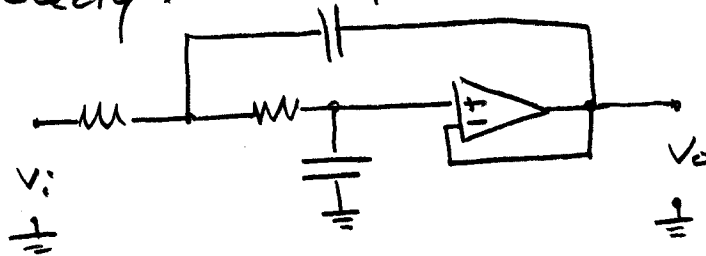- Sallen and Key designs incorporate an op amp configured as a voltage controlled voltage source (VCVS). You have seen one example already. From p. 3.1.10, a Sallen & Key lowpass



unit gain VCVS,
non-inverting

- The general S+K lowpass is

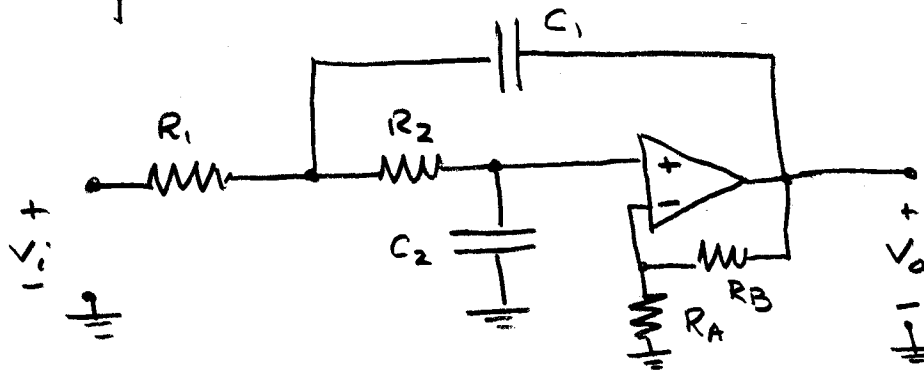

→ R_A, R_B serve to set the gain K of the embedded VCVS.

→ R_1, R_2, C_1, C_2 take various values depending on K

- Its transfer function:


$$H(s) = \frac{K}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2}\right)s + \frac{1}{R_1 R_2 C_1 C_2}}$$

and in normalized form

$$H(s) = \frac{K}{s^2 + \frac{1}{Q}s + 1}$$


for $\omega_0 = 1$,
 $2\zeta\omega_0 = 2\zeta = \frac{1}{Q}$
 Note DC gain K

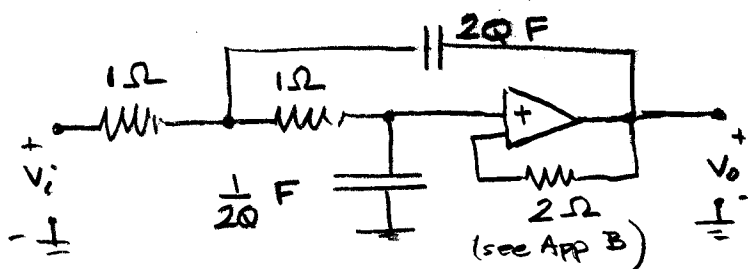- Three common forms: $K=1, 2, 4/3$ and match coeffs.




$K=1$

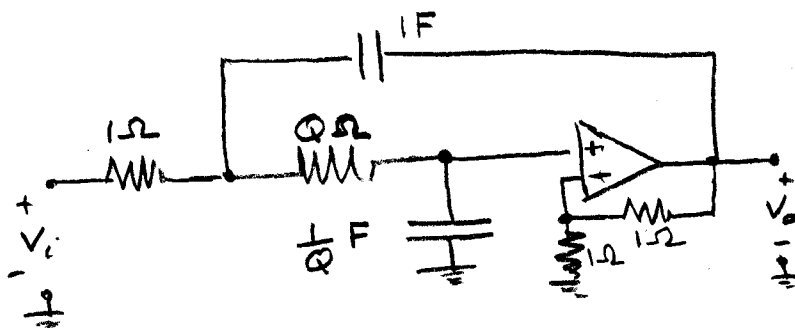Not bad, but
 relative cap sizes
 can get large
 $\frac{2Q}{1/2Q} = 4Q^2$ bias currents?



$K=2$

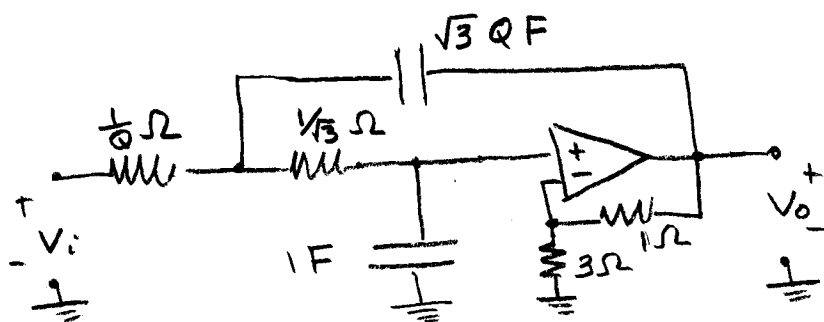component ratio is
 now $\frac{R_2}{R_1} = \frac{C_1}{C_2} = Q$,
 quite tolerable




$K=4/3$

less sensitive to
 component error.
 component ratio
 tolerable.

- Note $K=2, K=4/3$ designs should ideally choose
 $R_2 \parallel R_b \approx R_1 + R_2$ respectively, to minimize bias current effects.

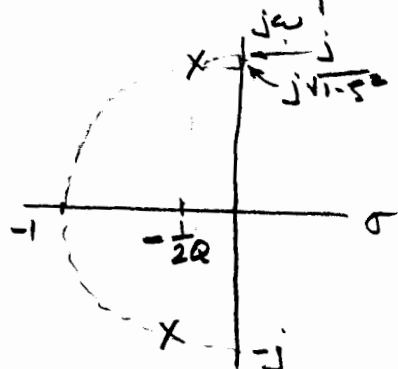- These three Sallen-Key designs implement the lowpass form of a (possibly) resonant filter. Two poles, no zero



on unit circle, since
normalized to $\omega_0 = 1$

$$\gamma\omega_0 = \gamma = \frac{1}{2Q}$$

- These are not the only Sallen-Key designs. We have five parameters: R_1, R_2, C_1, C_2, K , and three criteria: ω_c, Q , reasonable impedances.


- Suppose you have implemented a quad section using one of the three, but component value variation causes ω_c, Q to be off a little. Then

$$H(s) = \frac{\frac{K}{R_1 R_2 C_1 C_2}}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

(2) The result of
step (1) gives wrong
 Q . Adjust K to fix it.

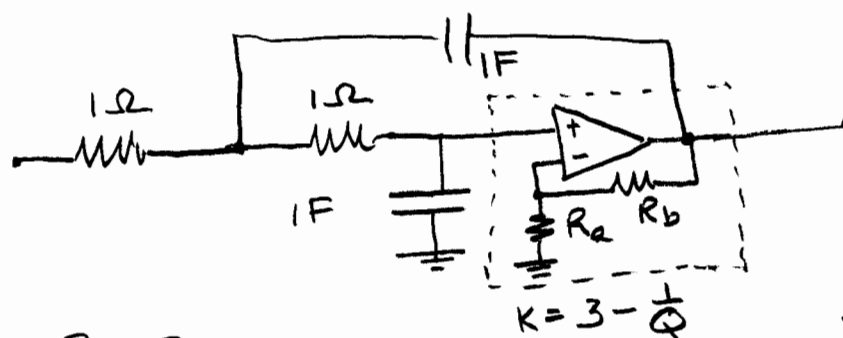(1) adjust these
to get ω_0

- Another canned design (but more sensitive to component variation):



$$\frac{R_b}{R_2} = 2 - \frac{1}{Q}$$

$$\text{for } K = 3 - \frac{1}{Q}$$

$$R_1 = R_2 = R$$


$$C_1 = C_2 = C$$

$$K = 3 - \frac{1}{Q}$$


$$\omega_0 = \frac{1}{RC} = 1 \text{ for proto section.}$$

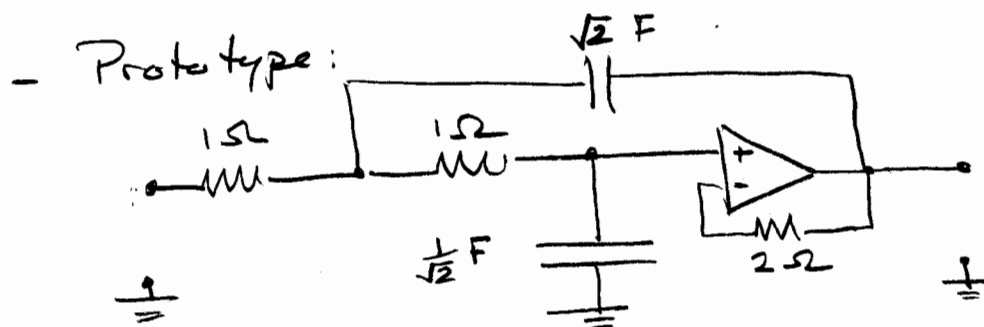• example.


- Design a 2nd order Butterworth active filter with cutoff frequency $\omega_c = 10 \text{ krad/s}$.
- Choose Sallen and Key structure because it's the only one we know so far. The Q factor $Q = \frac{1}{2\zeta} = \frac{1}{\sqrt{2}}$, so the $K=1$ design should work.



- Step 1: Frequency scale $K_f = 10^4$

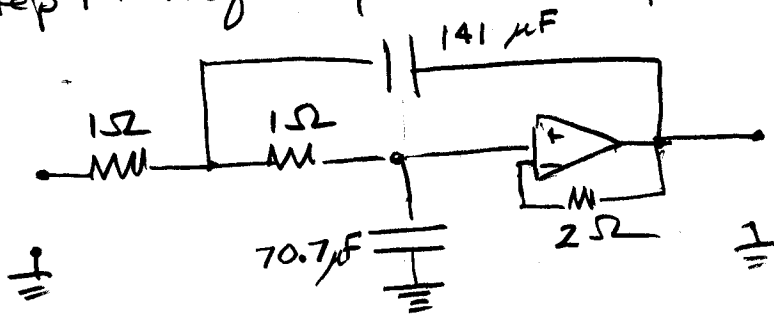

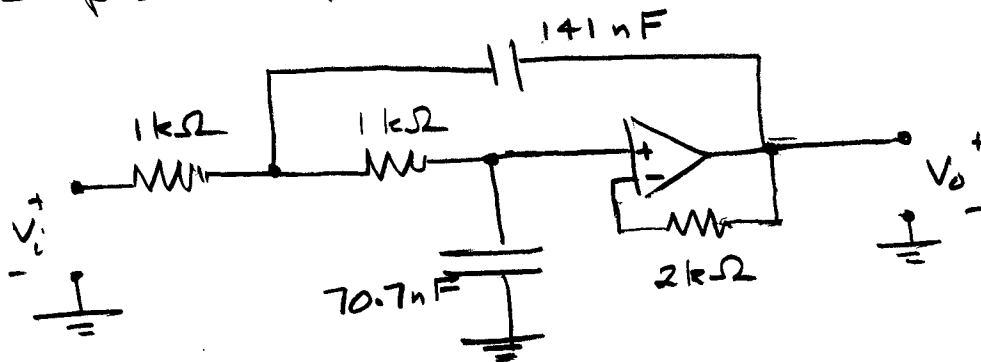- Step 2: Impedance scale (and compensate input bias current)
 $K_i = 1000$





- The dc gain is $K = 1$ here. Your text shows how to change this without changing other aspects of the transfer function

$$\boxed{DC + L 21.7}$$

- So far this has been easy. However, all we have tackled is a second order filter


• Higher order filters

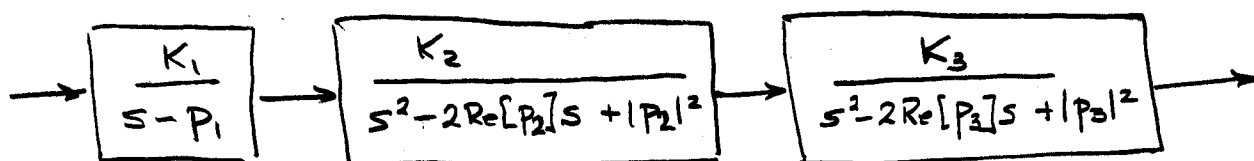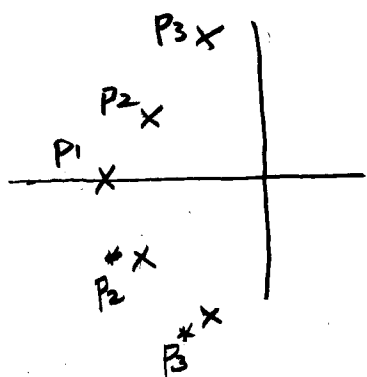- How to structure a 5th order filter? Trying complex arrangements of 5 capacitors, several resistors and some op amps is not attractive.
- Solution: Structure it as a cascade of quadratic sections (plus a first order section if the order is odd).



This is why tables of filter coefficients are often presented as products of quadratics.


- We already know how to implement

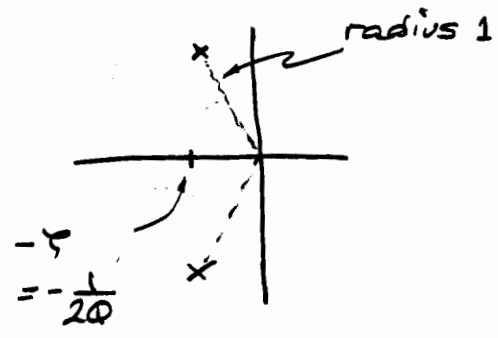

$$H(s) = \frac{K}{s^2 + \frac{1}{Q}s + 1} = \frac{K}{s^2 + 2\gamma s + 1}$$

for unit natural frequency.

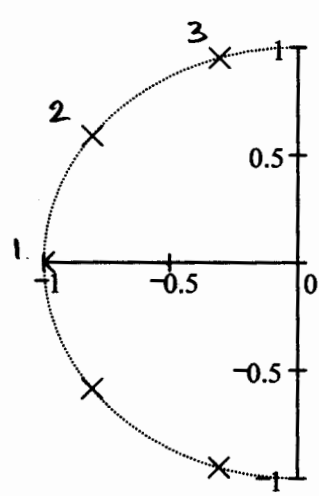- example Start with Butterworth, since all poles have the same radius. Try for a 5th order Butterworth, 3 dB bandwidth $\omega_c = 10 \text{ krad/s}$.




$p_3 = -0.309 + 0.951j$	$\rightarrow$	1.618	Q_3	Hmm. Golden mean values. $Q_3 = \frac{1}{Q_2}$
$p_2 = -0.809 + 0.588j$	$\rightarrow$	0.618	Q_2	
$p_1 = -1$	$\rightarrow$			
$p_2^* = -0.809 - 0.588j$	$\rightarrow$			
$p_3^* = -0.309 - 0.951j$	$\rightarrow$			


$Q = \begin{pmatrix} 1.618 \\ 0.618 \end{pmatrix}$

or from Table, p. 5.2.2


- Normalized Butterworth filter:

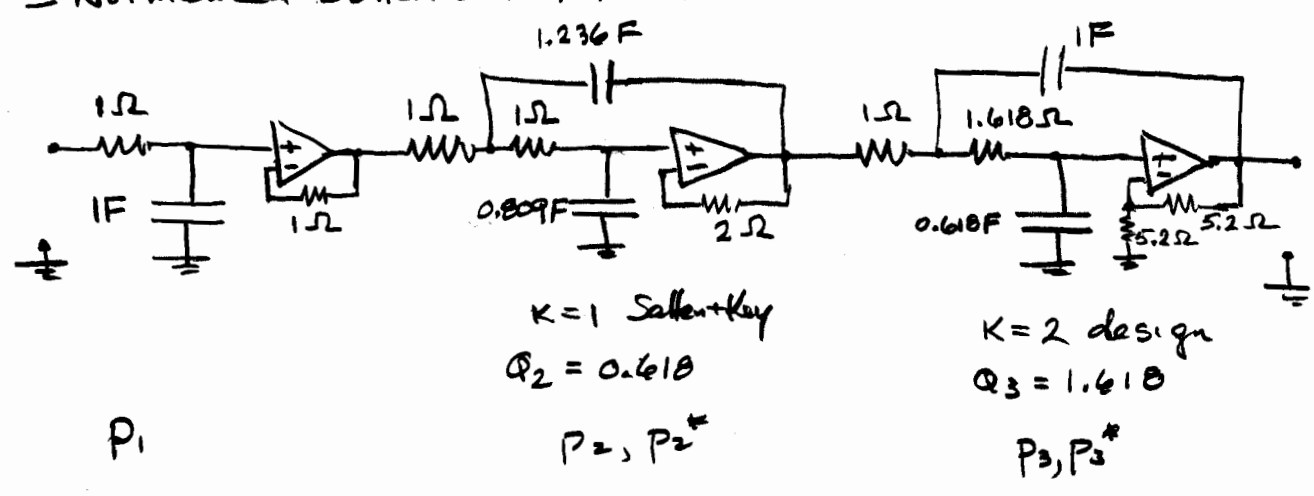

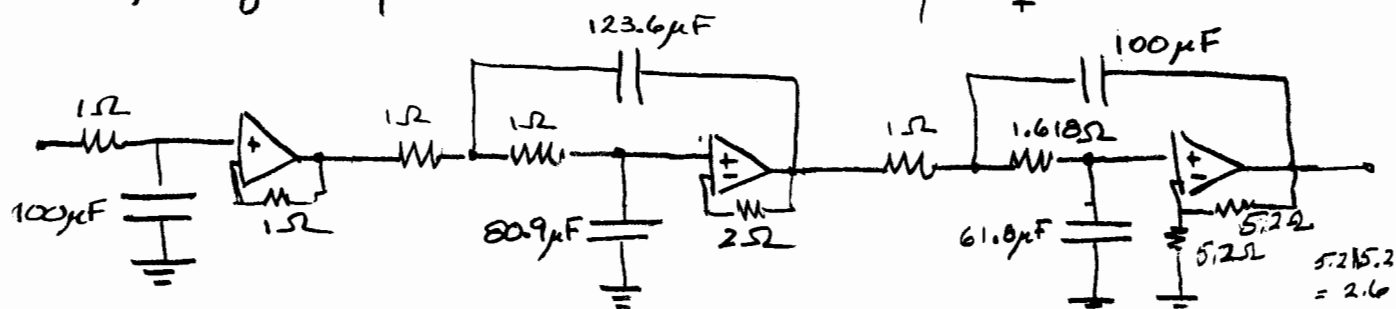
- Next, frequency scale all sections by $K_f = 10^4$.



- And impedance scale by, say, 100:

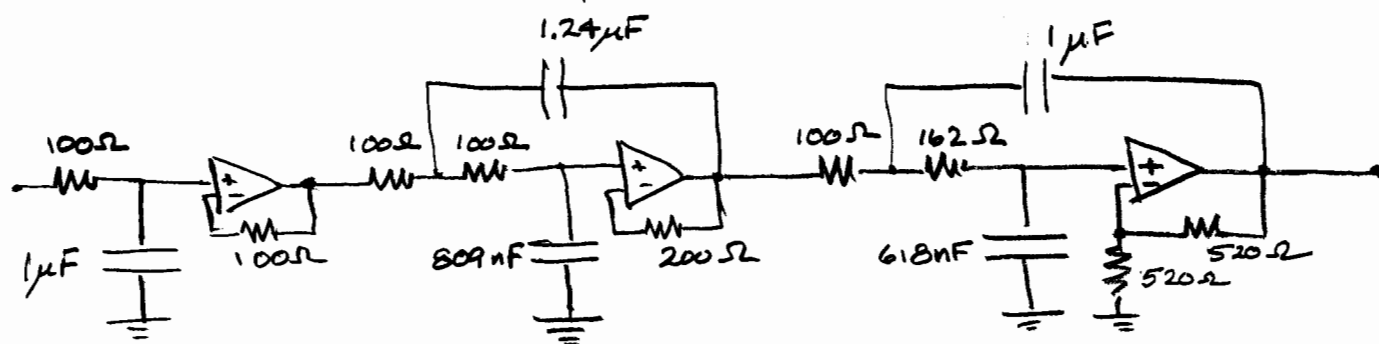

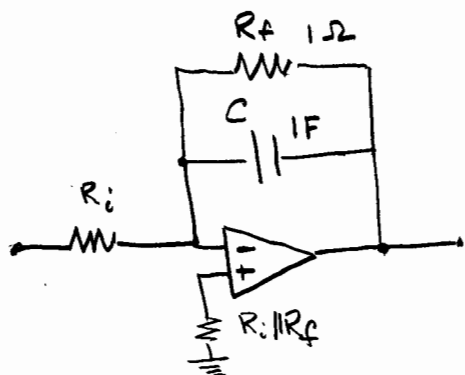- Note an alternative design for first-order stage




$$H(s) = -\frac{1/R_i C}{s + 1/R_f C}$$

shown for $\omega_c = 1 \text{ rad/s}$

Uses one more resistor, but DC gain $H(0) = R_f/R_i$ is selectable.

- High order Chebyshev filters are a little more complicated. Here's why:

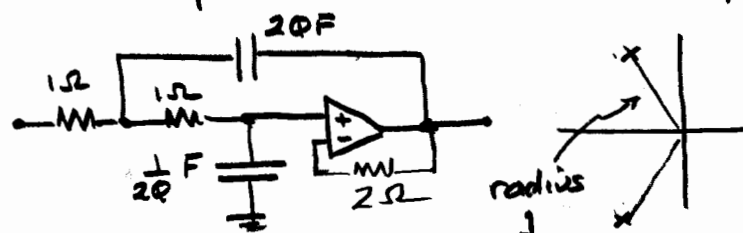- Our portfolio of prototype filters is set up for unit radius poles. For example,




$$H(s) = \frac{K}{s^2 + \frac{1}{Q}s + 1}$$

a special case of

$$H(s) = \frac{K\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

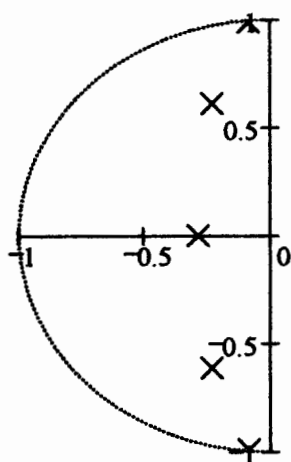- But the Chebyshev poles don't all have the same radius.



Chebyshev I filter, 1 dB ripple, 5th order. Pole locations, Q values and radii.

$$p = \begin{pmatrix} -0.089 + 0.99j \\ -0.234 + 0.612j \\ -0.289 \\ -0.234 - 0.612j \\ -0.089 - 0.99j \end{pmatrix}$$

$$Q = \begin{pmatrix} 5.589 \\ 1.4 \\ \dots \\ \dots \\ \dots \end{pmatrix}$$

$$\omega_0 = \begin{pmatrix} 0.994 \\ 0.655 \\ 0.289 \\ 0.655 \\ 0.994 \end{pmatrix}$$

Even though overall filter $\omega_p = 1$, individual sections have their own values for radius ω_0

and this means a different frequency scale factor for each pole when we implement

$$H(s) = \frac{0.123}{(s + 0.289)(s^2 + 0.468s + 0.429)(s^2 + 0.179s + 0.988)}$$

5th order, 1 dB ripple

- Here's how to handle implementation from the $H(s)$ polynomials without confusion:

- For each quadratic factor

$$s^2 + \frac{\omega_0}{Q} s + \omega_0^2,$$

calculate the Q . This number does not change with frequency scaling, which changes only the radius.

$$\text{eg } s^2 + 0.468 s + 0.429$$

$$Q = \frac{\sqrt{0.429}}{0.468} = 1.4$$

- For each denominator factor, linear or quadratic, calculate the pole radius, for use in frequency scaling.

$$\text{eg } s + 0.289 \quad \text{radius } \omega_0 = 0.289$$

$$\text{eg } s^2 + 0.468 s + 0.429$$

$$\omega_0 = \sqrt{0.429} = 0.655$$

— we could design it like this

→ sketch each unit-radius prototype filter with its own Ω .

→ frequency scale each prototype section down to its correct radius ω_0 ; the cascade of sections is now a Cheby filter for a unit passband.

→ frequency scale all sections by ω_p , the desired passband frequency.

but it is a lot easier to do one stage of scaling:

→ sketch each unit-radius prototype filter with its own Ω

→ frequency scale each section by $\omega_k \omega_p$, $k = 1 \dots \# \text{ of sections}$

— Each stage has dc gain equal to the gain of the embedded VCVS (i.e., 1, 2 or 4/3). The correct normalized gain of the cascade (if this is important) is

1, n odd

$\frac{1}{\sqrt{1+\epsilon^2}}$, n even

- example. Design a 5th order Chebyshev I filter with 1 dB passband ripple and a bandwidth $\omega_p = 10$ krad/s.

- From the table p. 5.3.7

$$H(s) = \frac{0.123}{\underbrace{(s+0.289)}_{\text{stage 1}} \underbrace{(s^2+0.4685s+0.429)}_{\text{stage 2}} \underbrace{(s^2+0.1795s+0.988)}_{\text{stage 3}}}$$

Note dc gain $H(0) = 1$.



- Find ω_0 , Q of each stage:

	<u>stage 1</u>	<u>stage 2</u>	<u>stage 3</u>
ω_0	0.289	$\sqrt{0.429} = 0.653$	$\sqrt{0.988} = 0.994$
Q		$\frac{\omega_0}{0.4685} = 1.4$	$\frac{\omega_0}{0.179} = 5.59$

- Frequency scale factors $K_{fk} = \omega_{0k} \omega_p$:


	<u>stage 1</u>	<u>stage 2</u>	<u>stage 3</u>
K_f	2,890.	6,550	9,940

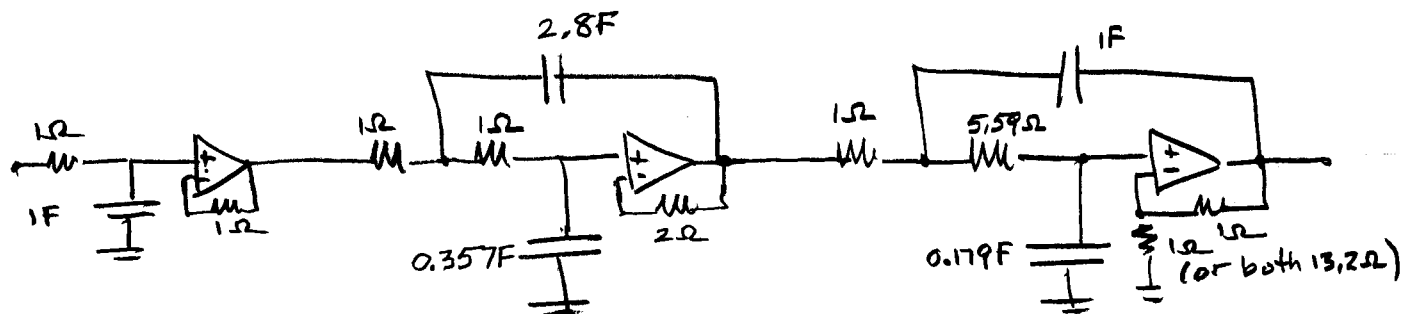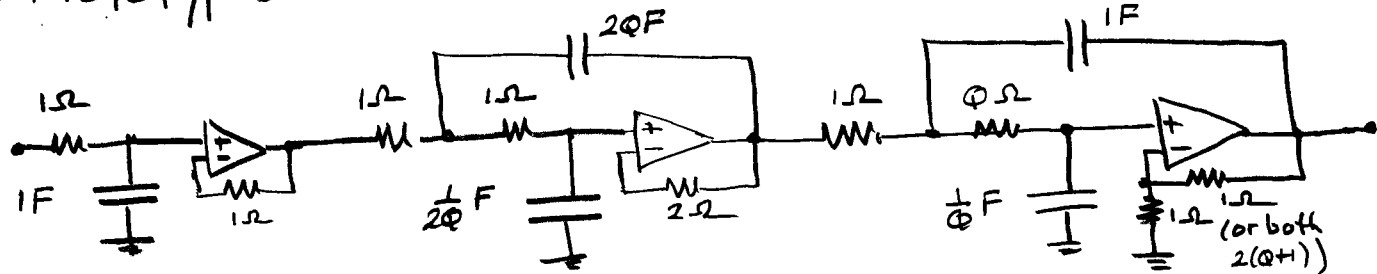- Prototypes with correct Q 's but incorrect K_F 's, K_i :




Note - this is not yet a Cheby filter

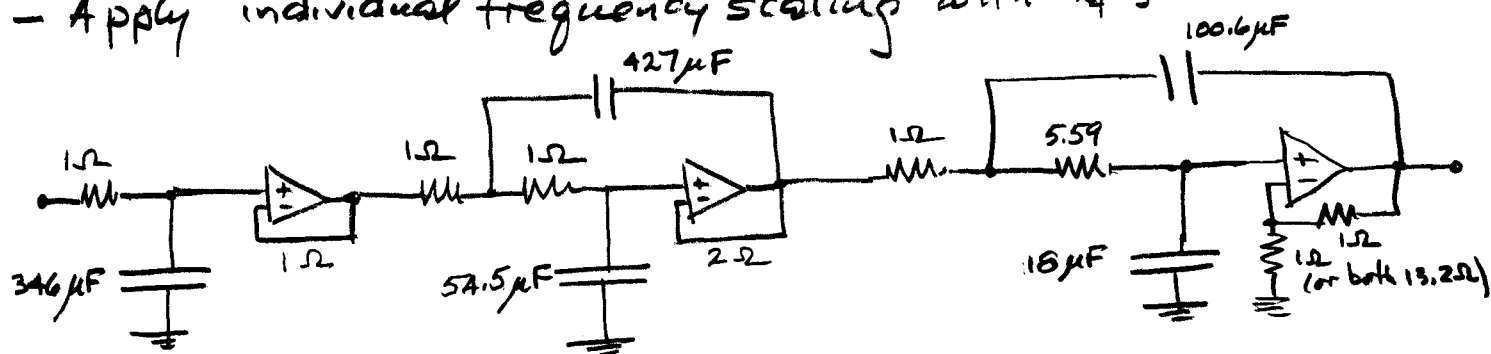- Apply individual frequency scaling with K_F 's



This is Chebyshev now.

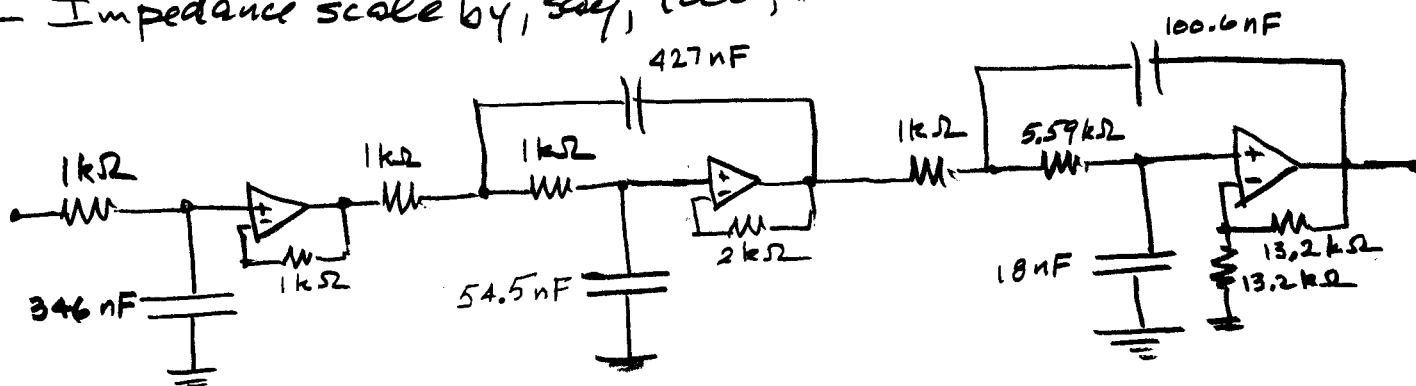- Impedance scale by, say, 1000, to obtain the final filter:



Done. DC gain is 2, contributed by 3rd stage.
Attenuate if you don't like it.