

6.5 Less-Than-Ideal Transformers DC+L 18.7 6.5.1

- Real-world transformers differ from the ideal model in several ways, such as:
 - (a) coupling coefficient $k < 1$
 - (b) finite permeability
 - (c) winding resistance and capacitance
 - (d) nonlinear ferromagnetic effects

The first three are linear, so we can model them using the methods of this course.

- Our models use an embedded ideal transformer. But we already have coupled coil models for $k < 1$ and finite μ — why bother with new ones?

- Coupled coil analysis usually has systems of equations
- Ideal transformers allow impedance, voltage and current transformations, so simpler analysis.


Modeling Finite Permeability

— Focus on finite μ , so $N_1 i_1 \neq -N_2 i_2$ and L_1, L_2, M are all finite.

— To keep it simple, retain $k=1$, so

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

— The coupled coil model, as usual, is

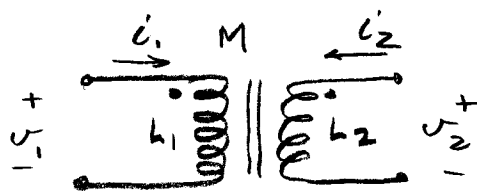


$$M = \sqrt{L_1 L_2} \text{ for } k=1$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = L_1 \frac{di_1}{dt} + \sqrt{L_1 L_2} \frac{di_2}{dt}$$

$$= L_1 \frac{d}{dt} \left(i_1 + \sqrt{\frac{L_2}{L_1}} i_2 \right)$$

which gives:

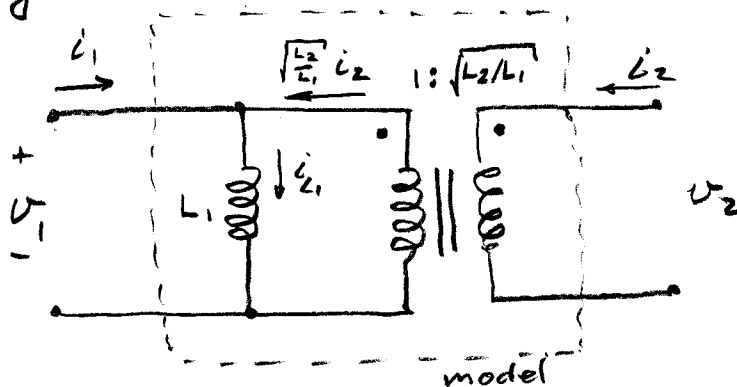looks like KCL with a current transformation




$$\text{since } V_1 = L_1 \frac{di_1}{dt} = L_1 \frac{d}{dt} \left(i_1 + \sqrt{\frac{L_2}{L_1}} i_2 \right)$$




The currents i_1, i_2 are no longer limited by $N_1 i_1 + N_2 i_2 = 0$

- A variation moves the inductor to the secondary, with impedance transformation. Seen from the secondary, L_1 looks like
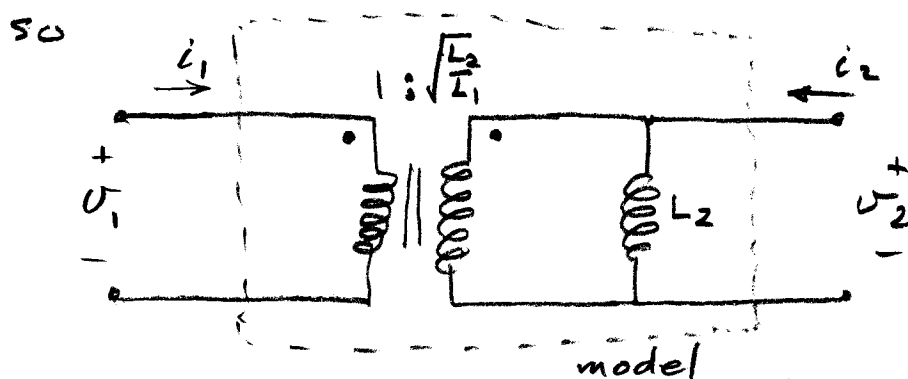
$$\underbrace{\left(\sqrt{\frac{L_2}{L_1}}\right)^2}_{\frac{N_2}{N_1}} L_1 = L_2$$




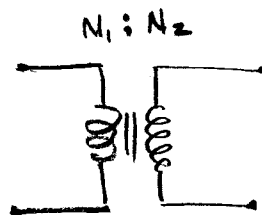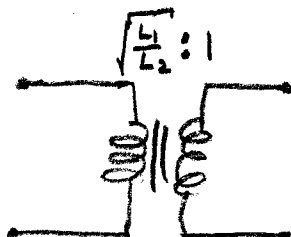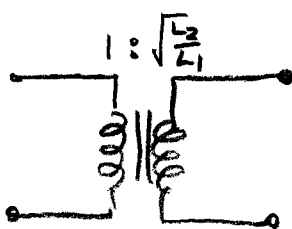Note that these ideal transformers are equivalent:




- example 18.15 from DC+L (resting on example 18.9)

– Radio front end:

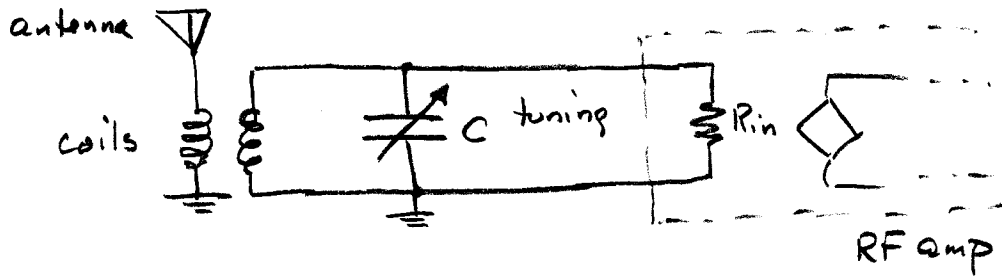

– Model with coils

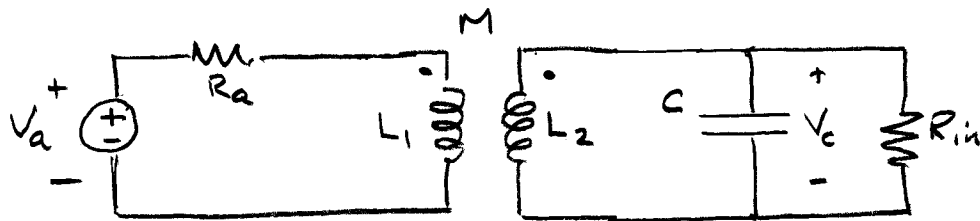

In example 18.9, values:


$$R_a = 300 \, \Omega$$

$$L_1 = 50 \, \text{nH} \quad L_2 = 2450 \, \text{nH} \quad M = 350 \, \text{nH} = \sqrt{L_1 L_2}$$

$$C = 104.5 \, \text{pF} \quad R_{in} = 14.7 \, \text{k}\Omega$$

- Use of coupled coil analysis gives coupled equations on the two sides which must be solved jointly.

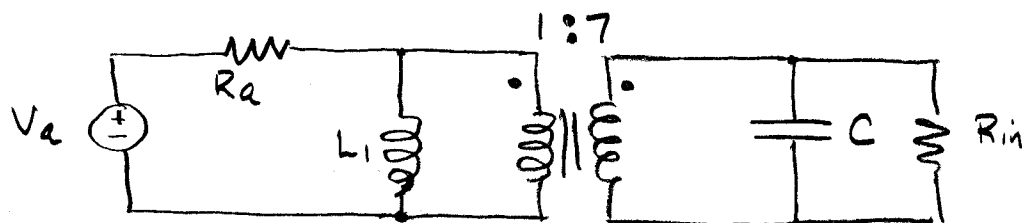
- New alternative: model coils with embedded ideal transformer



since $M = \sqrt{L_1 L_2} \Rightarrow k=1$

and $\sqrt{\frac{L_2}{L_1}} = \sqrt{\frac{2450}{50}} = 7$, $a = \frac{1}{7}$

Just refer secondary to the primary:

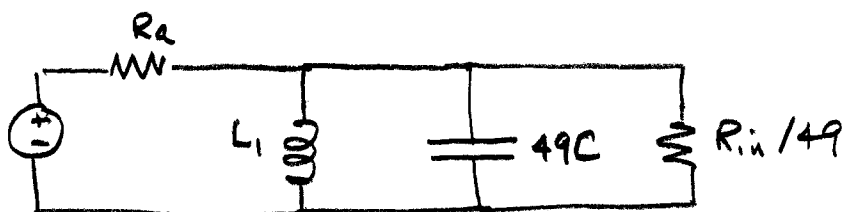


impedances scaled by a^2 ,
or $\frac{1}{49}$

Now it is a straightforward analysis.

Note that the cap looks bigger, so resonance frequency is 7 times lower than $\frac{1}{\sqrt{L_1 C}}$


Also, R_{in} appears as $R_{in}/49 = 14.7\text{k}\Omega/49 = 300\Omega$,
so it equals R_a — so max power transfer
at resonance, where the parallel LC
looks like an open circuit.

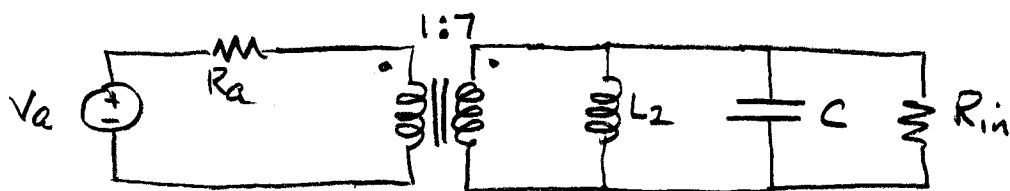- Even easier: use the model with inductor on the secondary



L_2 is $49L_1$ since unity coupling.

Transform the antenna:

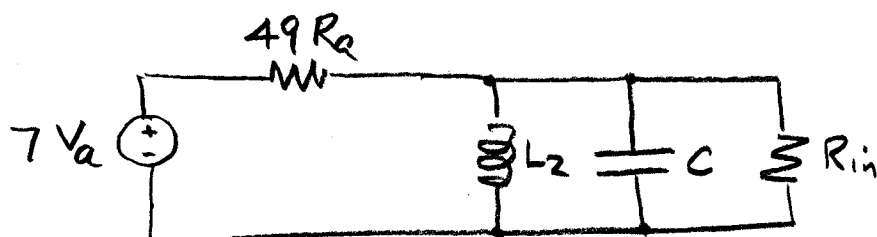


$49R_a = 49 \cdot 300 = R_{in}$, so matched at resonance

Voltage gain at resonance: $7 \times \frac{R_{in}}{R_{in} + 49R_a} = 3.5$

although no power gain in the transformer.



- A consequence of non-ideality is that impedance transformations with real transformers are only approximations of what you could obtain with ideal transformers (if you could obtain ideal transformers).

For example,

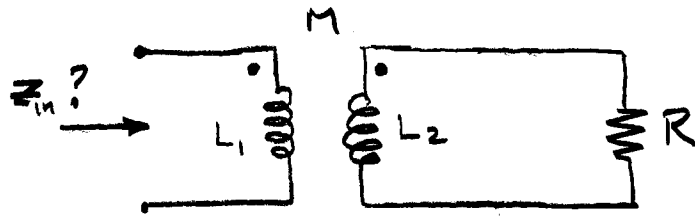

$$\text{Ideally, } Z_{in} = \left(\frac{N_1}{N_2}\right)^2 R = \frac{L_1}{L_2} R$$

More realistically,

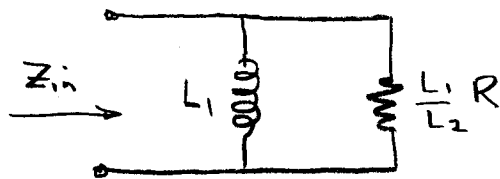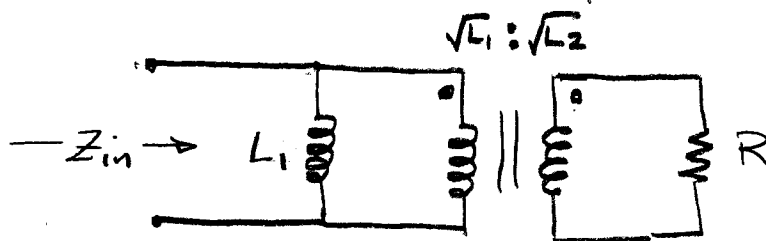


$$Z_{in}(s) = \frac{\frac{L_1}{L_2} R \cdot s L_1}{\frac{L_1}{L_2} R + s L_1} = \underbrace{\frac{L_1}{L_2} R}_{\text{ideal}} \cdot \underbrace{\frac{s}{s + \frac{R}{L_2}}}_{\approx 1 \text{ for } \omega \gg \frac{R}{L_2}}$$

If the frequency is too low, Z_{in} becomes small, since shunt L_1 has decreasing impedance.

Transformers don't work for DC.


• Modeling Finite μ and Coupling $k < 1$

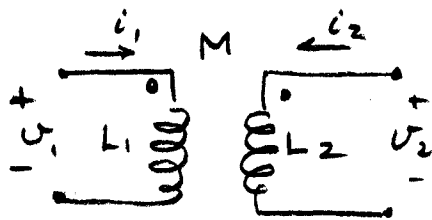- We can't quite reach $k=1$ in reality. If we have to account for $k < 1$, we could use coupled coil analysis, but it's tedious.
- There is a model with an embedded ideal transformer. Start with coupled coils



$$M^2 = k^2 L_1 L_2$$

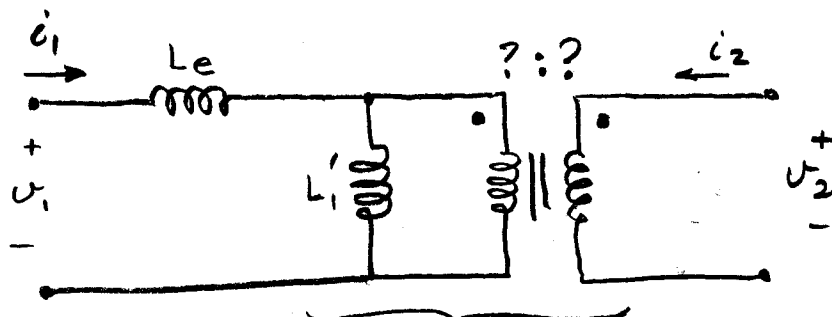Since $L_1, L_2 > M^2$, L_1 is larger than unity coupling with M, L_2 requires. Split L_1 into a unity coupling portion L_1' and the extra, L_e



based on unity coupling with M, L_2 .

- For the unity coupling subcircuit

$$L'_1 L_2 = M^2 = k^2 L_1 L_2$$

So


$$L'_1 = k^2 L_1$$

and the turns ratio is

$$1 : \sqrt{\frac{L_2}{L'_1}} \quad \text{or} \quad 1 : \sqrt{\frac{L_2}{M^2/L_1}}$$


$$\text{or } 1 : \frac{L_2}{M} \quad \text{or } M : L_2 \quad \text{or } \frac{M}{L_2} : 1 \text{ etc, etc.}$$

which gives

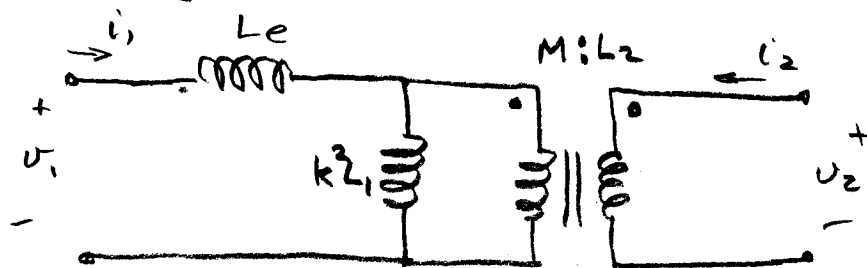


- The extra inductance $L_e = L_1 - k^2 L_1$
 $= (1 - k^2) L_1$

so final model is

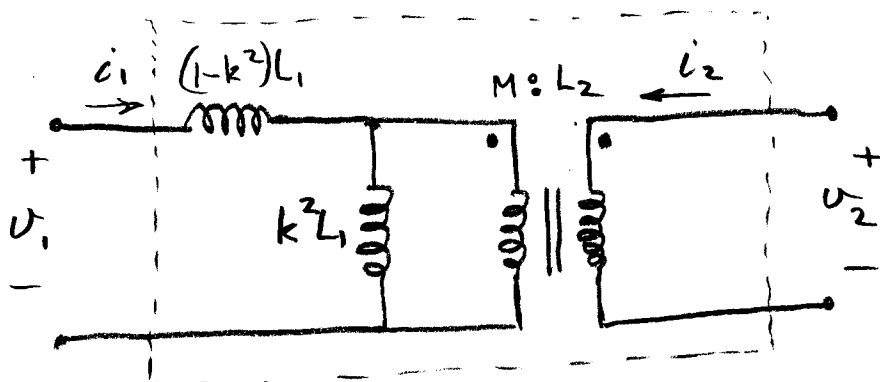


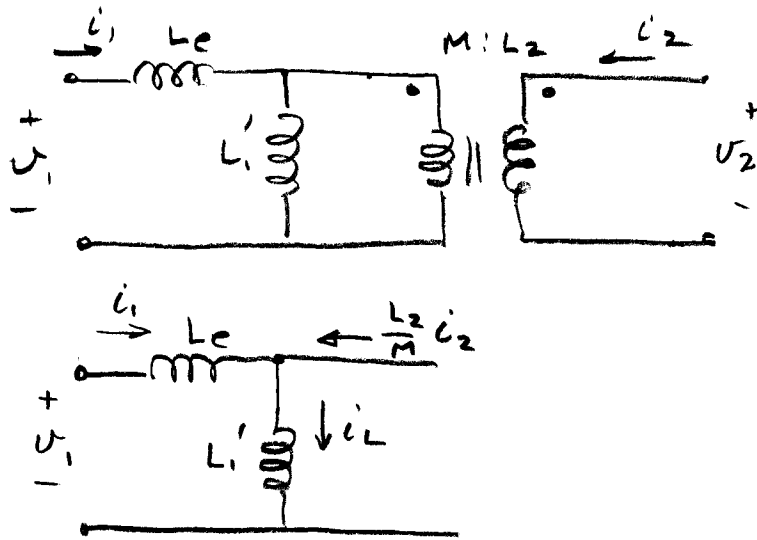- Quick confirmation that the model works: reduce it to coupled coils.



$$\begin{aligned}
 v_1 &= L_e \dot{i}_1 + L'_1 \left(\dot{i}_1 + \frac{L_2}{M} \dot{i}_2 \right) \\
 &= (1-k^2)L_1 \dot{i}_1 + k^2 L_1 \dot{i}_1 + \frac{L'_1 L_2}{M} \dot{i}_2 \\
 &= L_1 \dot{i}_1 + M \dot{i}_2
 \end{aligned}$$

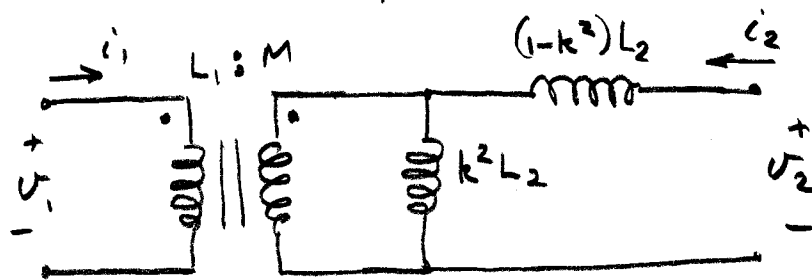- This model development could equally have broken up L_2




- And either of them could have referred the shunt inductor to the other side of the ideal transformer — four models

• Models for Some Other Non Idealities

6.5.11

- So far, even with $k < 1$ and finite μ , transformer models have been lossless - just inductors and ideal transformers.
- Real transformers have winding resistance and power loss due to hysteresis in the core. We can model them as resistors (approximately, in the case of hysteresis).

- Text presents (DC+L 18.8)

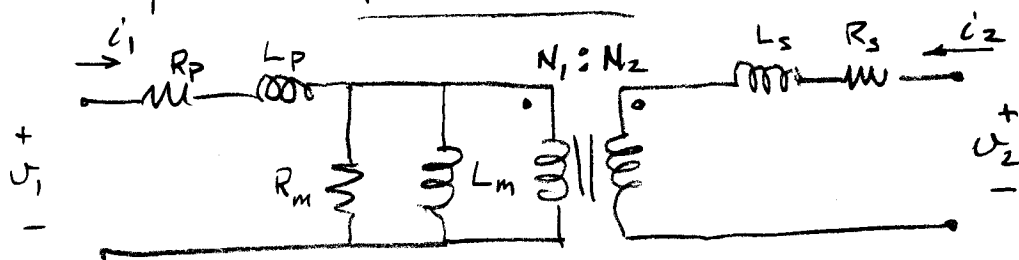

- We have already seen L_m (from finite μ) and L_p, L_s (from $k < 1$, but a more symmetric form).
- Resistors R_p, R_s are for windings, R_m for core loss.
- Then there is capacitance in the windings ...
- But enough! Consult a more advance text if necessary