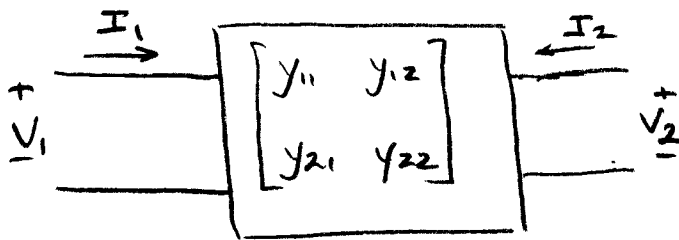


7.2 Admittance Parameter Analysis

7.2.1

DC+L 19.4, 19.5

- One way to characterize a two-port is with admittance parameters ("y parameters")



$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{or} \quad \begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$

where the elements are "short circuit admittances":

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

units:
Siemens

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

- We'll examine:
 - how to obtain y params from circuit diagram
 - how to calculate input impedance if two port is connected to load
 - how to calculate output impedance if two port is connected to source
 - how to calculate voltage gain if connected to source and load.

• Obtaining y-parameters from circuit diagram

— We can approach it in a couple of ways:


→ Work with the "short circuit" definitions explicitly; e.g.



and solve by circuit reduction or node, loop equations.

→ Or for a little more work, do all at once with a set of nodal equations.


— Simple example — passive circuit

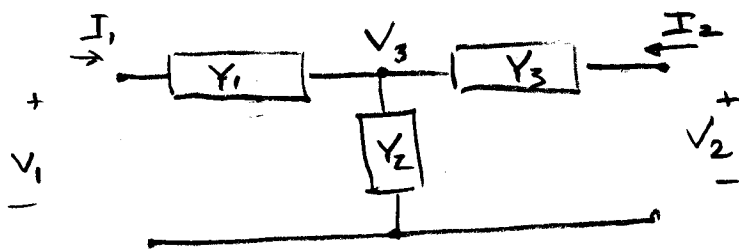

Y's are functions of s

By circuit reduction:
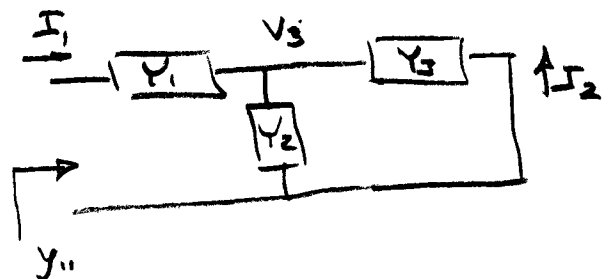
$$y_{11} = \frac{Y_1(Y_2 + Y_3)}{Y_1 + Y_2 + Y_3}$$



$$y_{21} = -\frac{I_2}{V_1} = -\frac{I_2}{V_3} \cdot \frac{V_3}{V_1} = -Y_3 \cdot \frac{\frac{1}{Y_2 + Y_3}}{\frac{1}{Y_1} + \frac{1}{Y_2 + Y_3}} = \frac{-Y_1 Y_3}{Y_1 + Y_2 + Y_3}$$

and so on.

- By nodal analysis, same circuit

$$I_1 = Y_1 V_1 - Y_1 V_3$$

$$I_2 = Y_3 V_2 - Y_3 V_3$$

$$0 = -Y_1 V_1 - Y_3 V_2 + (Y_1 + Y_2 + Y_3) V_3$$

or

$$\begin{bmatrix} I_1 \\ I_2 \\ 0 \end{bmatrix} = \begin{bmatrix} Y_1 & 0 & -Y_1 \\ 0 & Y_3 & -Y_3 \\ -Y_1 & -Y_3 & Y_1 + Y_2 + Y_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

All we want is equations in $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$, $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

so we should eliminate V_3 (and any other interior nodes, if it's a more complicated circuit).

Again, partition the matrix, for two sets of equations

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_1 & 0 \\ 0 & Y_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} -Y_1 \\ -Y_3 \end{bmatrix} V_3$$

$$0 = \begin{bmatrix} -Y_1 & -Y_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + [Y_1 + Y_2 + Y_3] V_3 \quad \leftarrow \text{solve for } V_3, \text{ subst into first eq'n.}$$

Solve 2nd equation for unwanted variable(s):

$$V_3 = -(Y_1 + Y_2 + Y_3)^{-1} \begin{bmatrix} -Y_1 & -Y_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Note nodal equations lend themselves to admittance analysis

and substitute:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_1 & 0 \\ 0 & Y_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} - \begin{bmatrix} -Y_1 \\ -Y_3 \end{bmatrix} (Y_1 + Y_2 + Y_3)^{-1} [-Y_1 - Y_3] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$= \left(\begin{bmatrix} Y_1 & 0 \\ 0 & Y_3 \end{bmatrix} - \frac{1}{Y_1 + Y_2 + Y_3} \begin{bmatrix} Y_1^2 & Y_1 Y_3 \\ Y_3 Y_1 & Y_3^2 \end{bmatrix} \right) \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$= \frac{1}{Y_1 + Y_2 + Y_3} \begin{bmatrix} Y_1 Y_2 + Y_1 Y_3 & -Y_1 Y_3 \\ -Y_3 Y_1 & Y_1 Y_3 + Y_2 Y_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$= \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Done. It agrees with calculation on previous page.

Now read DC+L example 19.7. Erratum: fourth eq'n p.809 should not contain $[s+3][s+3]$.

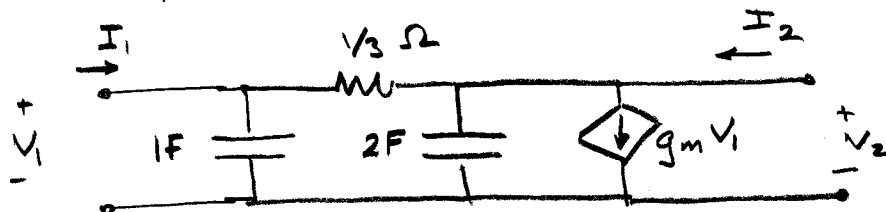- example with controlled source (like DC+L ex 19.6)



an easier example

Nodal equations again:

$$I_1 = s V_1 + 3(V_1 - V_2) = (s+3)V_1 - 3V_2$$

$$I_2 = g_m V_1 + 2s V_2 + 3(V_2 - V_1) = (g_m - 3)V_1 + (2s+3)V_2$$

or


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} s+3 & -3 \\ g_m-3 & 2s+3 \end{bmatrix}}_{\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Now read DC+L ex 19.8, with transformer.


- At this point, we have the tools to reduce any two-port circuit to the y parameters.

• A dependent-source model of a two-port circuit:
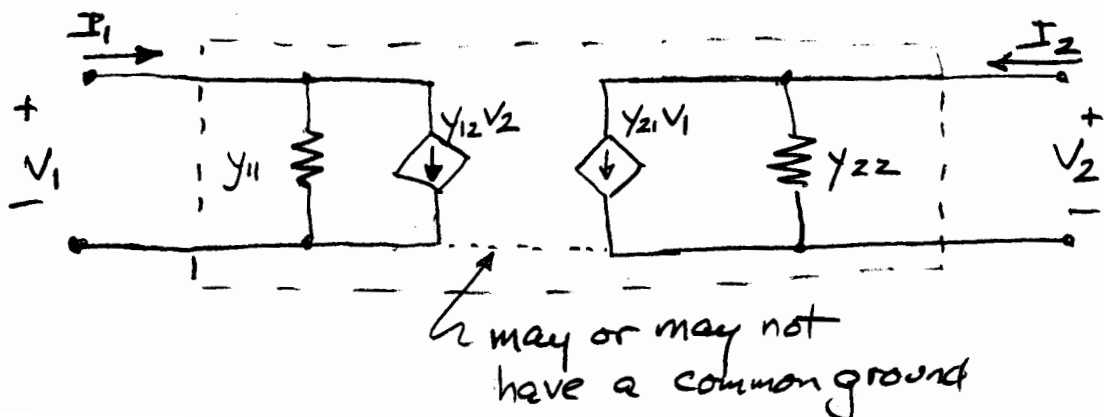
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{or} \quad \begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$



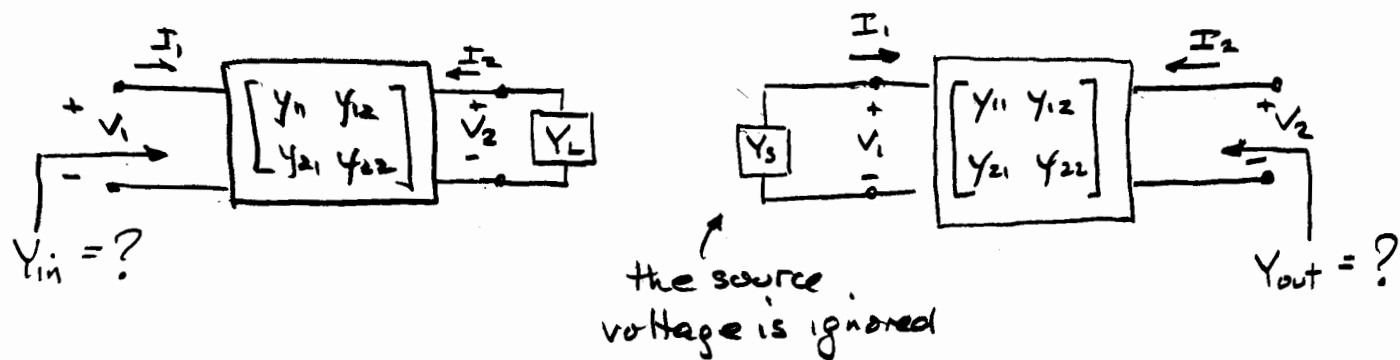• Calculating input and output admittances




- DC+L shows input admittance

$$Y_{in} = y_{11} - \frac{y_{12} y_{21}}{y_{22} + Y_L}$$

note pattern
of subscripts

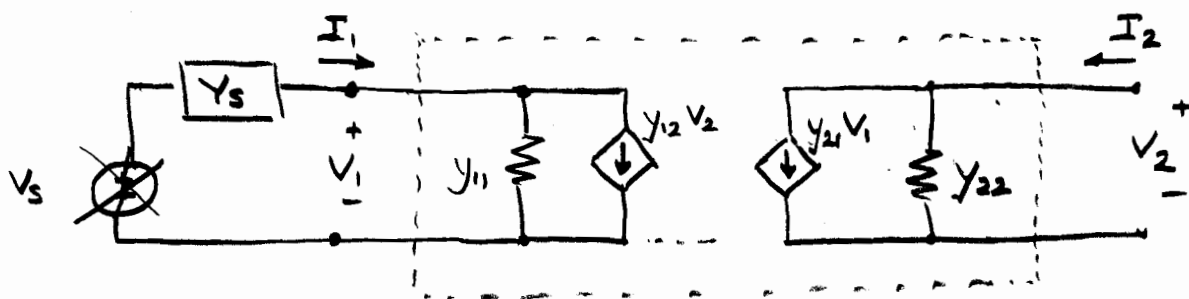- We can use this and symmetry to obtain Y_{out} .
Instead, do it ground-up, for the I_2, V_2 relation.



① Find V_1 on input side

$$y_{12} V_2 = -V_1 (y_{11} + Y_s)$$

or $V_1 = -V_2 \frac{y_{12}}{y_{11} + Y_s}$

② Eliminate V_1 on output side

$$\begin{aligned} I_2 &= y_{22} V_2 + y_{21} V_1 \\ &= y_{22} V_2 - \frac{y_{12} y_{21}}{y_{11} + Y_s} V_2 \end{aligned}$$

$$= \left(y_{22} - \frac{y_{12} y_{21}}{y_{11} + Y_s} \right) V_2$$

③


$$Y_{out} = y_{22} - \frac{y_{12} y_{21}}{y_{11} + Y_s}$$

note pattern of subscripts.

- example - the circuit of p. 7.2.4 with $g_m = 4$

7.2.7

Add a source and a load.

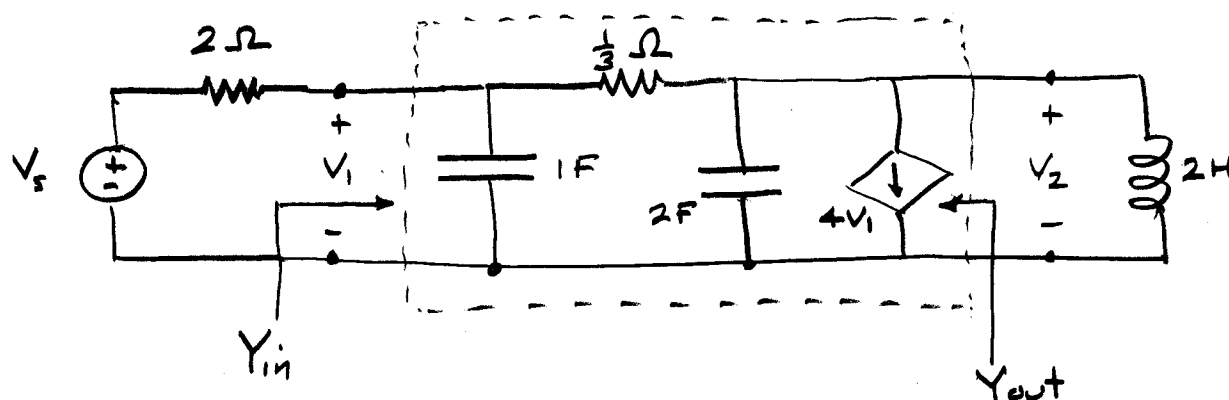

$$Y_s = \frac{1}{2}$$

$$\begin{bmatrix} s+3 & -3 \\ 1 & 2s+3 \end{bmatrix}$$

$$Y_L = \frac{1}{2s}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

Having done the work to obtain the admittance parameters of the two port, we don't have to solve it again.

$$Y_{in}(s) = y_{11} - \frac{y_{12} y_{21}}{y_{22} + Y_L} = s+3 - \frac{-3}{2s+3 + \frac{1}{2s}}$$

$$= \frac{4s^3 + 18s^2 + 25s + 3}{4s^2 + 6s + 1}$$

indep of Y_s !


$$Y_{out}(s) = y_{22} - \frac{y_{12} y_{21}}{y_{11} + Y_s} = 2s+3 - \frac{-3}{s+3 + \frac{1}{2}}$$

indep of Y_L !

$$= \frac{4s^2 + 20s + 27}{2s+7}$$


• Calculating the voltage gain

— Attach a source and a load.

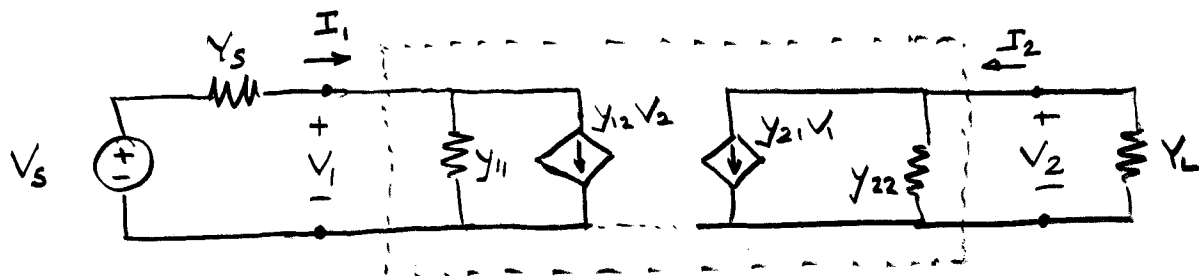


— What is the voltage gain $G_v = \frac{V_2}{V_s}$?

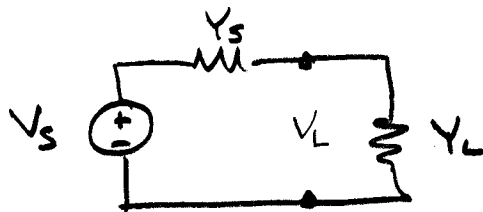— This is a reasonable question. We are used to asking it when we connect a source to a load:



$$V_L = \frac{Y_s}{Y_s + Y_L} V_s$$

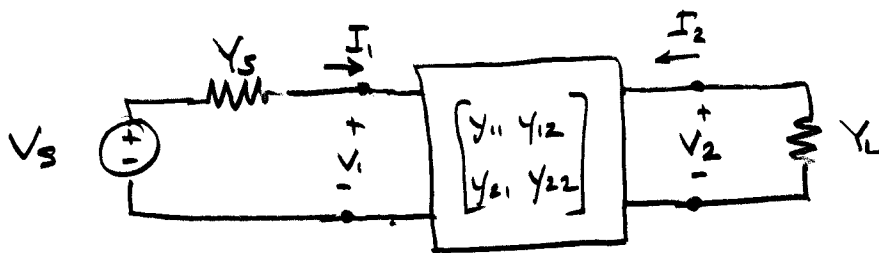Now we have a two port (e.g. amplifier, filter, etc) inserted between them



$$G_v = \frac{V_2}{V_s} = ?$$

— Following DC+L p.812:

$$G_v = \underbrace{\frac{V_2}{V_1}}_{G_{v2}} \cdot \underbrace{\frac{V_1}{V_s}}_{G_{v1}} \quad \text{and calculate them separately.}$$

First, $\frac{V_1}{V_s}$. Source sees




DC+L
erratum:
p. 813, first
equation
should be

$$G_{v1} = \frac{V_1}{V_s}$$

$$G_{v1} = \frac{V_1}{V_s} = \frac{Y_s}{Y_s + Y_{in}}$$

and Y_{in} depends on Y_L

Next, $\frac{V_2}{V_1}$. Load sees

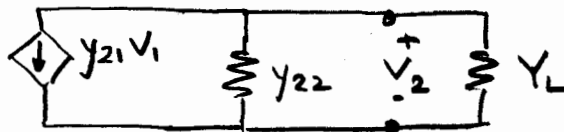

$$\text{So } V_2 = - \frac{y_{21} V_1}{y_{22} + Y_L}, \quad G_{v2} = - \frac{y_{21}}{y_{22} + Y_L}$$

Finally

$$G_v = G_{v1} \cdot G_{v2} = \left(\frac{Y_s}{Y_s + Y_{in}} \right) \cdot \left(\frac{-y_{21}}{y_{22} + Y_L} \right)$$

$$= \frac{-y_{21} Y_s}{(y_{22} Y_s + Y_s Y_L + y_{11} Y_L + y_{11} y_{22} - y_{12} y_{21})}$$

and

$$Y_{in} = y_{11} - \frac{y_{12} y_{21}}{y_{22} + Y_L}$$

- These are intricate equations, and we might reasonably ask why we should bother with them.

Answer: the four parameters and the source & load admittances (all functions of s) are a high-level summary of what can be elaborate circuits. They provide a "birds-eye" view of what's going on.