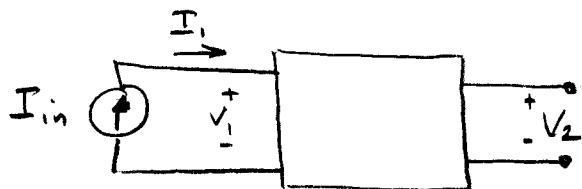


7.6 Reciprocal Networks


DC+L 19.10

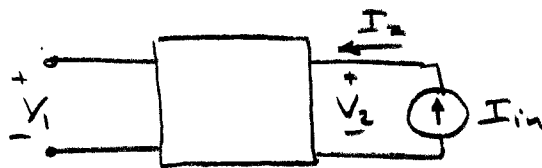7.6.1

- Recall that passive networks have symmetric y - and z -parameter matrices.
- This produces interesting properties.



the open circuit voltage response V_2 to current source I_{in} as I_1



is the same

the open circuit voltage response V_1 to current source I_{in} as I_2

Why?
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



Since $z_{12} = z_{21}$,

$$\left. \frac{V_2}{I_1} \right|_{I_2=0} = z_{21} = z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

Interchange current source and voltmeter,
no change to voltmeter reading.

It's no longer true if V_2 is terminated.

- Similarly,

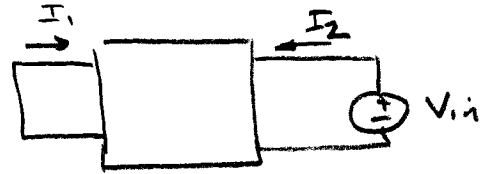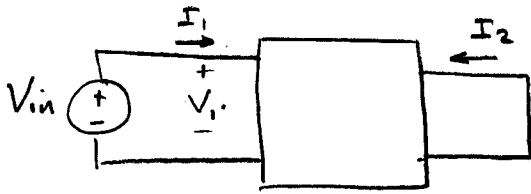

The short circuit current response to a voltage source on the other port is unaffected by an interchange.


Use y -parameters to see it.

- Reciprocal networks have equivalent circuits with no dependent voltage sources.

— First, for z -parameters,

$$V_1 = z_{11} I_1 + z_{12} I_2 = (z_{11} - z_{12}) I_1 + z_{12} (I_1 + I_2)$$
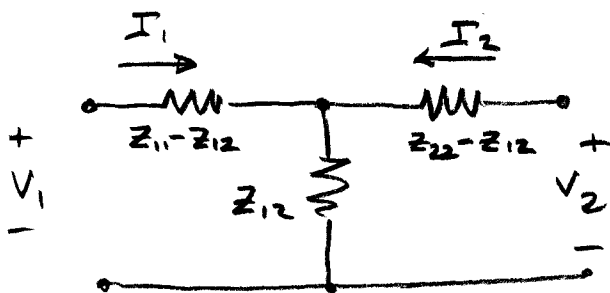
$$\begin{aligned} V_2 &= z_{21} I_1 + z_{22} I_2 = z_{21} (I_1 + I_2) + (z_{22} - z_{21}) I_2 \\ &= z_{12} (I_1 + I_2) + (z_{22} - z_{12}) I_2 \end{aligned}$$




T-equivalent for symmetric z params

— Next, y -parameters.

$$I_1 = y_{11} V_1 + y_{12} V_2 = (y_{11} + y_{12}) V_1 - y_{12} (V_1 - V_2)$$
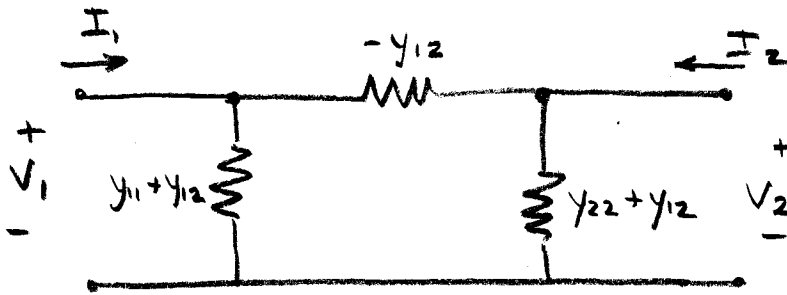
$$\begin{aligned} I_2 &= y_{21} V_1 + y_{22} V_2 = -y_{21} (V_2 - V_1) + (y_{22} + y_{21}) V_2 \\ &= -y_{12} (V_2 - V_1) + (y_{22} + y_{12}) V_2 \end{aligned}$$



Π -equivalent circuit for symmetric y -parameters.

Note DC+L
error p836

— So any passive network can be reduced to a T- or Π -equivalent network.