

8 THREE-PHASE CIRCUITS

8.0.1

DC+L Chpts 11, 12


- In this section, we shift our attention from filters and electronics to electric power:
 - how to calculate it
 - how to generate it
 - how to transmit it

We will deal solely with sinusoidal signals.


- Most of the topics in AC power apply equally to milliwatt electronics in the audio range, radio frequency circuits and megawatt 60 Hz power circuits — and almost all the topics will be familiar to you.
- Three phase power will be new to most of you, although you see examples of 3- ϕ systems almost every day. They are just three ordinary circuits with mutual phase angles of 120° ganged together. There are good reasons for doing so.

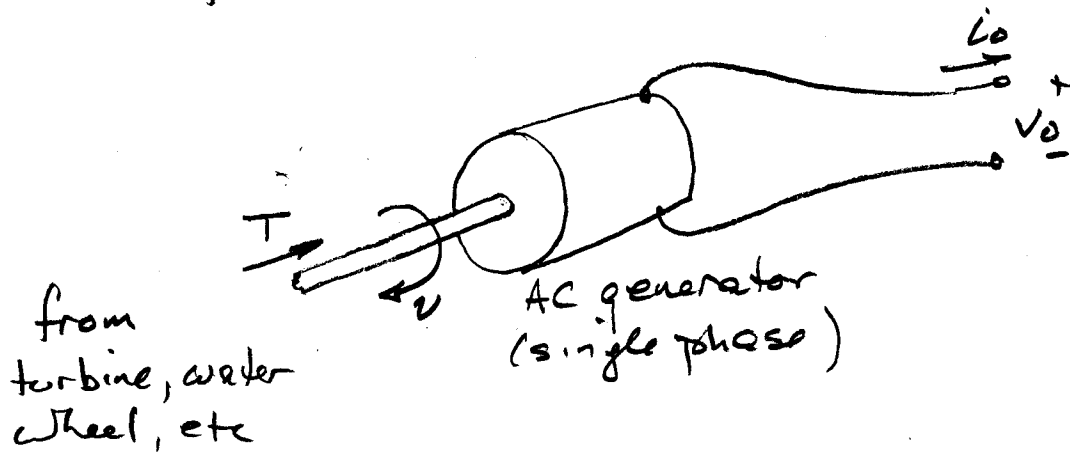8.1 Review of AC Power

- This is familiar stuff — instantaneous power, average power, power factor, rms quantities, impedance matching, etc. That's why it's a review.
- But first — where does AC power come from?



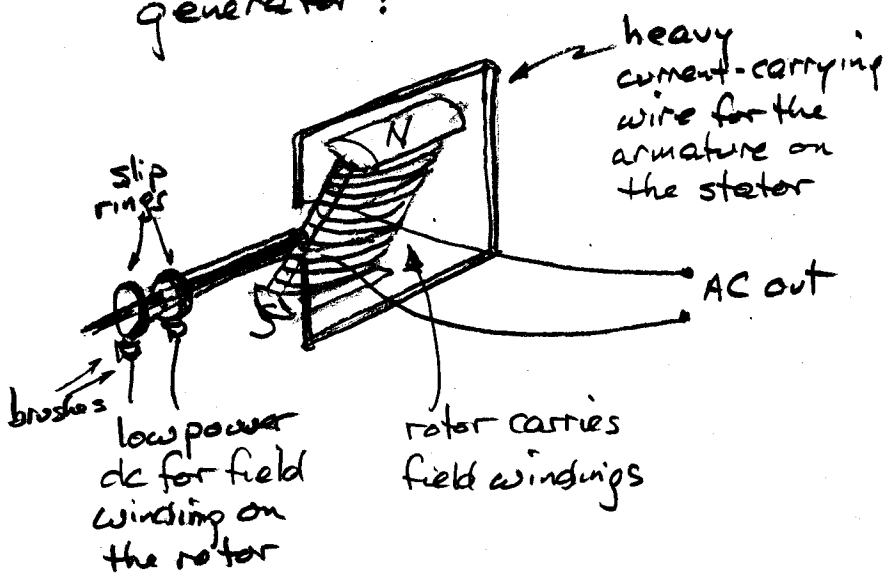
- Cross section of elementary two-pole, single phase generator:



Basic idea:


- Spin a magnet (the field) to induce voltage in a coil (the armature)
- Use an electromagnet powered through brushes and slip rings.

— Cross section again, showing iron:

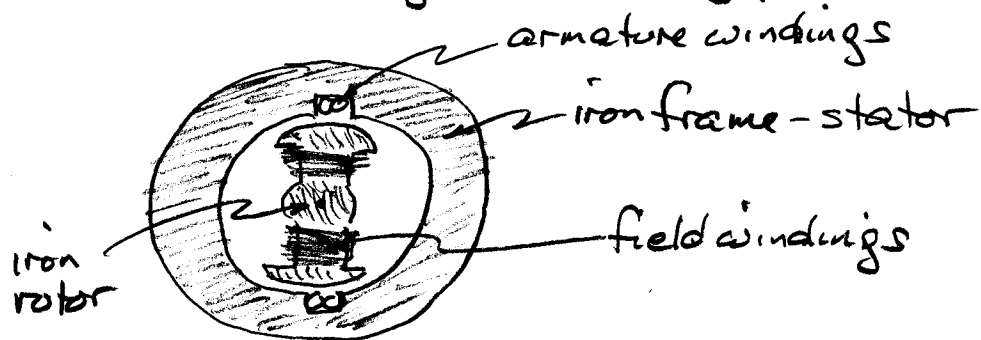


— Basic relations on the armature

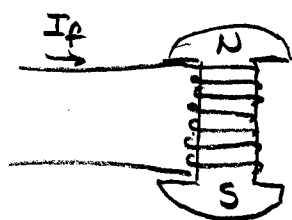- Generated voltage is proportional to rotor speed, field current (establishes B field), number of armature turns (wires).
- Torque experienced by turbine is proportional to armature current (depends on electrical load), field current, number of armature turns
- Generated frequency is proportional to rotor speed, number of poles.




two pole rotor

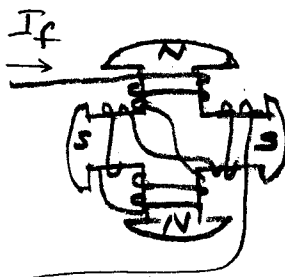

four pole rotor

Just imagine six!
(I won't draw it).
Quite common.

- This is an AC source

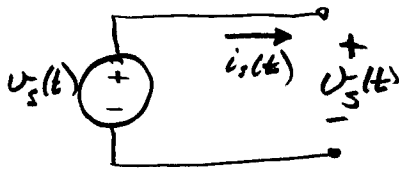

60 Hz in North America

50 Hz in UK, Aus, NZ

400 Hz in avionics

If the voltage is sinusoidal and the load is a linear circuit, then the current is sinusoidal with the same frequency.

$$v(t) = V_m \cos(\omega t + \theta_v) = \text{Re}[V e^{j\omega t}]$$


$\omega = 377 \text{ rad/s}$
here

$$\text{phasor } V = V_m e^{j\theta_v}$$

$$i(t) = I_m \cos(\omega t + \theta_i) = \text{Re}[I e^{j\omega t}]$$


- Instantaneous power varies across the cycle.

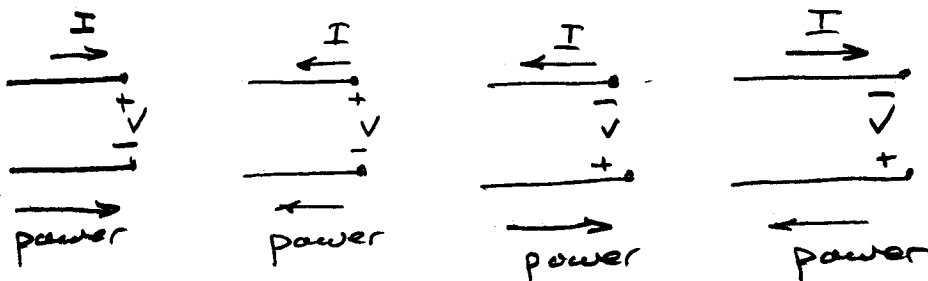- If it were dc, the direction of power flow would be like this:



but the voltage and current in AC vary over a cycle.

- Instantaneous power out of the source:

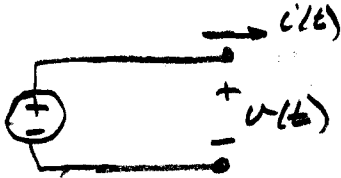

$$P(t) = v(t) i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \leftarrow \text{dc}$$

$$+ \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$


$\uparrow$ oscillates at 2ω

$$\begin{aligned} \cos(a) \cos(b) \\ = \frac{1}{2} \cos(a-b) \\ + \frac{1}{2} \cos(a+b) \end{aligned}$$

- First, consider current and voltage in phase

$$(\theta_i = \theta_v) \quad P(t) = \frac{1}{2} V_m I_m + \frac{1}{2} V_m I_m \cos(2\omega t + 2\theta_v)$$

$$= V I \cos^2(\omega t + \theta_v)$$

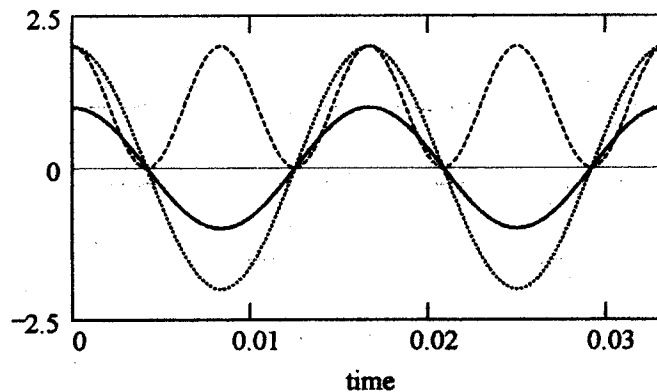


— voltage
- - - current
... power

$\theta_v - \theta_i = 0 \text{ deg lagging}$

→ Power fluctuates - it's not steady - 2ω

→ The average value of $\cos^2$ is $\frac{1}{2}$.

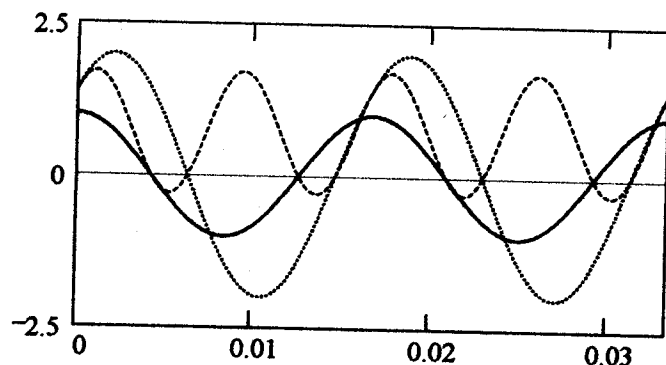
— Next, current lags voltage by 45° . Keep the same amplitudes



— voltage
— current
— power

time
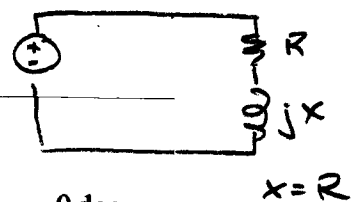
$$\theta_v - \theta_i = 45 \text{ deg lagging}$$





$$\theta_v = 0 \text{ deg}$$

$$\theta_i = -45 \text{ deg}$$

→ Same peak-to-peak power swing
→ Power flows back into source during part of the cycle!

— Now let current lag voltage by 90° .

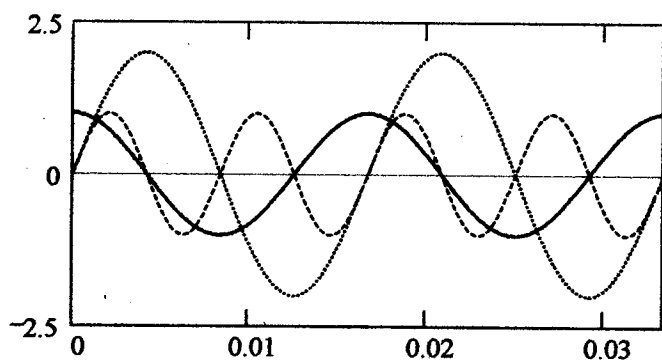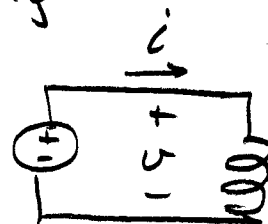

— voltage
— current
— power

time

$$\theta_v - \theta_i = 90 \text{ deg lagging}$$

$$\theta_v = 0 \text{ deg}$$

$$\theta_i = -90 \text{ deg}$$

→ Power flows out of source for $\frac{1}{2}$ cycle, back into it for $\frac{1}{2}$ cycle.
→ No net power flow either way.

- Lags of more than 90° cause net power flow into the source. The generator starts behaving like a motor (this can happen if the generator is connected to the power grid as a "load")
- Net (average) power doesn't depend on whether current lags or leads the voltage.

• Average power over a cycle is easy:

$$P(t) = \underbrace{\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)}_{\text{a constant, the average value}} + \underbrace{\frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)}_{\text{oscillatory, averages to zero}}$$

$$P_{av} = \underbrace{\frac{1}{2} V_m I_m}_{\substack{\uparrow \\ \text{a nuisance}}} \underbrace{\cos(\theta_v - \theta_i)}_{\substack{\text{the power factor (pf)} \\ \text{lagging pf if current lags voltage}}}$$

$$= V_{rms} I_{rms} \text{ p.f.}$$

Note — the p.f. can be positive (power to load)
or negative (power back into "generator")
or zero (if completely reactive load, 90°)


- A phasor interpretation:

$$v(t) = \operatorname{Re}[V e^{j\omega t}] \quad i(t) = \operatorname{Re}[I e^{j\omega t}]$$

$$P(t) = \operatorname{Re}[V e^{j\omega t}] \operatorname{Re}[I e^{j\omega t}]$$

$$= \frac{1}{2} \operatorname{Re}[VI^* + VI e^{j2\omega t}]$$
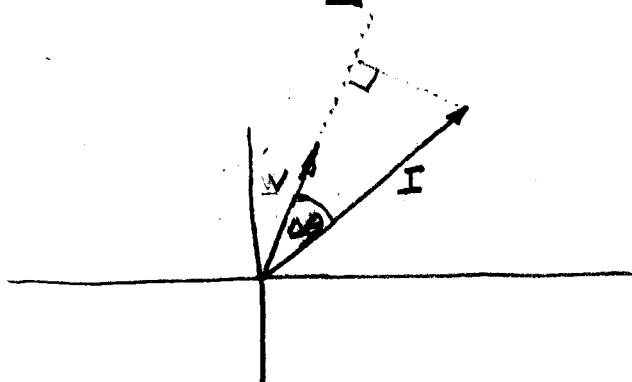
$$P_{av} = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\Delta\theta)$$




$I_m \cos(\Delta\theta)$ is the length of the projection of I onto V

$$\begin{aligned} \operatorname{Re}[\alpha] \operatorname{Re}[\beta] \\ = \frac{1}{2} \operatorname{Re}[\alpha\beta^* + \alpha\beta] \end{aligned}$$


covers many trig identities

- A complex interpretation:
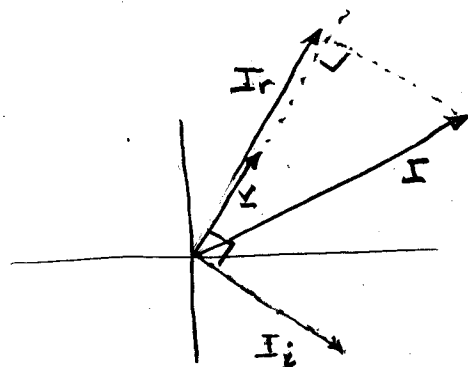
$$P = \frac{1}{2} VI^* = \underbrace{\frac{1}{2} \operatorname{Re}[VI^*]}_{\text{real power, watts}} + \underbrace{j \frac{1}{2} \operatorname{Im}[VI^*]}_{\text{reactive, imaginary, wattless power, VAR}}$$



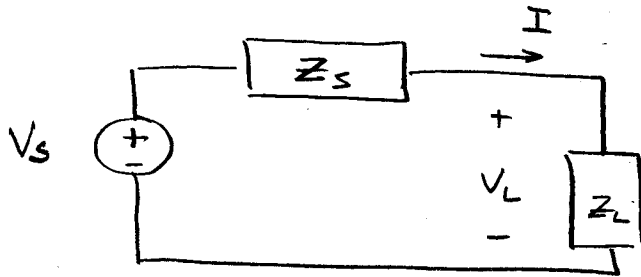- The nature of the load impedance or admittance has a significant effect on the efficiency of power delivery.



Typical loads in power systems have an inductive component, because of transformers and motors. This causes I to lag V_L :

$$Z_L = R_L + jX_L$$

or

$$Y_L = G_L - jB_L$$

$$\begin{aligned} & \begin{array}{c} R_L \\ jX_L \end{array} = |Z_L| \angle \theta_L \\ & \begin{array}{c} G_L \\ -jB_L \end{array} = |Y_L| \angle -\theta_L \end{aligned}$$

$$\begin{array}{c} G_L \\ -jB_L \end{array} = |Y_L| \angle -\theta_L$$

$$I = \frac{V_L}{Z_L} = \frac{|V_L|}{|Z_L|} \angle -\theta_L$$


A lagging power factor, less than 1.

The power to the load is less than $\frac{1}{2} V_m I_m$.

Next, some optimizations.

- Effect of source impedance on power transferred.

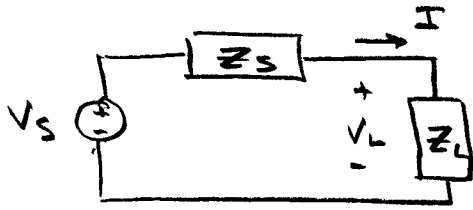- If we could choose source impedance, how could we maximize power transferred to the load, given Z_L ?



$$I = \frac{V_s}{Z_s + Z_L}$$

$$V_L = Z_L I = \frac{Z_L V_s}{Z_s + Z_L}$$

$$P_L = \frac{1}{2} \operatorname{Re}[V_L I^*] = \frac{1}{2} \frac{|V_s|^2 R_L}{|Z_s + Z_L|^2}$$

- Maximize with $Z_s = 0$ (a no-brainer)

- For non-zero Z_s , we can't add negative R_s , but we can change the reactive part of Z_s (i.e. X_s) by putting L or C in series or parallel.


$$P_L = \frac{1}{2} \frac{|V_s|^2 R_L}{|(R_s + R_L) + j(X_s + X_L)|^2}$$

Maximize with $X_s = -X_L$, so $Z_s + Z_L = R_s + R_L$, real

- This is the same condition as for resonance. Most circuits would not actually resonate, since resistance typically dominates reactance — but $X_s = -X_L$ does "tune" the system to ω , in a way.

• Effect of load impedance on power transferred.

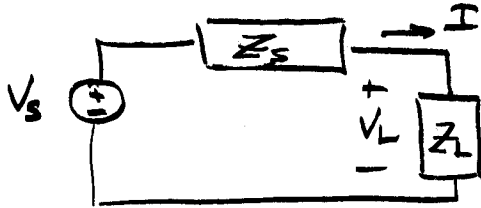- If we can choose load impedance, how can we maximize power transferred to the load, given Z_s ?



$$I = \frac{V_s}{Z_s + Z_L}$$

$$V_L = Z_L I = \frac{Z_L V_s}{Z_s + Z_L}$$

$$P_L = \frac{1}{2} \frac{|V_s|^2 R_L}{|Z_s + Z_L|^2}$$

- First, choose $X_L = -X_s$ to minimize the denominator

$$\text{Then } P_L = \frac{1}{2} \frac{|V_s|^2 R_L}{(R_s + R_L)^2} = \frac{1}{2} |V_L| |I|$$

- A familiar optimization: R_L too large makes I small without continued increase in V_L ; R_L too small makes V_L too small without continued increase in I . Optimum, by $dP_L/dR_L = 0$, is

$$R_L = R_s$$

$$\text{So } Z_L = Z_s^*, \text{ Also } I = \frac{V_s}{Z_s + Z_L} = \frac{V_s}{R_s + R_L} = \frac{V_s}{2R_s}$$

Current I is in phase with source V_s , so

$$\text{source } P_s = \frac{1}{2} \operatorname{Re}[V I^*] = \frac{1}{2} \frac{V_s^2}{2R_s} = \frac{1}{2} \frac{V_{s,rms}^2}{R_s}$$

— But would you want to operate a power system with matched load?


→ source and load each dissipate $\frac{1}{4} \frac{V_{rms}^2}{R_s}$

→ so the same power as the load (an entire suburb?) would be heating up the generator!

→ normally the load resistance is much higher than the source resistance in power systems

→ but in low power systems (sensors, antennas) the matching condition is common.

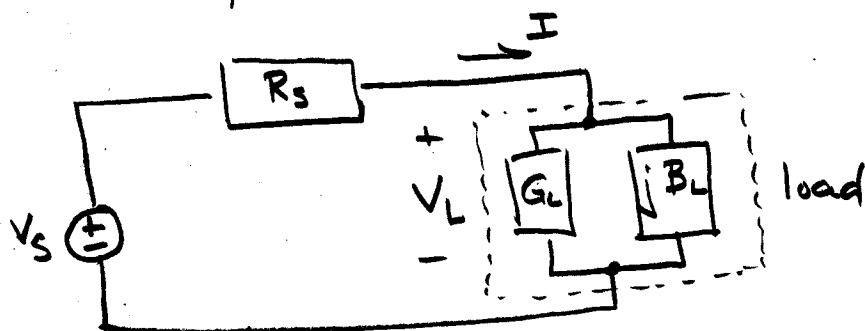• Another optimization: power factor correction.



— The load consumes power in G_L

— The susceptance B_L allows additional current to flow, without increasing load power.

— The extra current wastes more power in R_s — so cancel B_L by shunting $-B_L$ across the load.