

8.4 Three Phase Systems in Δ Format

- We have been connecting phases in Y format


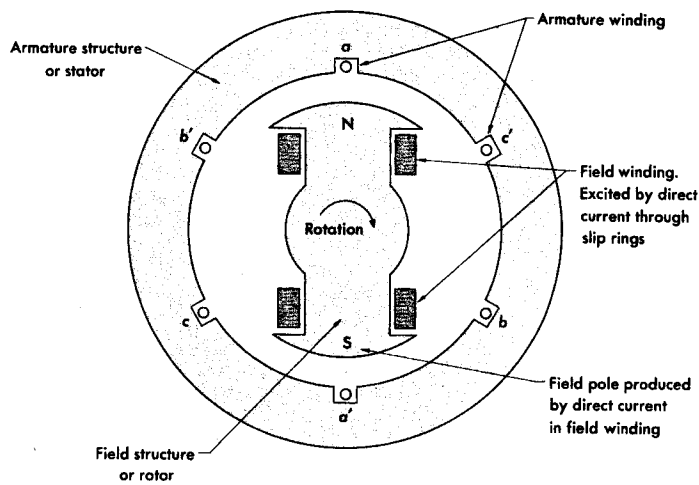
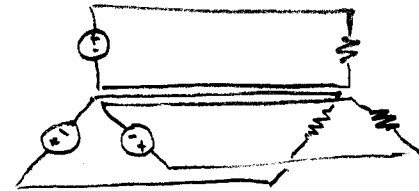


FIGURE 14-10 Elementary three-phase two-pole generator.

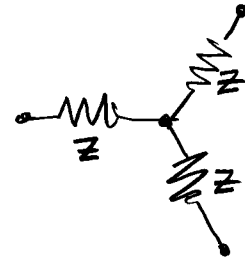

but we can also connect in Δ


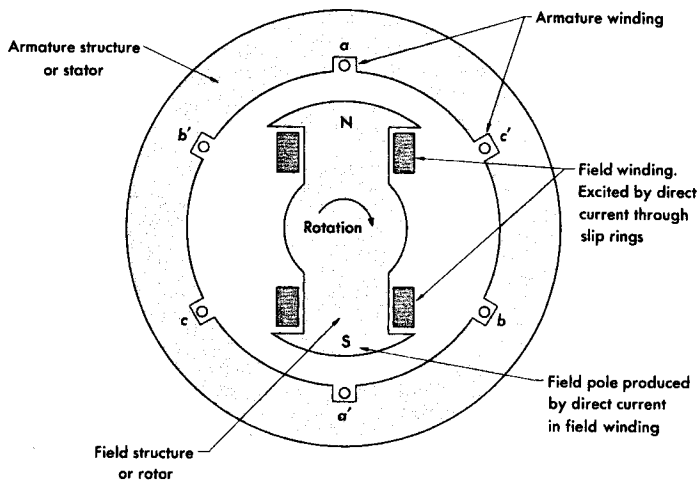
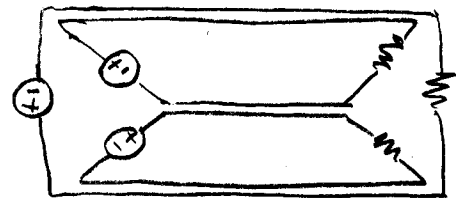



FIGURE 14-10 Elementary three-phase two-pole generator.

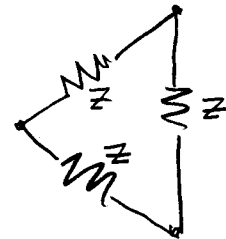


How to analyze them with a common framework?

- With two connection alternatives at the source — and at the load — we must be more careful about defining quantities:

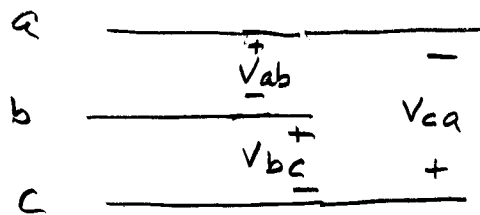
- labels a, b, c identify the lines
- line to line voltages V_{ab} , V_{bc} , V_{ca}



- line to neutral voltages

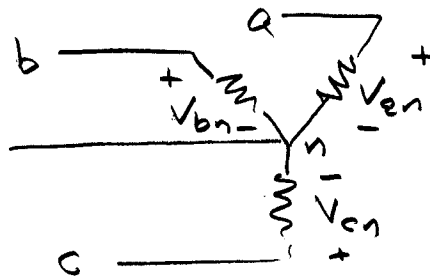

- line currents

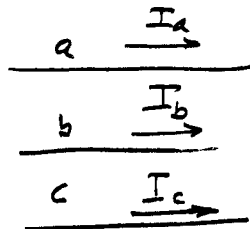


- phase voltages — less well defined — the voltages produced by the generator.

$$V_p \angle 0 \quad V_p \angle -120 \quad V_p \angle -240 \\ = V_p \angle 120$$

— phase currents — currents through each of the generator phases

• Here's Y again

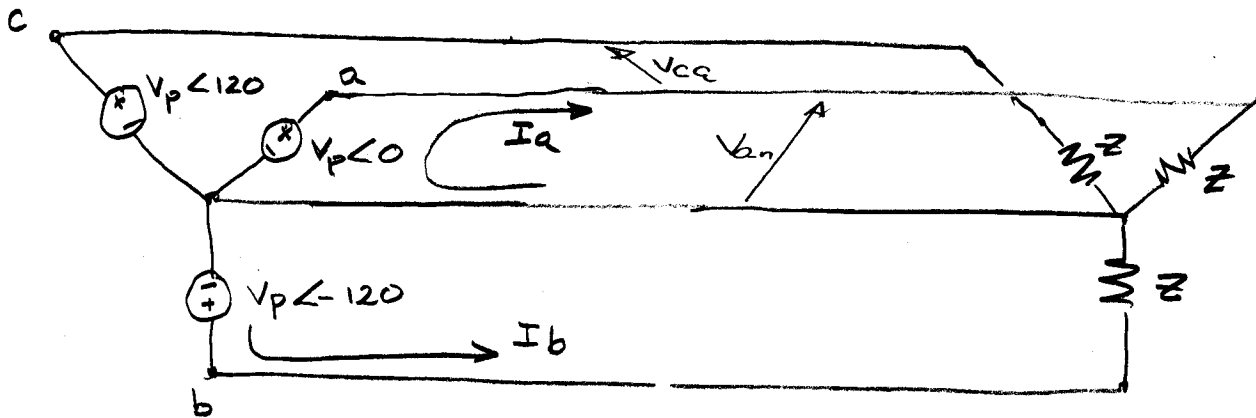

— line to neutral voltages equal phase voltages:

$$V_{an} = V_p \angle 0 \quad V_{bn} = V_p \angle -120 \quad V_{cn} = V_p \angle 120$$

— line currents equal phase currents:

$$I_a = V_{an}/Z \quad I_b = V_{bn}/Z \quad I_c = V_{cn}/Z$$

— power per phase is same, all phases


$$P_{\text{phase}} = \text{Re} [V_{\text{phase}} I_{\text{phase}}^*] \quad (\text{rms quantities})$$

$$= \text{Re} [V_{an} I_a^*] = \text{Re} [V_{an}^2 / Z^*]$$

$$= \frac{V_p^2}{|Z|} \cdot \frac{\cos(\angle Z)}{\text{pf}}$$

$$P_{\text{total}} = \frac{3 V_p^2}{|Z|} \cdot \text{p.f.}$$

— line to line voltages

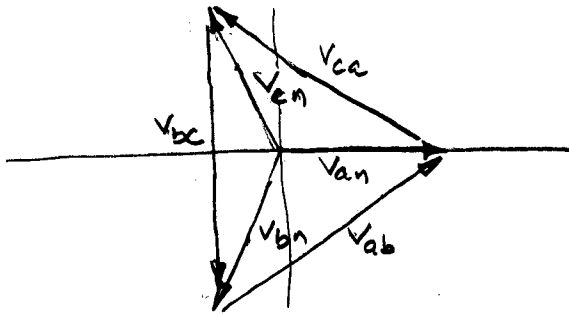


$$V_{ab} = V_{an} - V_{bn} \\ = \sqrt{3} V_p \angle 30^\circ$$

$$V_{bc} = V_{bn} - V_{cn} \\ = \sqrt{3} V_p \angle -90^\circ$$

$$V_{ca} = V_{cn} - V_{an} \\ = \sqrt{3} V_p \angle 150^\circ$$

line-line voltages are
 $\sqrt{3}$ times the line to neutral voltages
 and rotated 30°

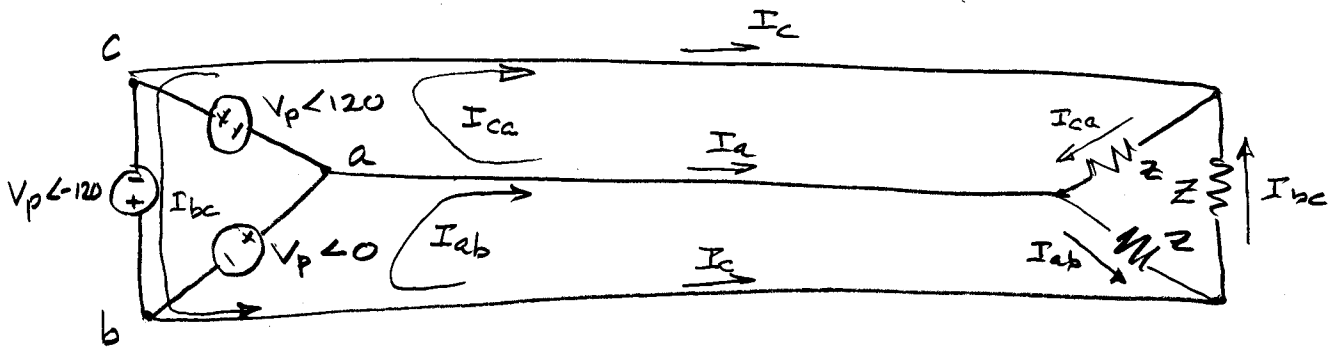- Now for Δ connection. First, we'll establish the basic relations, then find a simplification.



— line to line voltage equal phase voltages


$$V_{ab} = V_p \angle 0 \quad V_{bc} = V_p \angle -120 \quad V_{ca} = V_p \angle 120$$

— phase currents are now defined wrt phase voltages

$$I_{ab} = V_{ab}/Z \quad I_{bc} = V_{bc}/Z \quad I_{ca} = V_{ca}/Z$$

— line currents are sums of phase currents
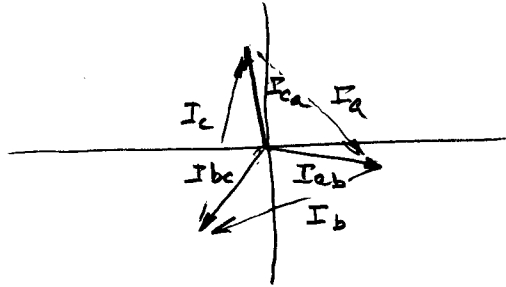
$$I_a = I_{ab} - I_{ca}, \quad I_b = I_{bc} - I_{ab}, \quad I_c = I_{ca} - I_{bc}$$



line currents are $\sqrt{3}$ times phase currents, 30° rotation

— Power per phase

$$P_{ab} = \operatorname{Re}[V_{ab} I_{ab}^*] = \operatorname{Re}\left[V_{ab} \frac{V_{ab}^*}{Z^*}\right]$$

$$= \frac{|V_{ab}|^2}{|Z|} \underbrace{\cos(\angle Z)}_{\text{p.f.}} = \frac{V_p^2}{|Z|} \text{ p.f.}$$

$$P_{\text{tot}} = \frac{3V_p^2}{|Z|} \text{ p.f.}$$

Same as in the Y connection.


• The Δ to Y transformation.

- We can transform a Δ connected load or generator to an equivalent Y connection.


A big help! It lets us analyze single line diagram (easy).

- First, look at load.


Transform this

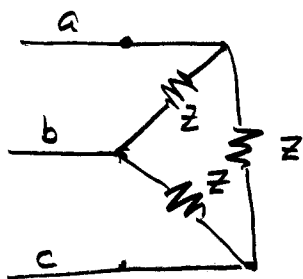

to this

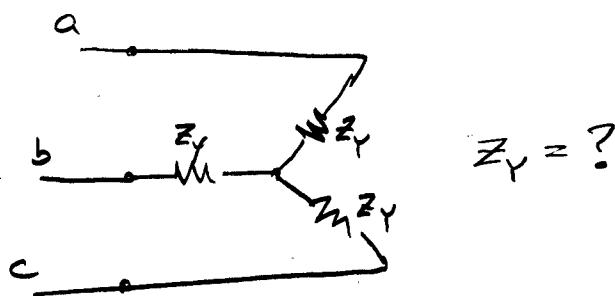

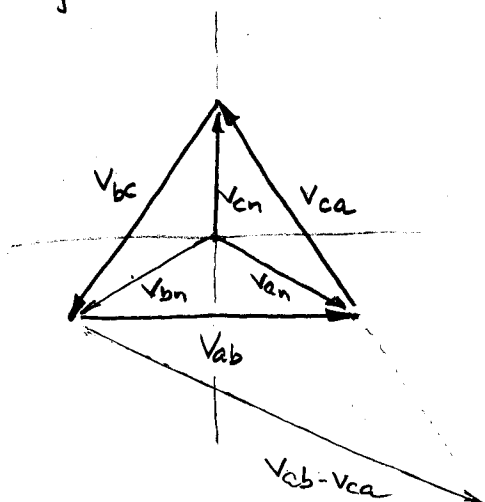Imagine that there is a neutral. Reconstruct V_{an} .




by construction

$$V_{an} = \frac{V_{ab} - V_{ca}}{3}$$


$$\begin{aligned} \text{(note } |V_{ab} - V_{ca}| &= \sqrt{3} |V_{ab}| \\ &= \sqrt{3} \sqrt{3} |V_{an}|) \end{aligned}$$

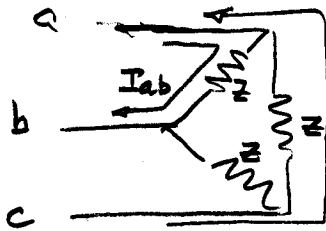Then for the Δ load, the current in line a is



$$\begin{aligned} I_a &= I_{ab} - I_{ca} \\ &= \frac{V_{ab}}{Z} - \frac{V_{ca}}{Z} \\ &= \frac{V_{ab} - V_{ca}}{Z} \end{aligned}$$



and for an equivalent Y load:

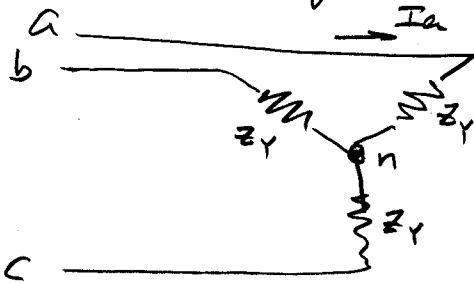


$$\begin{aligned} I_a &= \frac{V_{an}}{Z_Y} \\ &= \frac{V_{ab} - V_{ca}}{3} \cdot \frac{1}{Z_Y} \end{aligned}$$

Consequently $Z_Y = \frac{1}{3} Z$ Easy!

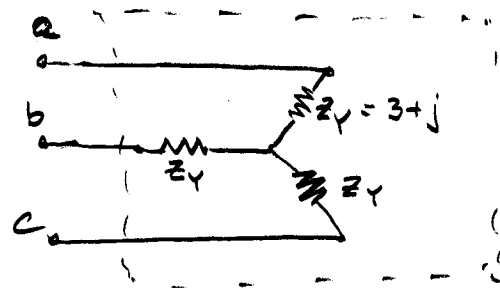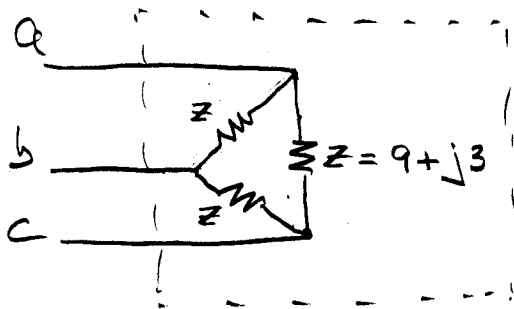example From a terminal perspective, these two loads are equivalent



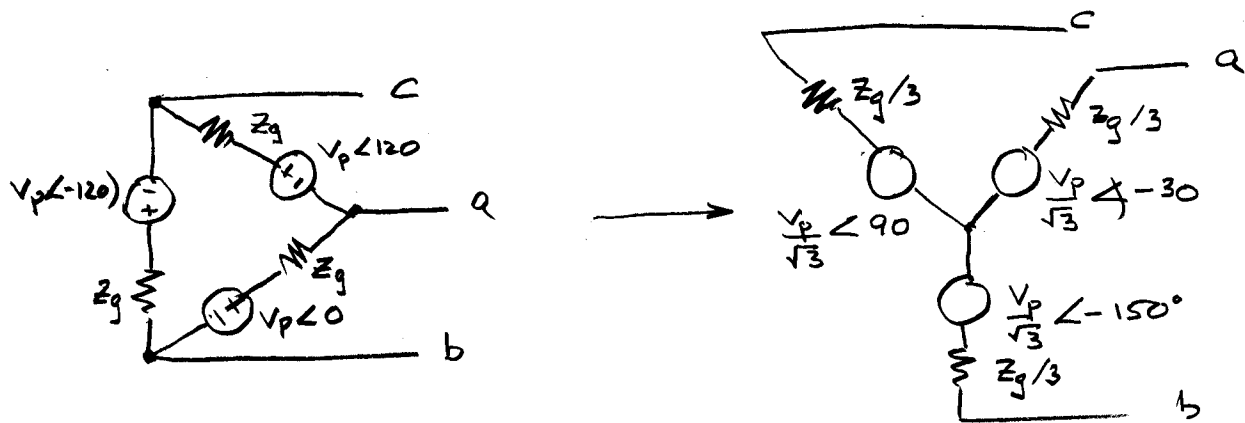
- For a source, including source resistance,



or just
give any
mutual
 120°

- Now we just replace Δ source or load with Y equivalent.

- example. Δ - Δ

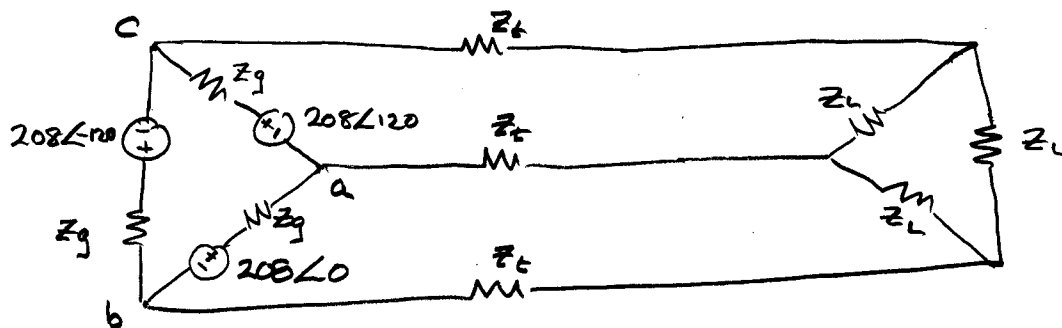

where $Z_g = 0.6 \angle 75^\circ$ $Z_L = 0.3 \angle 45^\circ$ $Z_L = 30 \angle 20^\circ$


- Find I_a , VA, watts, VAR per phase, p.f.
- Value of shunt capacitor to bring pf at load to 1.

— Transform to Y-Y


$$\frac{208}{\sqrt{3}} = 120$$

$$\frac{Z_1}{3} = 0.2 \angle 75^\circ$$

$$\frac{Z_L}{3} = 10 \angle 20^\circ$$

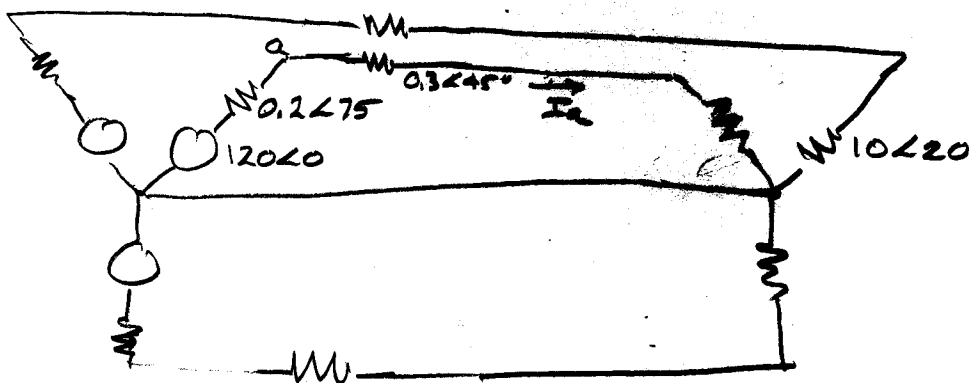

— Single line diagram

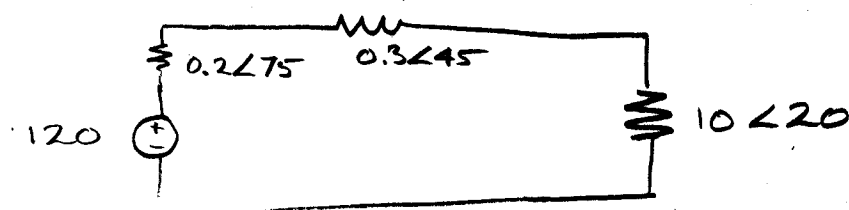

and this is identical to the problem on p. 8.3.10. The only remaining issue is the capacitor. In Y format, we found that C should be $90.2 \mu\text{F}$ (p. 8.3.13). In Δ , the impedance should be 3 times higher, so

$$C = 30.6 \mu\text{F}$$

THE END