
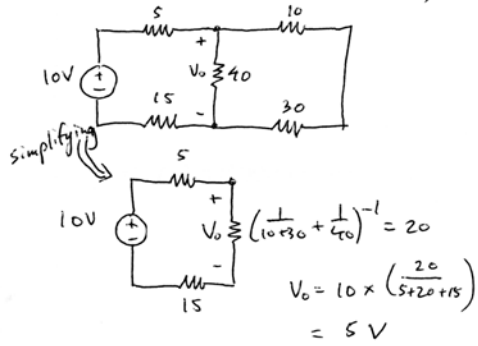



4.89 For the 10V source,

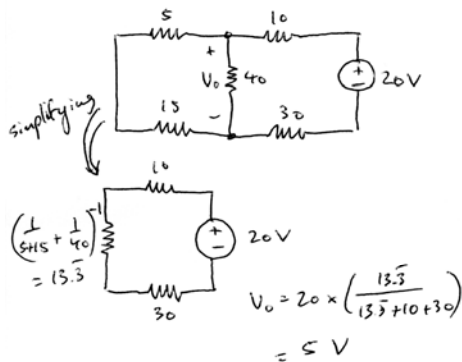

For the 20V source,



For the 6A source,

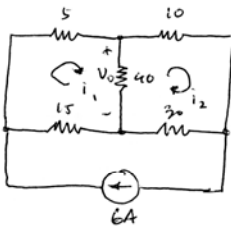

$$-5i_1 - 40(i_1 - i_2) - 15(i_1 - 6) = 0$$

$$-10i_2 - 30(i_2 - 6) - 40(i_2 - i_1) = 0$$

$$-60i_1 + 40i_2 = -90$$

$$40i_1 - 80i_2 = 180$$


$$i_1 = -4.5A \quad i_2 = -4.5A$$

$$V_o = 0 \quad V_o(\text{total}) = 5 + 5 + 0 = 10V$$

5.7 a) non-inverting

$$b) V_o = \frac{40k + 80k}{40k} (3) = 9V$$

5.16 a) summing

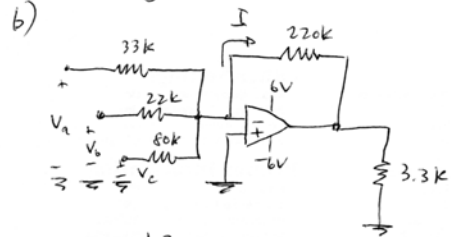

$$I = \frac{1.2}{33000} + \frac{-1.5}{22000} + \frac{4}{80000} = 0.018 \text{ mA}$$

$$V_o = -(0.018 \text{ mA})(220k) = -4V$$

c)  $|V_{\max}| = |V_{\min}| = 6V$

$$I_{\max} = \frac{6}{22000} = 0.027 \text{ mA} = |I_{\min}|$$


$$I_{\max} = \frac{1.2}{33000} + \frac{V_o(\max)}{22000} + \frac{4}{80000}$$

$$V_o(\max) = -1.3V$$

$$I_{\min} = \frac{1.2}{33000} + \frac{V_o(\min)}{22000} + \frac{4}{80000}$$

$$V_o(\min) = -2.5V$$

$$-2.5V < V_o < -1.3V$$

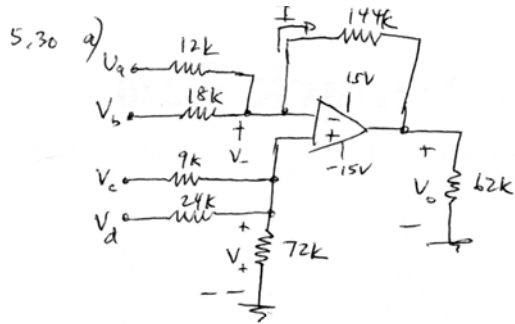

Node-voltage

$$\frac{V_+ - V_c}{9000} + \frac{V_+ - V_d}{24000} + \frac{V_+}{72000} = 0$$

$$8V_+ - 8V_c + 3V_+ - 3V_d + V_+ = 0$$

$$12V_+ = 8V_c + 3V_d$$

$$V_+ = 0.6V$$

$$= V_-$$

$$I = \frac{V_a - V_-}{12000} + \frac{V_b - V_-}{18000}$$

$$= \frac{0.5 - 0.6}{12000} + \frac{0.3 - 0.6}{18000}$$

$$= -0.025 \text{ mA}$$

$$V_o = (0.025 \text{ mA})(144\text{k}) + 0.6$$

$$= 4.2 \text{ V}$$

b) Derive equation for  $V_o$

Superposition  $V_a$  and  $V_b$  on  
 $V_c$  and  $V_d$  off

⇒ Summing amp

$$V_o = -\frac{144000}{12000} V_a - \frac{144000}{18000} V_b$$

$$= -12V_a - 8V_b$$

$V_a$  and  $V_b$  off  
 $V_c$  and  $V_d$  on

from part (a)

$$12V_+ = 8V_c + 3V_d$$

$$V_+ = \frac{2}{3}V_c + \frac{1}{4}V_d$$

$$I = -\frac{V_+}{12000} - \frac{V_+}{18000}$$

$$= -\frac{V_+}{7200}$$

$$V_o = \frac{V_+}{7200} (144000) + V_+$$

$$= 21V_+$$

$$= 14V_c + 5.25V_d$$

$$V_o(\text{total}) = -12V_a - 8V_b + 14V_c + 5.25V_d$$

plug in for  $V_a, V_b, V_d$

$$V_o(\text{total}) = 14V_c - 4.2$$

$$V_{\text{max}} = |V_{\text{min}}| = 15 \text{ V}$$

$$V_c(\text{max}) = 1.371 \text{ V}$$

$$V_c(\text{min}) = -0.771 \text{ V}$$

$$-0.771 \text{ V} \leq V_c \leq 1.371 \text{ V}$$

5.40 a) Using equation 5.55, pg. 200 (7th ed)

$$\frac{V_o}{V_g} = \frac{[(R_f + R_s) + (R_o R_o / A R_i)]}{R_s + \frac{R_o}{A} (1 + K_r) + \frac{R_f R_s + (R_f + R_s)(R_i + R_g)}{A R_i}}$$

$$K_r = \frac{R_s + R_g}{R_i} + \frac{R_f + R_s}{R_L} + \frac{R_f R_s + R_f R_g + R_g R_s}{R_i R_L}$$

$$\begin{aligned} R_s &= 40k & R_i &= 400k & R_L &= 4 \\ R_g &= 100k & R_f &= 80k & R_o &= 5k \\ A &= 20000 \end{aligned}$$

$$K_r = 39500.35$$

$$\frac{V_o}{V_g} = 2.406$$

b)  $V_g = 1V$   $V_o = 2.406V$

equation 5.50, pg. 177

$$\frac{V_n}{R_s} + \frac{V_n - V_g}{R_g + R_i} + \frac{V_n - V_o}{R_f} = 0$$

$$\begin{aligned} \frac{V_n}{40000} + \frac{V_n - 1}{100000 + 400000} + \frac{V_n - 2.406}{80000} &= 0 \\ 100V_n + 8V_n - 8 + 50V_n - 120.281 &= 0 \\ V_n &= 812mV \end{aligned}$$

equation 5.52, pg. 200

$$\frac{V_p - V_g}{R_g} = \frac{V_n - V_g}{R_i + R_g}$$

$$V_p = \left( \frac{V_n - V_g}{R_i + R_g} \right) R_g + V_g$$

$$\begin{aligned} &= \left( \frac{0.812 - 1}{400000 + 100000} \right) 100000 + 1 \\ &= 962mV \end{aligned}$$

c)  $V_p - V_n = 150476mV$

d)  $\frac{V_g - V_p}{100000} = 376191pA$

e) a)  $\frac{V_o}{V_g} = \frac{80k + 40k}{40k} = 3$

b)  $V_p = V_n = 1V = 1000mV$

c)  $V_p - V_n = 0mV$

d) no current drain

Note: If you used a  $4k\Omega$  resistor in place of the  $4\Omega$  resistor you will get:

a) 2.9986

b)  $V_n = 999.567mV$

$V_p = 999.9134mV$

c) 346.4mV

d) 866pA

e) same as for  $4\Omega$  resistor