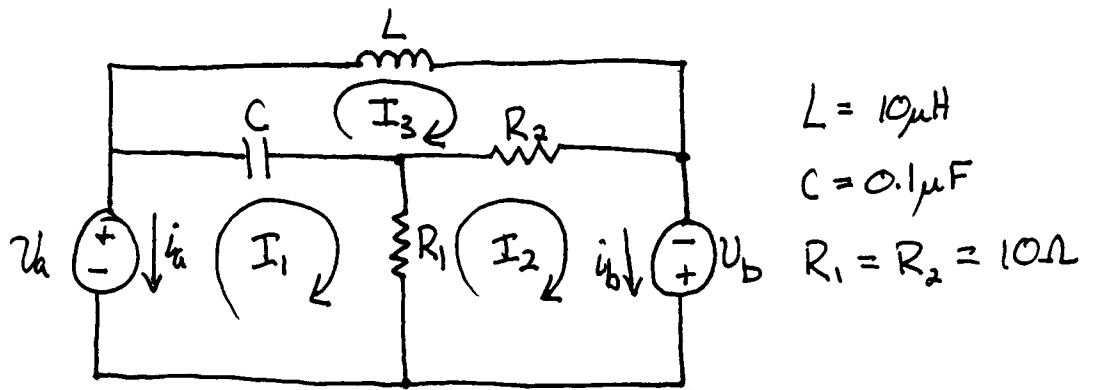


P9.65



$$v_a = 50\sin 10^6 t = 50\cos(10^6 t - 90^\circ)$$

$$V_a = 50\angle -90^\circ = -j50$$

$$v_b = 25\cos(10^6 t + 90^\circ)$$

$$V_b = 25\angle 90^\circ = j25$$

$$Z_L = j\omega L = j10^6(10\mu) = j10\Omega$$

$$Z_C = -j/\omega C = -j/10^6(0.1\mu) = -j10\Omega$$

$$\text{mesh 1: } V_a - Z_C(I_1 - I_3) - R_1(I_1 - I_2) = 0$$

$$-j50 + j10(I_1 - I_3) - 10(I_1 - I_2) = 0$$

$$(-10 + j10)I_1 + 10I_2 - j10I_3 = j50$$

$$\text{mesh 2: } V_b - R_1(I_2 - I_1) - R_2(I_2 - I_3) = 0$$

$$j25 - 10(I_2 - I_1) - 10(I_2 - I_3) = 0$$

$$10I_1 - 20I_2 + 10I_3 = -j25$$

$$\text{mesh 3: } -Z_L I_3 - R_2(I_3 - I_2) - Z_C(I_3 - I_1) = 0$$

$$-j10I_3 - 10(I_3 - I_2) + j10(I_3 - I_1) = 0$$

$$-j10I_1 + 10I_2 - 10I_3 = 0$$

$$\begin{bmatrix} -10+j10 & 10 & -j10 \\ 10 & -20 & 10 \\ -j10 & 10 & -10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} j50 \\ -j25 \\ 0 \end{bmatrix}$$

$$I_1 = .5 - j1.5$$

$$I_2 = -1 + j.5$$

$$I_3 = -2.5$$

$$I_a = -I_1$$

$$= -.5 + j1.5$$

$$= 1.58113883 \angle 108.4349488^\circ$$


$$I_b = -I_2 = 1 - j.5$$

$$= 1.118033989 \angle -26.56505118^\circ$$

$$i_a = 1.58 \cos(10^6 t + 108.4^\circ) \text{ A}$$

$$i_b = 1.12 \cos(10^6 t - 26.6^\circ) \text{ A}$$

P 10.25

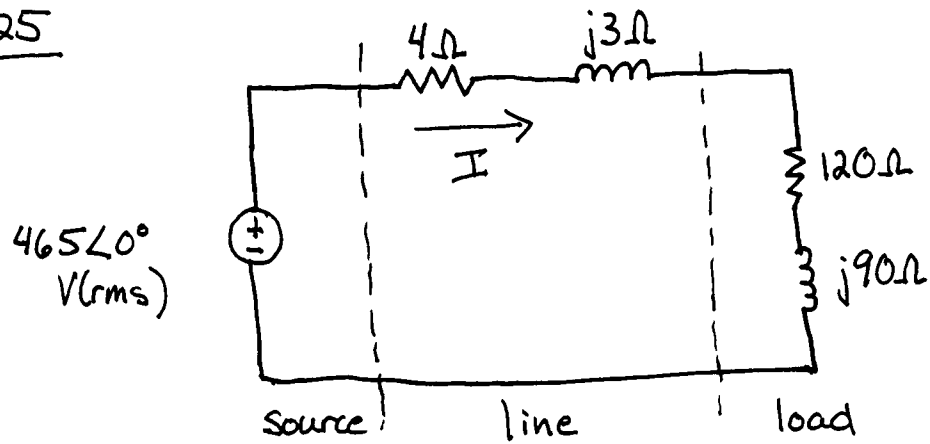


$$\begin{aligned} a) \quad Z &= 4 + j3 + 120 + j90 \\ &= 124 + j93 \\ &= 155\angle 36.86989765^\circ \end{aligned}$$

$$I = \frac{465\angle 0^\circ}{155\angle 36.9^\circ} = 3\angle -36.9^\circ = 2.4 - j1.8$$

$$\begin{aligned} V_{\text{line}} &= Z_{\text{line}} I \\ &= (4 + j3)(2.4 - j1.8) \end{aligned}$$

$$\begin{aligned} S_{\text{line}} &= V_{\text{line}} I^* \\ &= (4 + j3)(2.4 - j1.8)(2.4 + j1.8) \\ &= (4 + j3)(5.76 + 3.24) \\ &= (4 + j3)9 \\ &= 36 + j27 \end{aligned}$$
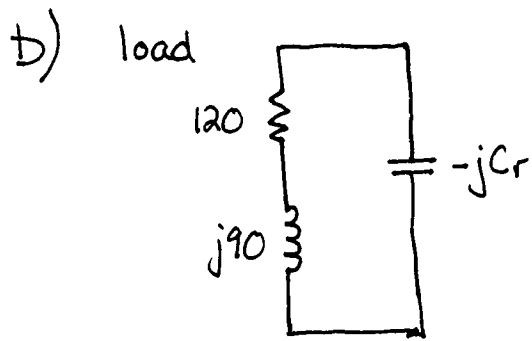
$$\Rightarrow P_{\text{avg}} = 36\text{W}$$



$$Z = \left( \frac{1}{120 + j90} - \frac{1}{jCr} \right)^{-1}$$

$$S_{\text{load}} = P + jQ \leftarrow \text{want } Q = 0$$

-without the added capacitor

$$\begin{aligned} V_{\text{load}} &= I Z_{\text{load}} \\ &= (2.4 - j1.8)(120 + j90) \\ &= 450V \end{aligned}$$

$$\begin{aligned} S_{\text{load}} &= V_{\text{load}} I^* \\ &= 450(2.4 + j1.8) \\ &= 1080 + j810 \end{aligned}$$

$$X_c = \frac{|V_{\text{eff}}|^2}{-Q} = \frac{450^2}{-810} = -250 \Rightarrow C_r = 250 \Omega$$

$$c) Z_{\text{load}} = \left( \frac{1}{120 + j90} - \frac{1}{j250} \right)^{-1} = 187.5 \Omega$$


$$\begin{aligned} d) Z &= 187.5 + 4 + j3 \\ &= 191.5 + j3 \\ &= 191.5234973 \angle 0.897510597^\circ \end{aligned}$$

$$I = \frac{465 \angle 0^\circ}{191.52 \angle 0.898^\circ} = 2.427900527 \angle -0.898^\circ$$

$$\begin{aligned} P_{\text{avg}} &= (2.427900527)^2 (4) \\ &= 23.57880388 \text{ W} \end{aligned}$$

$$e) \% \text{ power} = \frac{23.58}{36} = 65.4966775\%$$

P14.15

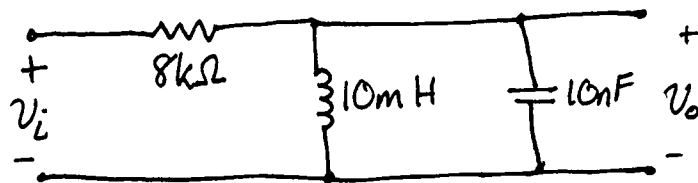

following example 14.6

$$a) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10\text{m}(10\text{n})}} = 1 \times 10^5 \text{ rad/s} = 100 \text{ krad/s}$$

$$b) f_0 = \frac{\omega_0}{2\pi} = \frac{1 \times 10^5}{2\pi} = 1.591549431 \times 10^4 \text{ Hz} = 15.92 \text{ kHz}$$

$$c) Q = \sqrt{\frac{R^2 C}{L}} = \sqrt{\frac{(8\text{k})^2 (10\text{n})}{10\text{m}}} = 8$$

$$\begin{aligned} d) \omega_{c1} &= -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \\ &= -\frac{1}{2(8\text{k})(10\text{n})} + \sqrt{\left(\frac{1}{2(8\text{k})(10\text{n})}\right)^2 + \frac{1}{10\text{m}(10\text{n})}} \\ &= -6.25 \times 10^3 + 100 \times 10^3 \\ &= 9.375 \times 10^4 \text{ rad/s} = 93.75 \text{ krad/s} \end{aligned}$$

$$e) f_{c1} = \frac{\omega_{c1}}{2\pi} = \frac{9.375 \times 10^4}{2\pi} = 1.492077591 \times 10^4 \text{ Hz} = 14.92 \text{ kHz}$$

$$\begin{aligned} f) \omega_{c2} &= \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \\ &= 6.25 \times 10^3 + 100 \times 10^3 \\ &= 1.0625 \times 10^5 \text{ rad/s} = 106.25 \text{ krad/s} \end{aligned}$$

$$g) f_{c2} = \frac{\omega_{c2}}{2\pi} = \frac{1.0625 \times 10^5}{2\pi} = 1.69102127 \times 10^4 \text{ Hz} = 16.91 \text{ kHz}$$

$$\begin{aligned} h) \beta &= \frac{1}{RC} = \frac{1}{8\text{k}(10\text{n})} = 1.25 \times 10^4 \text{ rad/s} = 12.5 \text{ krad/s} \\ &= 1.99 \text{ kHz} \end{aligned}$$