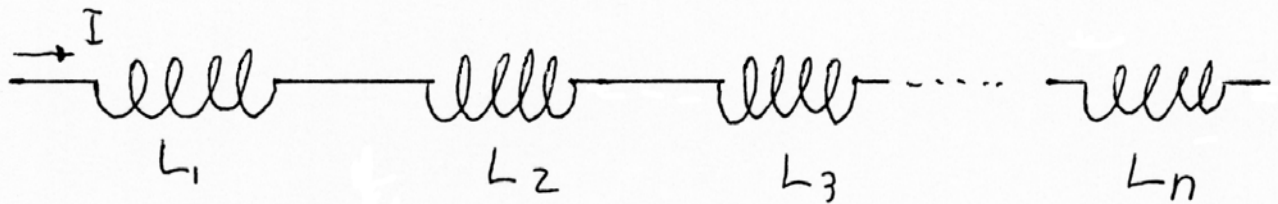


Inductors in Series

- Inductors in series act just like one large inductor
- Inductors in series add to the total inductance
- "Inductors in series act like resistors in Series"


$$L_{total} = \sum_{j=1}^n L_j$$

- Warning: this assumes the magnetic fields do not interact
- Thus no mutual inductance



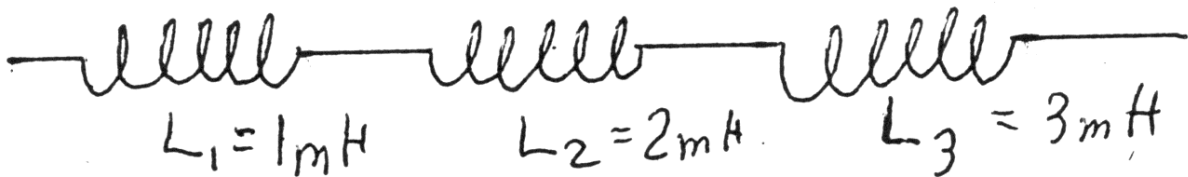- Example: 1, 2, and 3 mH inductors in series. What is L_{total}
- Thus total is

$$L_{total} = \sum_{j=1}^n L_j = L_1 + L_2 + L_3 = 10^{-3} + 2 \times 10^{-3} + 3 \times 10^{-3} = 6 \text{ mH}$$



Inductors in Parallel

- "Inductors in Parallel act like resistors in Parallel"
- Inverse of the total equals the sum of the inverses

$$\frac{1}{L_{total}} = \sum_{j=1}^n \frac{1}{L_j}$$


- Again important the magnetic fields do not interact
- Why do Inductors act different than C's?
- Consider parallel L's
- Voltage across each inductor is the same.
- Recall the Current is given by:

$$I = \frac{1}{L} \int V(t) dt$$

- Thus the total current through the inductors is:

$$I_{total} = \sum_{j=1}^n I_j = \sum_{j=1}^n \left[\frac{1}{L_j} \int V(t) dt \right] = \left[\sum_{j=1}^n \frac{1}{L_j} \right] \int V(t) dt$$

- Where t is the time of measurement

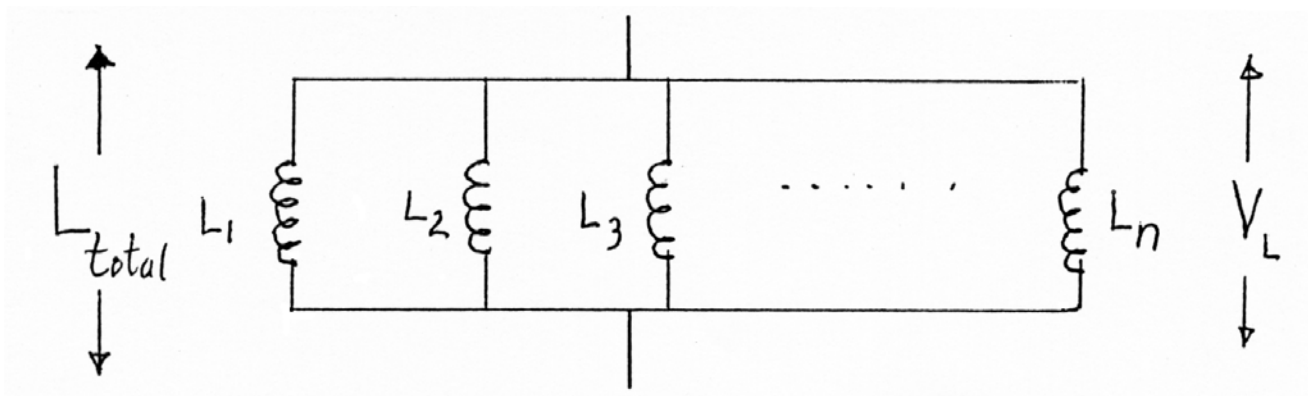


Example Parallel Inductors

Example: two inductors in parallel: $L_1 = 1 \text{ mH}$, $L_2 = 2 \text{ mH}$

Thus total is

$$\frac{1}{L_{total}} = \frac{1}{L_1} + \frac{1}{L_2} = \frac{1}{10^{-3}} + \frac{1}{2 \times 10^{-3}} = \frac{3}{2 \times 10^{-3}} \text{ H}$$
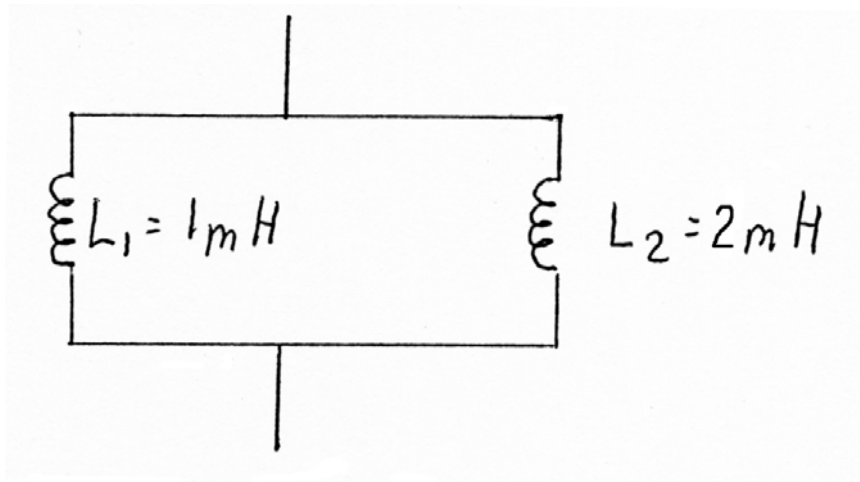
$$L_{total} = \frac{2 \times 10^{-3}}{3} = 0.667 \text{ mH}$$




Practical Inductors

- Real inductors are often air coils: just coiled wire
- Advantage: high speed, very easy to make, calculate and tune
- Disadvantage: lower inductance, high resistance (from wire)
- Needs lots of turns of wire
- Typical values μH to mH



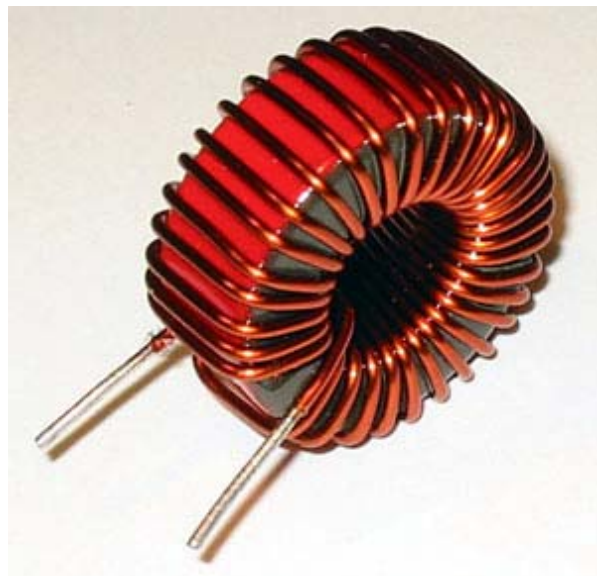- Often bend coil into a torus (donut core with wire wound around)
- Reason magnetic field confined to the torus core
- Thus ideally no mutual inductance
- Also field is stronger in core, and thus L larger & smaller size



Ferrite Core Inductors

- Ferrite (iron) core inductors are most common
- Advantages:
 - Much smaller for given inductance
 - Can get very high inductance (henries!) with big ones
 - Magnetic field mostly stays within the Ferrite area
- Disadvantage:
 - Much harder to calculate (depends on iron type)
 - Hence must be measured
 - Also iron gets hot (heated by induction)



Natural Response of Resistor Capacitor (EC 7))

- **Natural Response:** behaviour of a circuit to a sudden change
- Consider a Capacitor in series with a resistor R
- At time $t=0$ a switch connects this to a voltage V_0
- Recall the capacitor current behaviour


$$i(t) = C \frac{dv}{dt}$$

- Or rewriting this

$$v(t) = \frac{1}{C} \int_0^t i(t) dt$$

- Then writing the KVL for the circuit
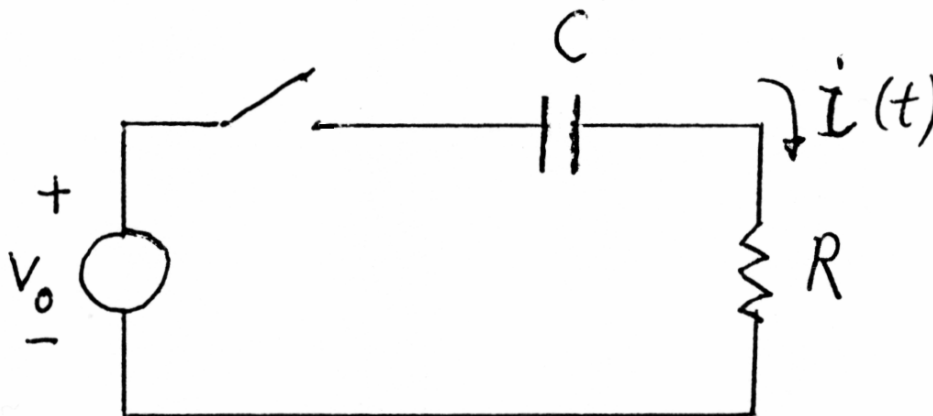
$$V_0 - \frac{1}{C} \int_0^t i(t) dt - i(t)R = 0$$




Natural Resistor Capacitor Response: Differential Equations

- Differentiating with respect to time

$$R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$$

- This is the "Differential Equation" form of the KVL equation
- Using the integration solution method for DE's
- To solve get into integral form
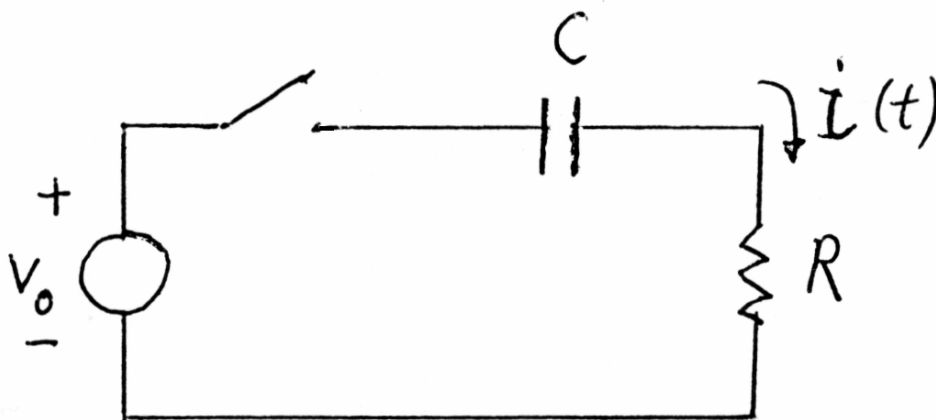
$$\int \frac{1}{i(t)} di = -\frac{1}{RC} \int dt$$



Natural Resistor Capacitor Response: Solutions

$$\int \frac{1}{i(t)} di = -\frac{1}{RC} \int dt$$

- Integrating both sides to solve

$$\ln(i(t)) = -\frac{t}{RC} + A$$


- Where A is a constant of integration
- Taking the exponential of each side
- Then setting at time $t=0$ call the current I_0 then

$$i(t) = I_0 \exp\left(-\frac{t}{RC}\right)$$

- The time constant is

$$\tau = RC$$

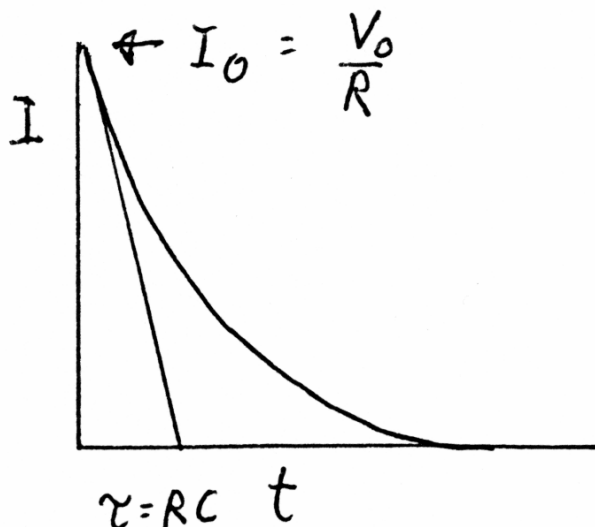- This is an exponential decay of current
- Thus at as time goes to infinity Capacitors act as opens
- Current goes to zero



Natural Resistor Capacitor Response: Initial Conditions

- With the voltage suddenly applied
- Eventually C becomes charge to voltage source level
- At time zero Capacitors act as short circuits
- Thus for $t=0$ can ignore capacitor, so


$$I_0 = i(t=0) = \frac{V_0}{R}$$

- Thus the current equation is

$$i(t) = \frac{V_0}{R} \exp\left(-\frac{t}{RC}\right)$$

- Initial slope of line of line is
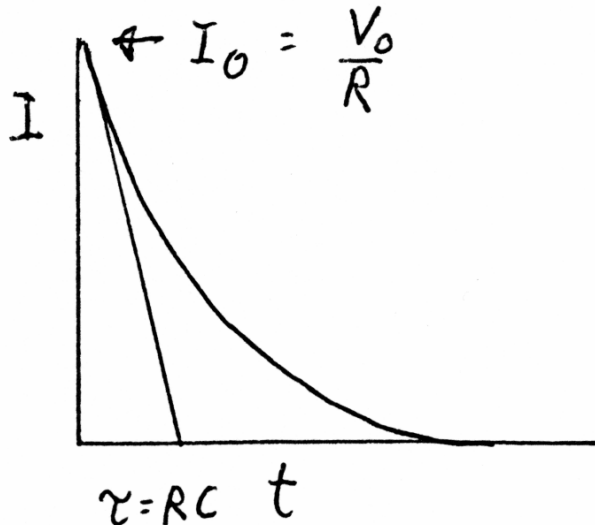
$$\frac{di(t=0)}{dt} = -\frac{I_0}{\tau} = -\frac{V_0}{R^2 C}$$



Natural Resistor Capacitor Response: Voltage

- Final voltage on Capacitor matches the V source

$$V_C(t \rightarrow \infty) = V_0$$

- Voltage across the capacitor from the KVL

$$v_C(t) = V_0 - i(t)R = V_0 - \frac{V_0}{R} \exp\left(-\frac{t}{RC}\right)R = V_0 \left(1 - \exp\left(-\frac{t}{RC}\right)\right)$$

- Thus voltage rises to equal the voltage source exponentially
- Same equations for C charge to initial voltage plus R with no V
- Only difference is final voltage on Capacitor now zero
- Both called "RC circuits"

