

## General Exponential

- Many circuits respond to step change with an exponential.
- General form of an exponential decay

$$a(t) = A_0 \exp\left(-\frac{t}{\tau}\right)$$

Where

$a(t)$  = signal at time  $t$

$A_0$  = max signal ( $t=0$  value)

exp = natural exponential,  $e = 2.718$

$t$  = time in seconds

$\tau$  = "time constant" in seconds

- Time constant: time to decay to  $1/e = 0.368$  of max
- System response measured in terms of time constant
- $\tau$  = projection of initial slope on  $t$  axis

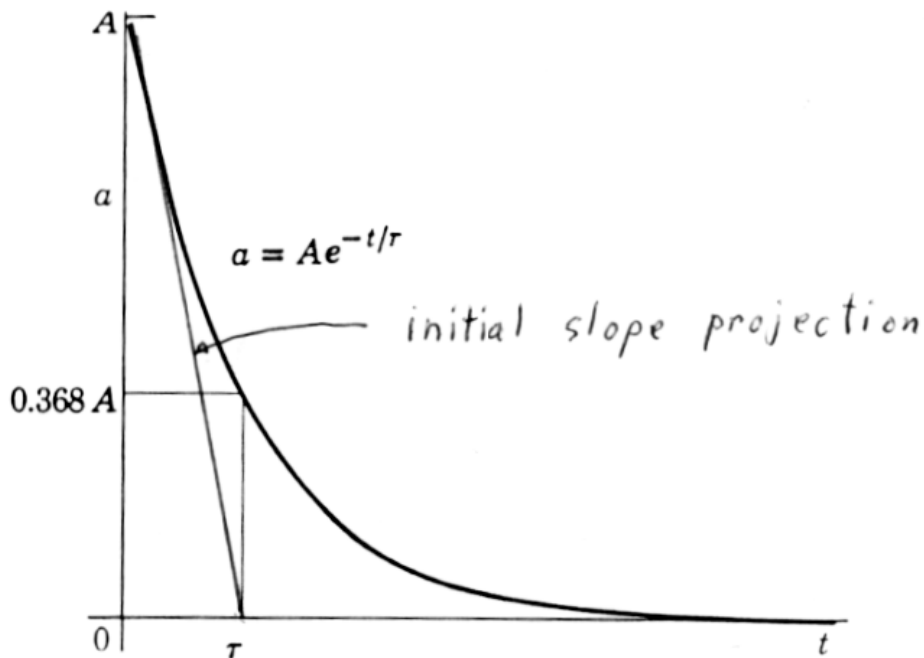



Figure 3.3 The decaying exponential.

## Exponential Increase

- Cannot have a true exponential increase: goes forever
- Response to a sudden increase often an "exponential change"

$$a(t) = A_0 \left[ 1 - \exp\left(-\frac{t}{\tau}\right) \right]$$

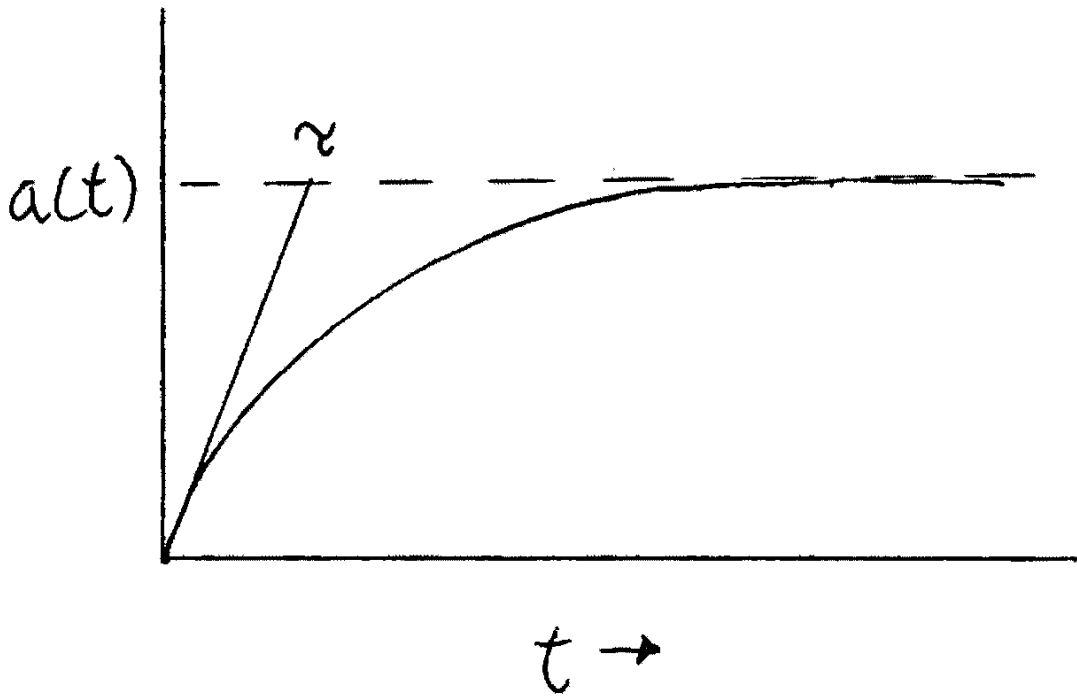- This is an exponential "decay" to new steady state value
- Very common behaviour in electronic circuits



## Exponential Importance

- Exponentials importance: derivative & integral are exponentials

$$a(t) = A_0 \exp\left(-\frac{t}{\tau}\right)$$

$$\frac{da(t)}{dt} = -\frac{A_0}{\tau} \exp\left(-\frac{t}{\tau}\right)$$

$$\int a(t) dt = -\tau A_0 \exp\left(-\frac{t}{\tau}\right)$$

- For circuits with inductors and capacitors:  
voltage/current related by derivative/integrals
- Thus exponential voltages will generate exponential currents

## Example Exponential Voltages and Currents

- Eg. RC circuit with capacitor initially charged
- Charged capacitor will decay exp. through the resistor
- $C = 2 \mu\text{F}$  initially charged to  $V_c(t=0) = 10 \text{ V}$ ,
- Current discharges through  $R = 1000 \Omega$  which removes energy
- Thus max current at  $t=0$  is

$$I_0 = i(t=0) = \frac{V_0}{R} = \frac{10}{1000} = 0.01 \text{ A} = 10 \text{ mA}$$

- Time constant is




$$\tau = RC = 1000(2 \times 10^{-6}) = 0.002 \text{ sec} = 2 \text{ ms}$$

- Thus the current  $i(t)$  at time  $t$  is

$$i(t) = \frac{V_0}{R} \exp\left(-\frac{t}{RC}\right) = 0.01 \exp\left(-\frac{t}{0.002}\right) \text{ Amp}$$

- By KVL the Voltage across  $C = V$  across  $R$

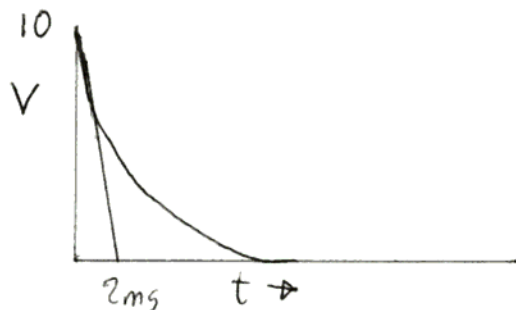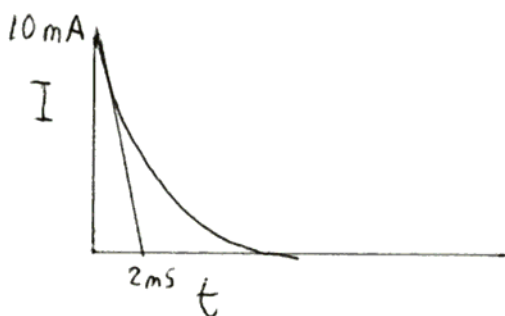
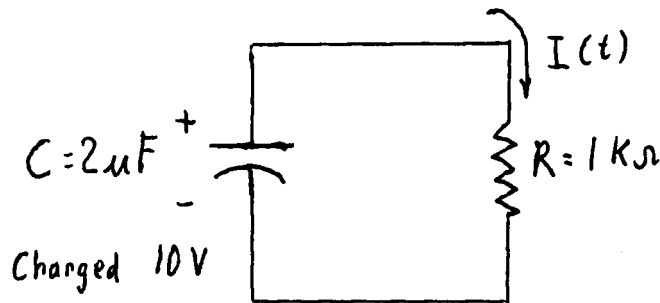
$$i(t)R = 0.01(1000) \exp\left(-\frac{t}{0.002}\right) = 10 \exp\left(-\frac{t}{0.002}\right) \text{ V}$$




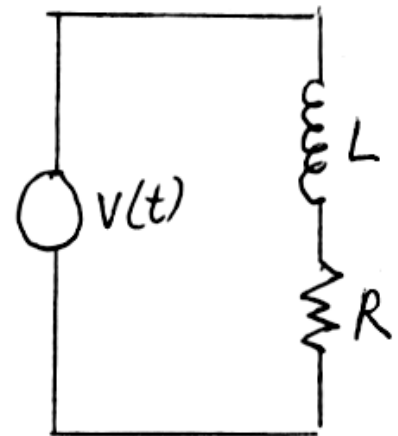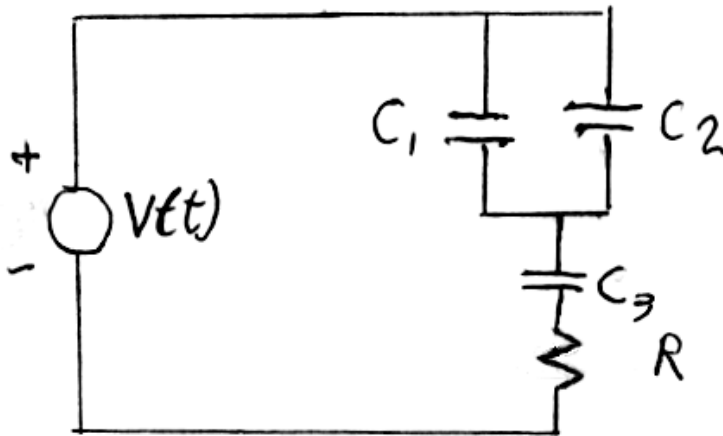
## Natural Response and First Order Circuits

- Looking at response to a sudden change.
- The applied  $V$  or  $I$  is called the Forcing Function
- Basic Type: first order circuits
- Has only one energy storage device:  $C$  or  $L$
- The  $RC$  circuit called a First order circuit
- Can have capacitors or inductors if combinable to a single
- Use simple  $C$  or  $L$  parallel/series combinations
- However for 1<sup>st</sup> order cannot mix  $C$  and  $L$
- 1<sup>st</sup> order: only 1<sup>st</sup> derivative in equations
- Thus creates first order differential equations
- 1<sup>st</sup> order general behaviour exponential in form for sudden change




## Initial and Final Response to a "Step Function"

- Often want to know circuit response to a sudden V or I change
- Called a **Step Function**:
- Sudden instantaneous change in voltage or current
- Has two regions:

$$V(t) = 0 \quad t < 0$$

$$V(t) = V_0 \quad t > 0$$

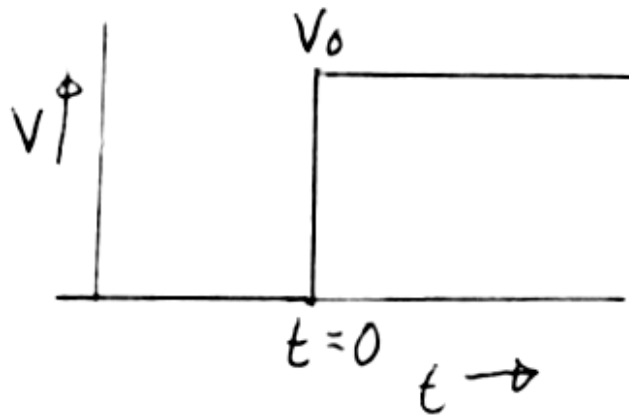- Often call time just prior to step  $0^-$
- Time just after step  $0^+$
- Step function in current similar
- In practice an ideal step is impossible to create:
- Real systems do not have an instantaneous change




## C with Initial Energy Storage

- Capacitors or Inductors may start with stored energy
- Capacitors with a stored charge has an initial voltage across it from

$$V = \frac{Q}{C}$$

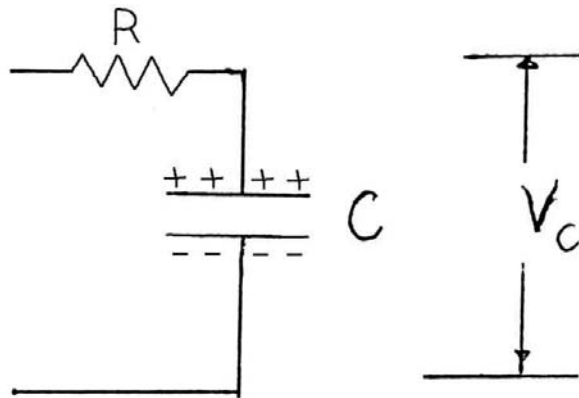- Charged capacitors can exist in an open circuit





## L with Initial Energy Storage

- Inductors can only have stored energy with flowing current
  - Thus a voltage/current source present before any change in circuit
  - Then use a switch to remove (short out) initial source
  - But still keep L as part of a circuit
- 
- Sometimes have both applied step function & initial stored energy
  - Then voltage on C or current in L when new source applied

