

## How Impedances Combine


- Impedances Combine just like resistors
- However, must use complex numbers and math
- Impedances in series add to the total impedance

$$Z_{total} = \sum_{j=1}^n Z_j$$

- All these additions are using complex numbers
- Thus in the RLC example

$$Z_{total} = Z_R + Z_L + Z_C$$
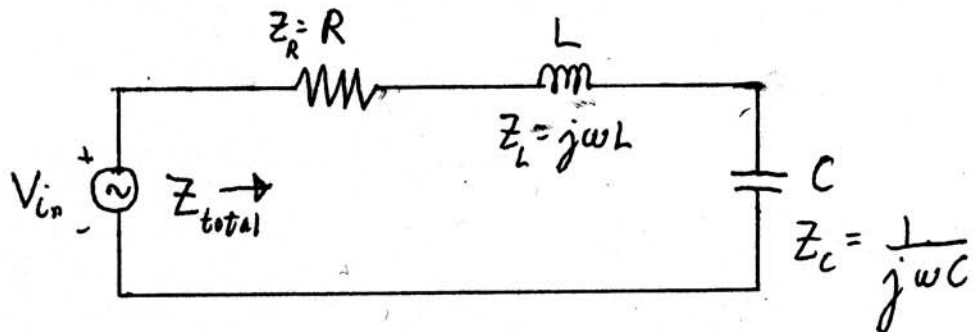
$$Z_{RLC} = R + j \left[ \omega L - \frac{1}{\omega C} \right]$$



## Impedances in Parallel

- Impedances in parallel:
- inverse of the total equals the sum of the inverses

$$\frac{1}{Z_{total}} = \sum_{j=0}^n \frac{1}{Z_j}$$

- note how this generates the laws for Capacitors
- thus for capacitors in parallel:

$$\left[ \frac{1}{j\omega C_{total}} \right]^{-1} = \sum_{k=1}^n \left[ \frac{1}{j\omega C_k} \right]^{-1}$$

Thus

$$C_{total} = \sum_{j=1}^n C_j$$

- Unites are mhos or Siemens (S)
- The complex conductance has real and imaginary parts

$$Y = \frac{1}{Z} = G + jB = Y/\theta_y$$

Where

G = conductance

B = susceptance

- Thus For circuit in parallel just add admittances

$$Y_{parallel} = \sum_{j=1}^n Y_j$$


## Parallel RLC circuit

- Consider a R, L and C in parallel
- Then their admittance is:

$$Y = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C = \frac{1}{R} + j\left[\omega C - \frac{1}{\omega L}\right]$$

- If driven by an AC current source
- Then acts as a filter of the voltage

$$I = VY$$

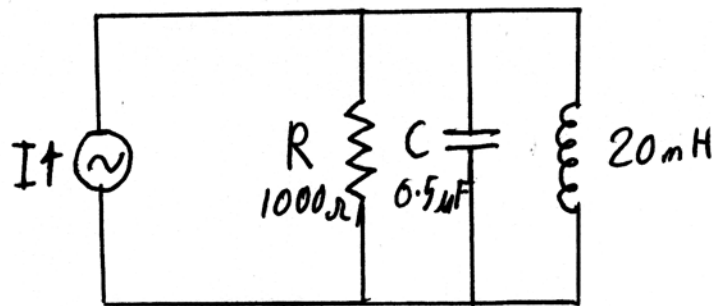

## Example Parallel RLC circuit

- eg.  $R=1000$  ohms,  $L=20$  mH and  $C=0.5$   $\mu$ F in parallel
- Then the admittance is:

$$Y = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C = \frac{1}{R} + j\left[\omega C - \frac{1}{\omega L}\right]$$

- The frequency of natural response is

$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.02 \times 5 \times 10^{-7}}} = 10^4 \text{ rad/s}$$

- At the natural frequency admittance is minimum

## **KVL, KCL and Complex impedances**

- Kirchoff's laws, KVL and KCL work in complex  $Z$
- Voltage dividers, current dividers, Thevenin/Norton  
Mesh/Node analysis all work as with resistances
- just use the complex impedances  $Z$  did resistances
- However all solutions must use complex math
- Apply a sin wave input use phasor form
- will get a phase shift in the  $V$  and  $I$


## RL and RC reactance and phase angle

- Adding a resistor to L or C changes the impedance
- Eg. For an RL system

$$Z = R + j\omega L$$

$$\theta = \arctan\left[\frac{\omega L}{R}\right]$$

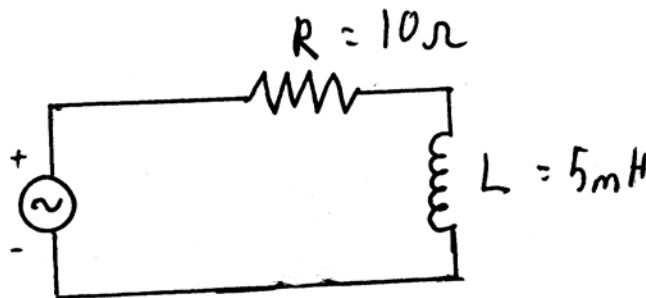- the phase angle is thus decreased
- the larger the resistance, the smaller the phase angle
- the larger the frequency, the closer to  $90^\circ$



## Example RL reactance and phase angle

- eg. For  $R = 10$  ohms,  $L = 5$  mH
- applied voltage 10 V at 60 Hz and 1000 Hz

$$\vec{Z}_{60} = 10 + j377 \times 0.005 = 10 + j1.89$$

$$Z_{60} = (10^2 + 1.89^2)^{1/2} = 10.18 \text{ ohms}$$

$$\theta = \arctan \left[ \frac{1.9}{10} \right] = 10.6^\circ$$

$$\vec{Z}_{60} = 10.18 \angle 10.7^\circ$$

- Thus the is mostly real


- For the circuit

$$I = \frac{V}{Z_{60}} = \frac{10}{10.18 \angle 10.7^\circ} = 0.937 \angle -10.7^\circ \text{ Amp}$$

$$V_R = IZ_R = 0.937 \angle -10.7^\circ \times 10 = 9.37 \angle -10.7^\circ \text{ V}$$

$$V_L = IZ_L = 0.937 \angle -10.7^\circ \times 1.89 \angle 90^\circ = 1.77 \angle 79.3^\circ \text{ V}$$

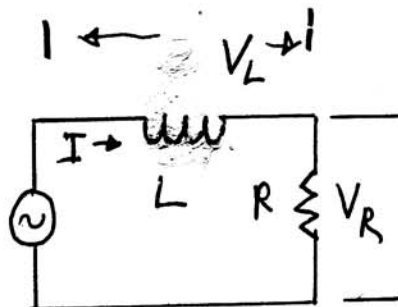- Note: This is a complex voltage divider
- But output voltages have different phase relationship



## Example RL reactance and phase angle

- At 1000 Hz then

$$\vec{Z}_{1000} = 10 + j6283 \times 0.005 = 10 + j31.4 \text{ ohms}$$

$$\vec{Z}_{1000} = 33.0 \angle 72.3^\circ$$

- For the circuit

$$I = \frac{V}{Z_{1000}} = \frac{10}{33.0 \angle 72.3^\circ} = 0.303 \angle -72.3^\circ \text{ Amp}$$

$$V_R = IZ_R = 0.303 \angle -72.3^\circ \times 10 = 3.03 \angle -72.3^\circ \text{ V}$$

$$V_L = IZ_L = 0.303 \angle -72.3^\circ \times 31.4 \angle 90^\circ = 9.52 \angle 17.7^\circ \text{ V}$$


- Thus acting closer to an inductive reactance


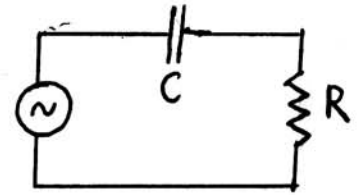
## RC reactance and phase angle

- For an RC system

$$Z = R + \frac{1}{j\omega C} = R - j\frac{1}{\omega C}$$



- the phase angle is thus reduced
- the larger the resistance, the smaller the phase angle
- the smaller the frequency, the closer to  $-90^\circ$
- eg.  $R=10$  ohms,  $C=2 \mu\text{F}$ , at 60 Hz, 1 KHz, 10 KHz

$$\vec{Z}_{60} = 10 - j\frac{1}{377 \times 2 \times 10^{-6}} = 10 - j1326$$

$$\vec{Z}_{60} = 1329 \angle -89.6^\circ$$

- Thus the is mostly capacitive reactive

- At 1000 Hz then

$$\vec{Z}_{1000} = 10 - j\frac{1}{6283 \times 2 \times 10^{-6}} = 10 + j79.6 \text{ ohms}$$

$$\vec{Z}_{1000} = 80.2 \angle -82.8^\circ$$

- At 10 KHz then


$$\vec{Z}_{10K} = 10 - j\frac{1}{62830 \times 2 \times 10^{-6}} = 10 + j7.95 \text{ ohms}$$

$$\vec{Z}_{10K} = 12.8 \angle -38.5^\circ$$

- Thus acting closer to an real resistance
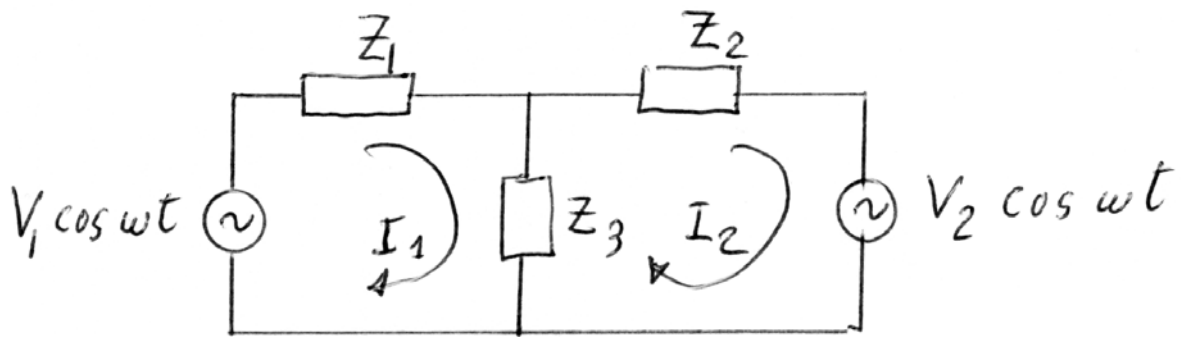
## Impedance and Circuit Analysis

- Can use the  $Z$ 's to analysis frequency domain response
- $Z$ 's work just as resistors before
- All current/voltage dividers, mesh and node analysis
- Only requires that you use complex numbers



## Impedance Divider Example

- Example Consider an impedance divider
- For input waves can find the phase delay
- e.g. RL circuit: what is voltage across capacitor

$$V_L = \frac{Z_L}{Z_{RL}} V_{in}$$


$$Z_L = j\omega L = \omega L \angle 90^\circ$$

$$Z_{RL} = R + j\omega L$$

- The voltage divider equation is

$$V_L = \frac{Z_L}{Z_{RL}} V_{in} = \frac{j\omega L}{R + j\omega L} V_{in}$$

- Note the sensitivity to frequency

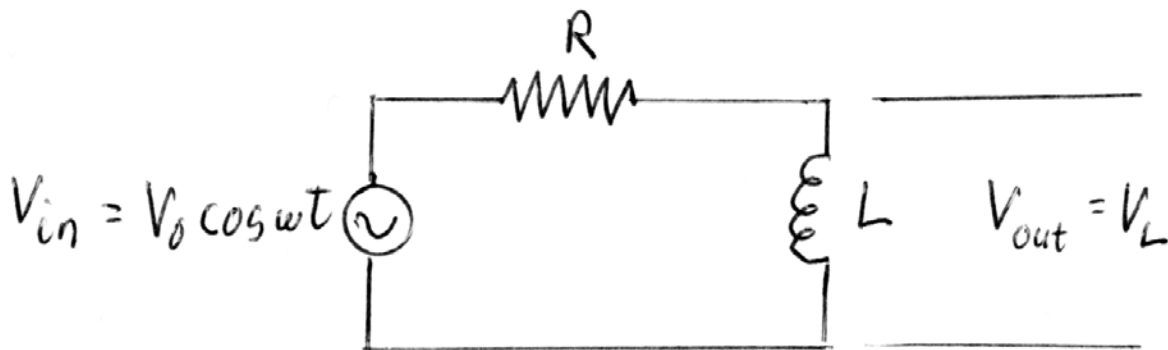

## Example RL Divider


- Consider the RL divider voltage across L
- For  $R = 10$  ohms,  $L = 5$  mH,
- Driven by a 5 V, 60 Hz with a phase of  $45^\circ$
- As before the "Input Impedance" seen by the source

$$Z_{RL60} = R + j\omega L = 10 + j377 \times 0.005 = 10 + j1.89 = 10.18 \angle 10.6$$

Thus the output is

$$V_L = \frac{Z_L}{Z_{RL}} V_{in} = \frac{1.89 \angle 90^\circ}{10.18 \angle 10.6^\circ} 5 \angle 45^\circ$$
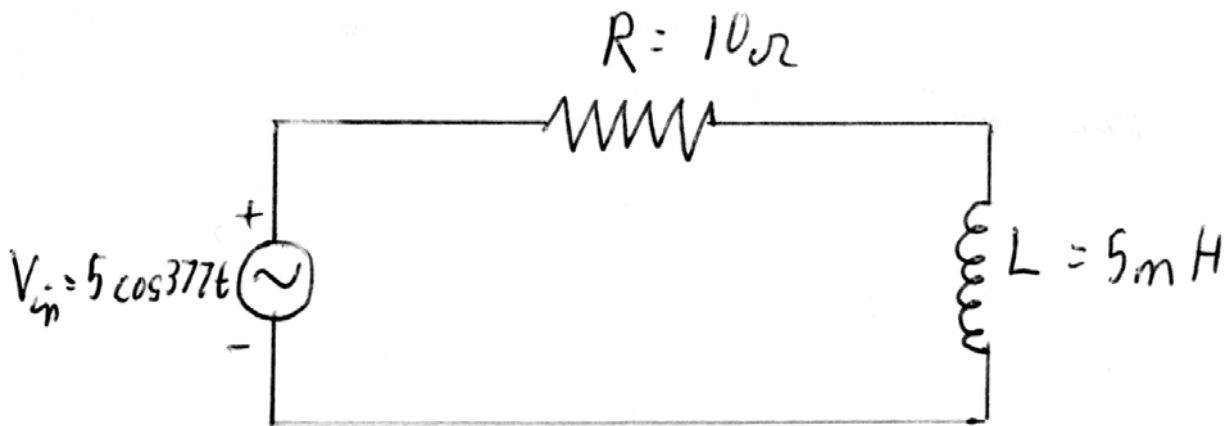
$$V_L = \frac{Z_L}{Z_{RL}} V_{in} = \frac{1.89}{10.18} 5 \angle 90 - 10.6 + 45^\circ = 0.93 \angle 124.5^\circ$$



## Dual Circuits and Complex Impedance

- Just as with resistors can create a dual  $Z$  circuit
- Dual circuit behaves same in  $I$  as first circuit does in  $V$
- Replace  $Z$  with  $Y$ 's and  $V$  with  $I$ 's
- Also replace  $L$  with  $C$  and  $C$  with  $L$
- The table of replacements are:

Table 5-2 Dual Quantities

$L$	$R$	$C$	$v$	$i$	$Z$	$X$
$C$	$G$	$L$	$i$	$v$	$Y$	$B$

Table 5-3 Dual Relations

Loop current	Node voltage
Kirchhoff's voltage law	Kirchhoff's current law
Series connection	Parallel connection
Current source	Voltage source
Short circuit	Open circuit

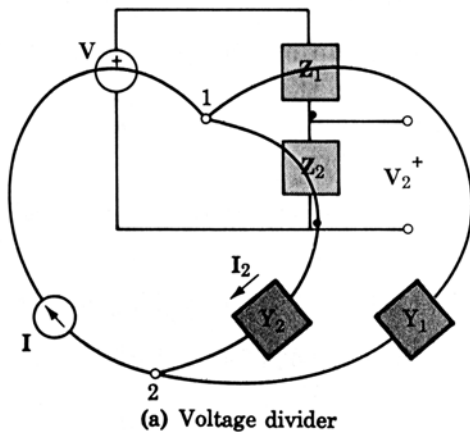


Figure 5.18 Deriving the dual of a circuit.


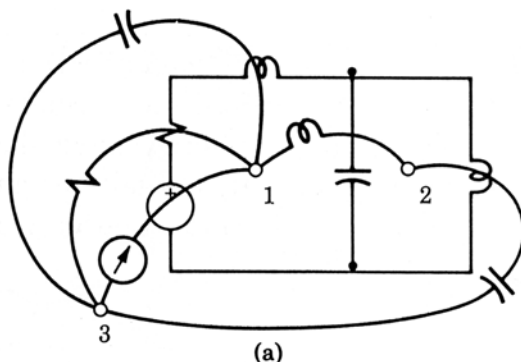
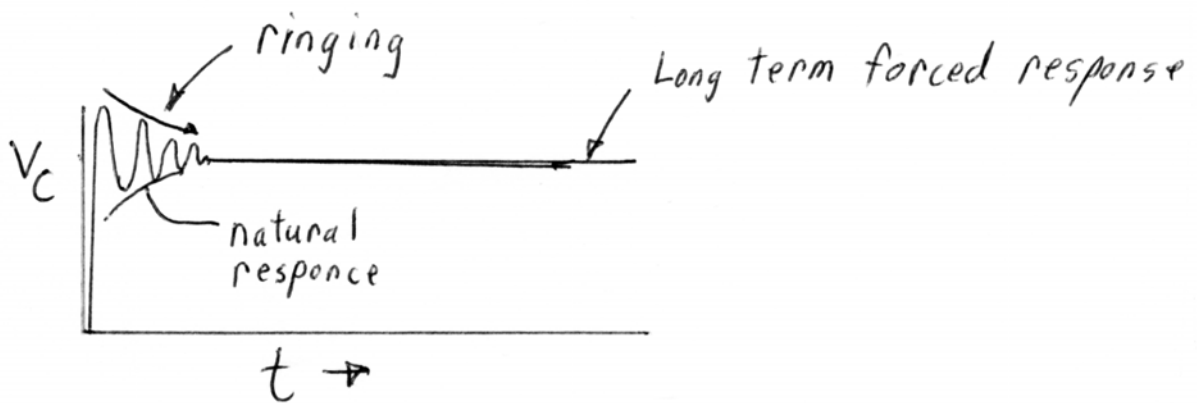


Figure 5.17 Construction of a dual circuit.
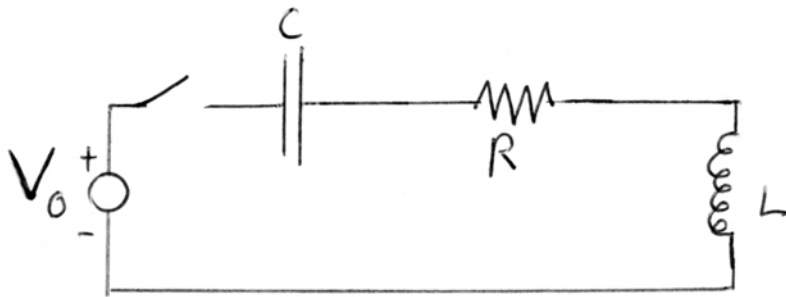
## Complete Response

- Combines both natural and forced response
- Complete response: what happens to a sudden change
- e.g. Suddenly close a switch
- Response is:

$$V_{complete} = V_{natural} + V_{forced}$$



## Initial Underdamped Second Order Systems Con'd


- for the example case  $L = 5 \text{ mH}$ ,  $C = 2 \mu\text{F}$ ,  $R = 10 \text{ ohms}$
- Exposed to a square wave: 0 to 1 V changes.
- as solved in the RCL underdamped example

$$i(t) = A_1 \exp(-\alpha t) 2j \sin(\omega t)$$

$$A_1 = \frac{V_c}{2j\omega L} = \frac{1}{2j \times 9.95 \times 10^3 \times 0.005} = \frac{20}{2j} \text{ mA}$$

The  $2j$  term is eliminated that from the sin function

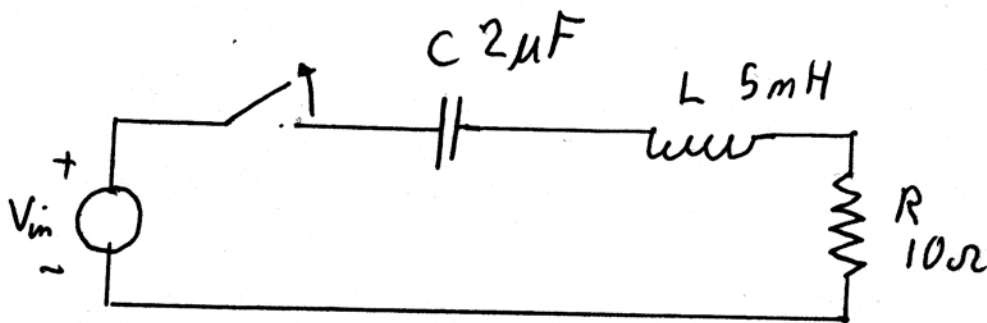
$$i(t) = 20 \exp(-10^3 t) \sin(9.95 \times 10^3 t) \text{ mA}$$



\* Simple RLC circuit

Date/Time run: 03/13/92 00:30:45

Temperature: 27.0

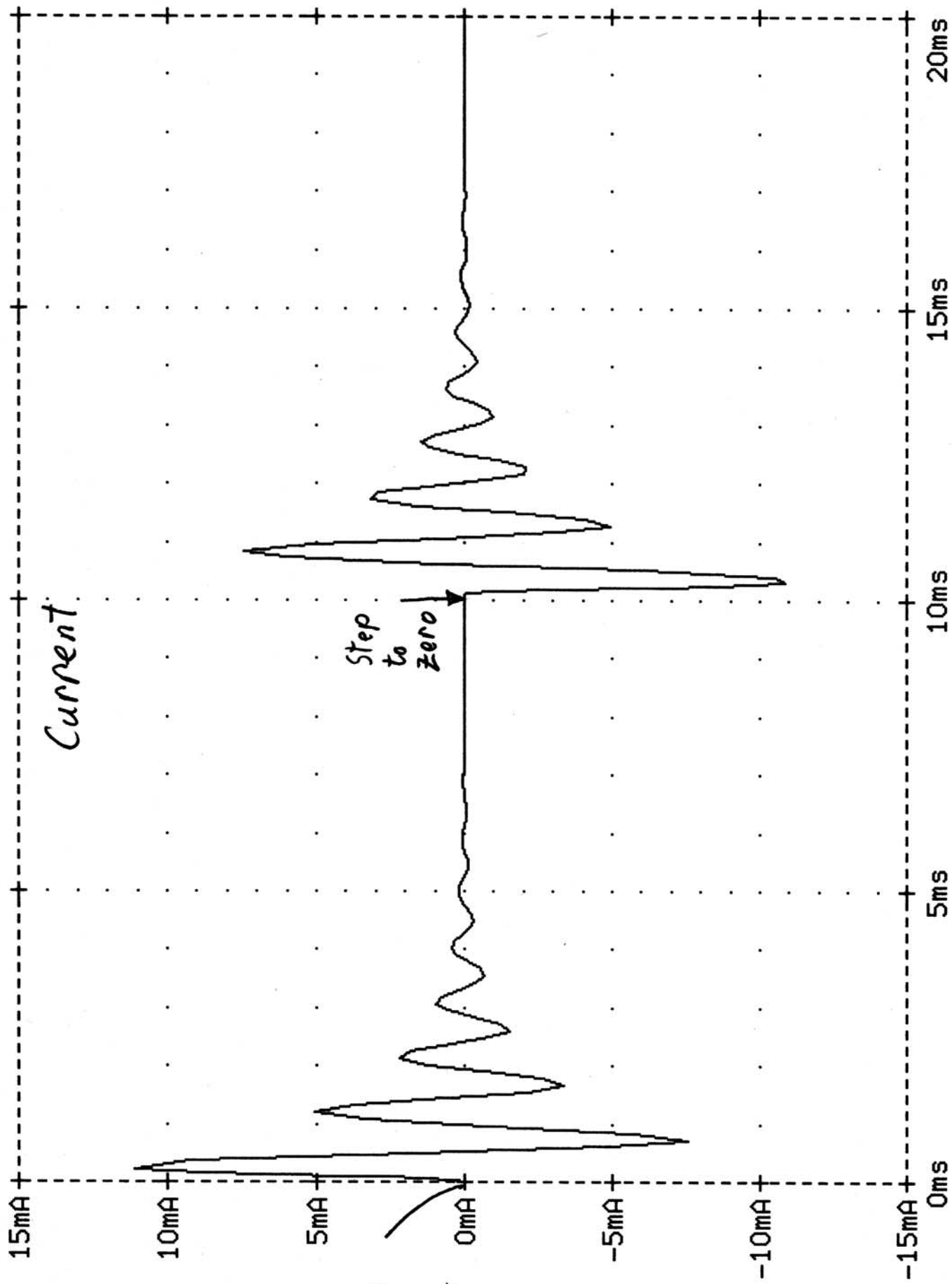

□ I (C1)


Time



\* Simple RLC circuit

Date/Time run: 03/13/92 00:30:45

Temperature: 27.0

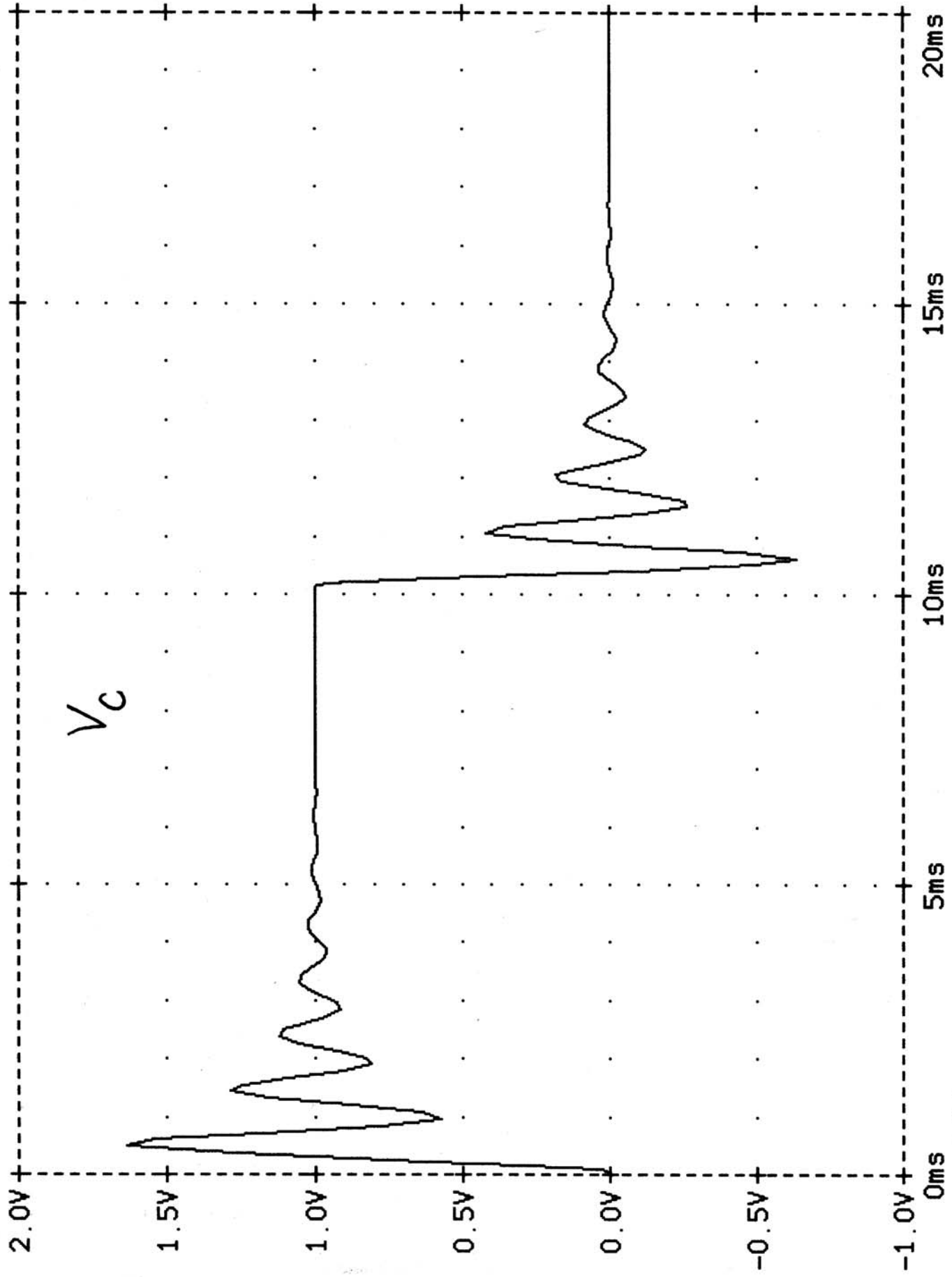

v(3)

Time

## **Complete Response: Sudden AC changes**

- Use same complete response procedure for AC
- Long term AC response given by  $Z$  impedance
- procedure the same as sudden DC changes

$$V_{complete} = V_{natural} + V_{ACforced}$$

- in long term get a phase shifted AC wave
- phase is same as  $Z$  calculations give after time
- but near switching variations

## Complete Response: Sudden AC changes on RL

- Consider an RL circuit with a switched AC voltage
- at  $t=0$  an AC voltage is switched on so

$$V(t \geq 0)_{in} = V_0 \cos(\omega t) \quad V(t < 0) = 0$$

- This is called an AC voltage step

(1) From previous results the natural response is:

$$I(t)_{nat} = A \exp\left[-\frac{Rt}{L}\right]$$

(2) In the long term the complex impedance applies


- Input Impedance of the circuit is

$$Z = R + j\omega L$$

$$I_{AC} = \frac{V}{Z} = \frac{V_0}{R + j\omega L} = V_0 \frac{R - j\omega L}{R^2 + (\omega L)^2}$$

$$\theta_Z = \arctan\left[\frac{\omega L}{R}\right]$$

$$I_{AC} = |I_{AC}| \cos(\omega t - \theta_Z)$$

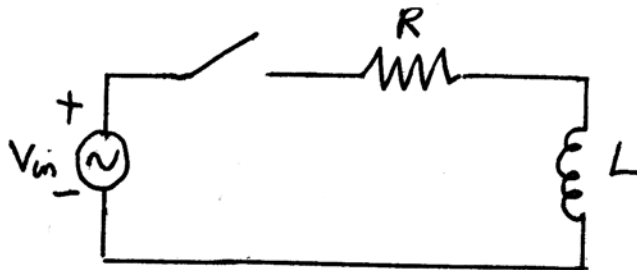

## Sudden AC changes on RL Con'd

(3) Combining the equations

$$I(t) = A \exp\left[-\frac{Rt}{L}\right] + I_{AC} \cos(\omega t - \theta_Z)$$

(4) Solve for initial conditions

At  $t=0$  L is open so no current must flow

$$0 = I(t) = A \exp\left[-\frac{R0}{L}\right] + |I_{AC}| \cos(\omega 0 - \theta_Z)$$

$$0 = A + |I_{AC}| \cos(-\theta_Z)$$

$$A = -|I_{AC}| \cos(-\theta_Z)$$

• Note: as this becomes purely inductive:

$$\theta_Z \rightarrow 90^\circ \quad A \rightarrow 0$$

## Example of sudden AC changes on RL

- Example: RL circuit subjected to a sudden AC signal
- $R = 4$  ohms,  $L = 10$  mH, and 2 V, 60 Hz cos wave
- For the natural response the decay factor is

$$\frac{R}{L} = \frac{4}{0.01} = 400 \text{ sec}^{-1}$$


- and Time constant

$$\tau = \frac{L}{R} = 2.5 \text{ msec}$$

- The AC response at long time has an impedance

$$Z = R + j\omega L = 4 + j377 \times 0.01 = 4 + j3.77 = 5.50/43.3^\circ$$
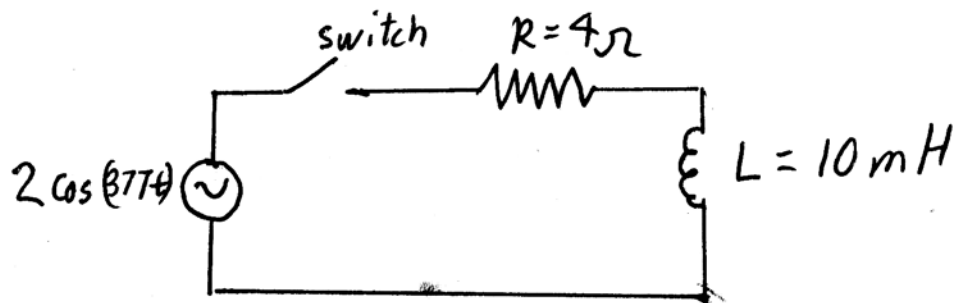
$$I_{AC} = \frac{V}{Z} = \frac{2/0}{5.50/43.3^\circ} = 0.364/43.3^\circ \text{ Amp}$$



## Example Sudden AC changes on RL Con'd

(3) Combining the equations

$$I(t) = A \exp[-400t] + I_0 \cos(377t - 43.3^\circ)$$

(4) Solving for initial conditions

At  $t=0$  L is open so no current must flow

$$A = -|I_{AC}| \cos(-\theta_Z) = 0.364 \cos(-43.3^\circ) = -0.264 \text{ Amp}$$


$$I(t) = 0.364 \cos(377t - 43.3^\circ) - 0.264 \exp(-400t)$$

- NOTE: with phasors there are two used values
- work with Peak V or I (best for cases like above)
- work with RMS V or I (best for power calculations)
- either are correct
- Do not mix the two types in one problem

Date/Time run: 03/16/92 11:35:13

Temperature: 27.0

\* Simple RL to sudden AC switch on

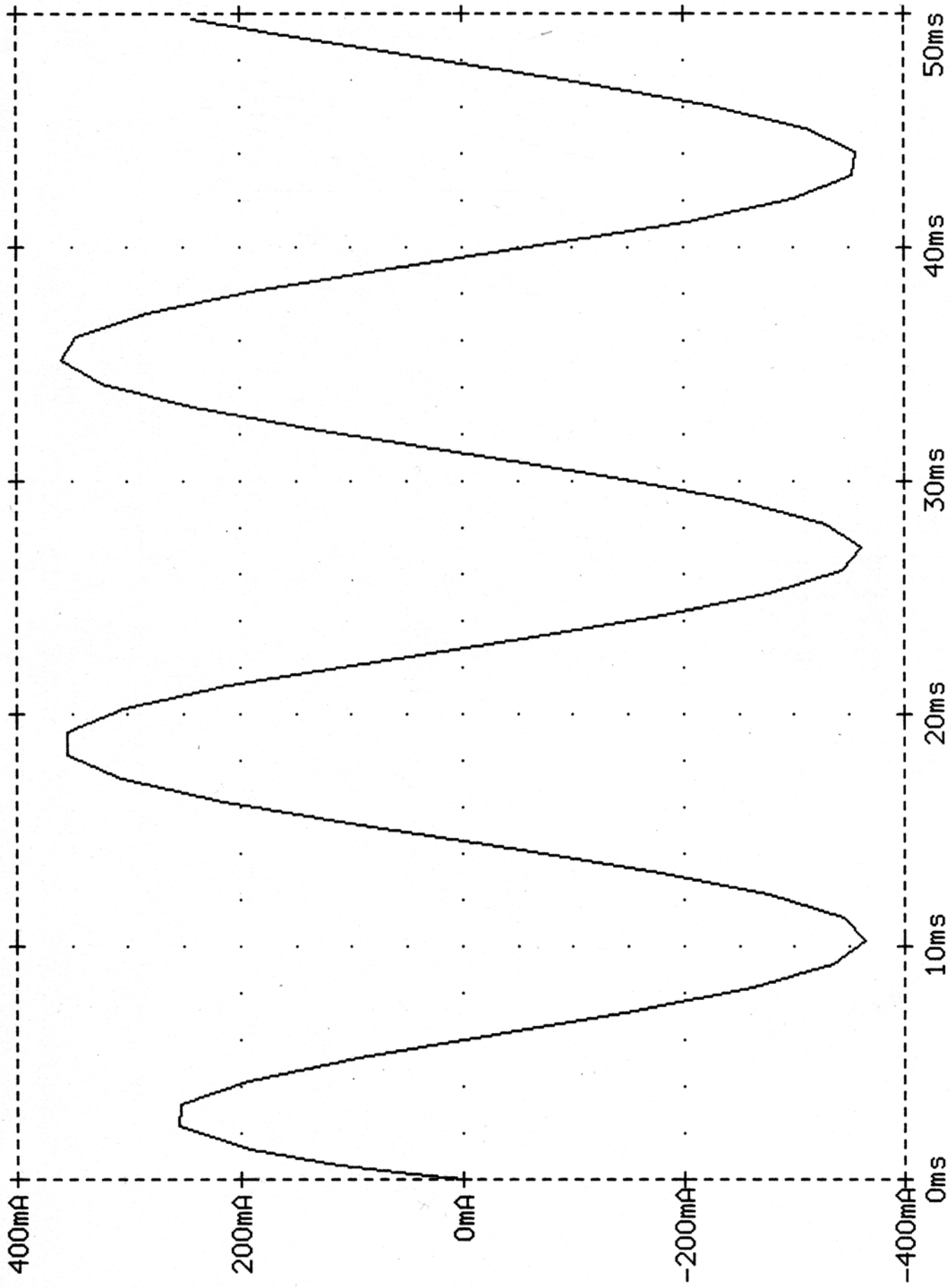

□ I (R1)

Time