

ENSC 220 Assignment 4 (Oct. 28, 2005, due Nov. 4, 2005)

1.

$$\begin{aligned} \text{[a] } \quad v_o &= -\frac{220}{44}v_a - \frac{220}{27.5}v_b - \frac{220}{80}v_c = -5v_a - 8v_b - 2.75v_c \\ v_o &= -5(1) - 8(1.5) - 2.75(-4) \\ v_o &= -5 - 12 + 11 = -6 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{[b] } \quad v_o &= 6 - 8v_b = \pm 10 \\ \therefore v_b &= -0.5 \text{ V} \quad \text{when } v_o = 10 \text{ V}; \quad v_b = 2.0 \text{ V} \quad \text{when } v_o = -10 \text{ V} \\ \therefore -0.5 \text{ V} &\leq v_b \leq 2.0 \text{ V} \end{aligned}$$

2.

[a] Assume the op-amp is operating within its linear range, then

$$i_L = \frac{9}{5} = 1.8 \text{ mA}$$

$$\text{For } R_L = 4 \text{ k}\Omega \quad v_o = (4 + 5)(1.8) = 16.2 \text{ V}$$

Now since $v_o < 18 \text{ V}$ our assumption of linear operation is correct, therefore

$$i_L = 1.8 \text{ mA}$$

$$\begin{aligned} \text{[b] } \quad i_L &= 1.8(5 + R_L) \\ 5 + R_L &= 10 \text{ k}\Omega, \quad R_L = 5 \text{ k}\Omega \end{aligned}$$


$$\text{[c] } \quad \text{Op-amp saturates for } R_L \geq 5 \text{ k}\Omega, \quad \therefore i_L = \frac{18}{5 + 7} = 1.5 \text{ mA}$$

If we assume $i_1 = i_2 \approx 0$, the voltage across the input terminals of the op-amp is

$$v_{21} \approx 9 - 5(1.5) = 1.5 \text{ V}$$

If we assume $R_{in} = 500 \text{ k}\Omega$, then $i_1 = -i_2 = -(1.5/500) = -3 \mu\text{A}$, which is small compared to i_L .

[d]

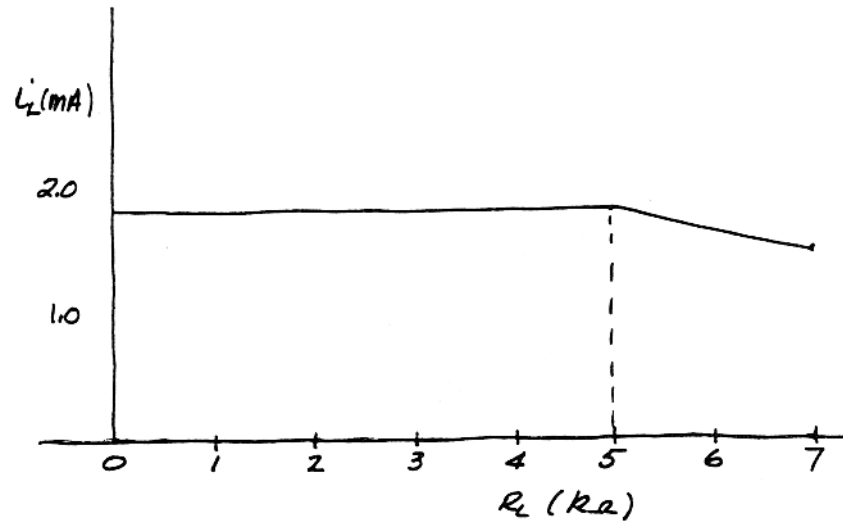

3.

$$[a] \quad \frac{v_1}{R_g} + \frac{v_1 - v_o}{180} = 0$$

$$\therefore v_o = \left(1 + \frac{180}{R_g}\right) v_1 = Gv_1 = Gv_2$$

$$\frac{v_2 - v_a}{8} + \frac{v_2 - v_b}{2} + \frac{v_2 - v_c}{1} + \frac{v_2}{9} = 0$$

$$\therefore 125v_2 = 9v_a + 36v_b + 72v_c$$

$$\therefore v_o = \frac{9Gv_a}{125} + \frac{36Gv_b}{125} + \frac{72Gv_c}{125}$$

It follows that $\frac{9G}{125} = 1.8$, $G = 0.2(125) = 25$

$$\therefore 1 + \frac{180}{R_g} = 25, \quad R_g = \frac{180}{24} = 7.5 \text{ k}\Omega$$

$$[b] \quad v_o = 1.8(0.5) + 7.2(0.25) + 14.40(0.15) = 4.86 \text{ V} = 194.40 \text{ mV}$$

$$V_2 = V_1 = \frac{4.86(7.5)}{187.5} = 194.4 \text{ mV}$$

$$i_a = \frac{500 - 194.4}{8} = 38.20 \mu\text{A}$$

$$i_b = \frac{250 - 194.4}{2} = 27.80 \mu\text{A}$$

$$i_c = \frac{150 - 194.4}{1} = -44.40 \mu\text{A}$$


$$i_g = \frac{194.40}{7.5} = 25.92 \mu\text{A}$$

$$i_h = \frac{194.40}{9} = 21.60 \mu\text{A}$$

$$i_o = -\frac{4860}{3.6} = -25.92$$

$$i_o = -1375.92 \mu\text{A}$$

4.

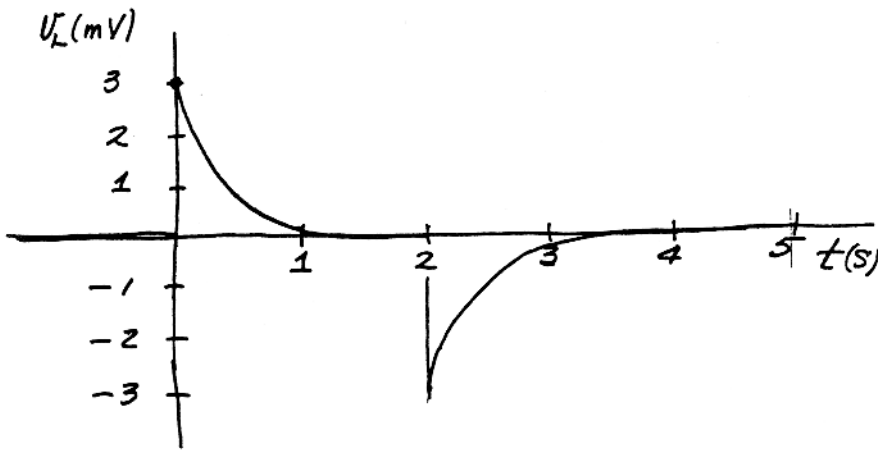

$$0 \leq t \leq 2 \text{ s}$$

$$i_L = \frac{-10^3}{2.5} \int_0^t 3 \times 10^{-3} e^{-4x} dx + 1 = -1.2 \frac{e^{-4x}}{-4} \Big|_0^t + 1$$

$$= 0.3e^{-4t} + 0.7 \text{ A}, \quad 0 \leq t \leq 2 \text{ s}$$


$$2 \text{ s} \leq t \leq \infty$$

$$i_L = \frac{-10^3}{2.5} \int_2^t -3 \times 10^{-3} e^{-4(x-2)} dx + 0.7$$

$$\text{Note: } i_L(2) = 0.3e^{-8} + 0.7 \approx 0.7 \text{ A}$$

$$i_L = 1.2 \left[\frac{e^{-4(x-2)}}{-4} \Big|_2^t + 0.7 \right] = -0.3 [e^{-4(t-2)} - 1] + 0.7$$
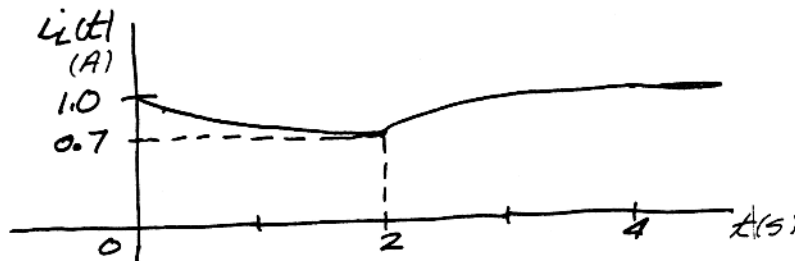
$$= -0.3e^{-4(t-2)} + 1.0 \text{ A}, \quad 2 \text{ s} \leq t \leq \infty$$



5.

$$[a] \quad w(0) = \frac{1}{2}C[v(0)]^2 = \frac{1}{2}(0.2) \times 10^{-6}(150)^2 = 2250 \times 10^{-6} = 2.25 \text{ mJ}$$

$$[b] \quad v = (A_1t + A_2)e^{-5000t}$$

$$v(0) = A_2 = 150 \text{ V}$$

$$\frac{dv}{dt} = -5000e^{-5000t}(A_1t + A_2) + e^{-5000t}(A_1)$$

$$= (-5000A_1t - 5000A_2 + A_1)e^{-5000t}$$

$$\frac{dv}{dt}(0) = A_1 - 5000A_2$$

$$i = C \frac{dv}{dt}, \quad i(0) = C \frac{dv(0)}{dt}$$

$$\therefore \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{250 \times 10^{-3}}{0.2 \times 10^{-6}} = 1250 \times 10^3$$

$$\therefore 1.25 \times 10^6 = A_1 - 5000(150)$$

$$A_1 = 1.25 \times 10^6 + 75 \times 10^4 = 2.0 \times 10^6 \frac{\text{V}}{\text{s}}$$

$$[c] \quad v = (2 \times 10^6t + 150)e^{-5000t}$$

$$i = C \frac{dv}{dt} = 0.2 \times 10^{-6} \frac{d}{dt}(2 \times 10^6t + 150)e^{-5000t}$$

$$i = \frac{d}{dt} [(0.4t + 30 \times 10^{-6})e^{-5000t}]$$

$$= (0.4t + 30 \times 10^{-6})(-5000)e^{-5000t} + e^{-5000t}(0.4)$$

$$= (-2000t - 150 \times 10^{-3} + 0.4)e^{-5000t}$$

$$= (0.25 - 2000t)e^{-5000t} \text{ A}, \quad t \geq 0$$

6.


48 μF in series with 16 μF is 12 μF with an initial voltage of 20 V, i.e.,

$$12 \mu\text{F} \frac{1}{\text{T}} \frac{-}{+} 20\text{V}$$


12 μF in parallel with 3 μF is 15 μF charged to 20 V, i.e.,

$$15 \mu\text{F} \frac{1}{\text{T}} \frac{-}{+} 20\text{V}$$

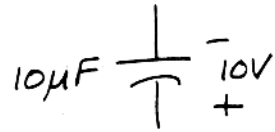
$15 \mu\text{F}$ in series with $30 \mu\text{F}$ is $10 \mu\text{F}$ with a net charge of 10 V , i.e.,



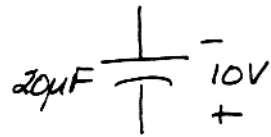$10 \mu\text{F}$ in parallel with $10 \mu\text{F}$ is $20 \mu\text{F}$ with a charge of 10 V , i.e.,




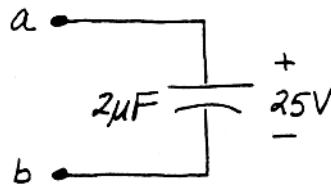$5 \mu\text{F}$ in series with $20 \mu\text{F}$ in series with $4 \mu\text{F}$ is $2 \mu\text{F}$ with a net charge of 25 V .



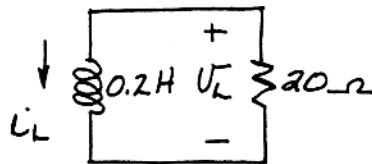7.

$$t > 0: \quad i_L(0) = \left(\frac{80}{20}\right) \left(\frac{50}{80}\right) = 2.5 \text{ A}$$



$$\tau = \frac{0.2}{20} = 0.01 \text{ s}$$

$$\frac{1}{\tau} = 100$$

$$i_L = 2.5e^{-100t} \text{ A}, \quad t \geq 0^+$$

$$v_L = -20i_L = -50e^{-100t} \text{ V}, \quad t \geq 0^+$$

$$v_o = -15i_L = -37.5e^{-100t} \text{ V}, \quad t \geq 0^+$$