
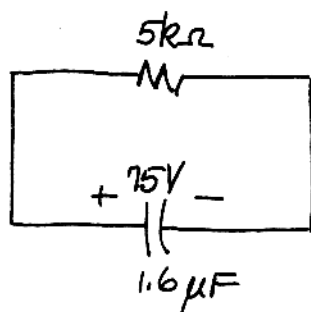


ENSC 220 Assignment 5 solutions (2005)

1.

[a] $t > 0$:

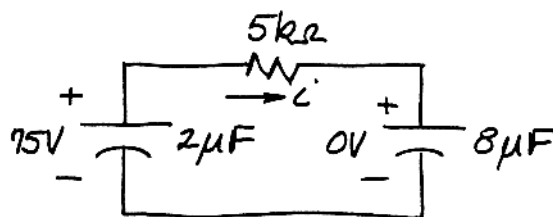

$$\tau = 8 \times 10^{-3} = 8 \text{ ms}$$

$$1/\tau = 125$$

$$i(0^+) = \frac{75}{5} \times 10^{-3} = 15 \text{ mA}$$

$$i(t) = 15e^{-125t} \text{ mA}, \quad t \geq 0^+$$

$$\begin{aligned} v_1 &= -\frac{10^6}{2} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 75 \\ &= 60(e^{-125t} - 1) + 75 = 60e^{-125t} + 15 \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} v_2 &= \frac{10^6}{8} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 0 \\ &= -15(e^{-125t} - 1) = -15e^{-125t} + 15 \text{ V}, \quad t \geq 0 \end{aligned}$$

[b] $w(0) = \frac{1}{2}(2 \times 10^{-6})(75)^2 = 5625 \mu\text{J}$

[c] $W_{\text{trapped}} = \frac{1}{2}(2 \times 10^{-6})(15)^2 + \frac{1}{2}(8 \times 10^{-6})(15)^2 = 225[10^{-6} + 4 \times 10^{-6}]$

$$W_{\text{trapped}} = 1125 \mu\text{J}$$

$$W_{\text{diss}} = w(0) - W_{\text{trapped}} = 4500 \mu\text{J}$$

$$\begin{aligned} \text{Check: } W_{\text{diss}} &= \int_0^{\infty} 225 \times 10^{-6} e^{-250t} (5000) dt \\ &= 1125 \times 10^{-3} \frac{e^{-250t}}{-250} \Big|_0^{\infty} = 4500 \mu\text{J} \end{aligned}$$

2.

[a] $v_o(0^-) = v_o(0^+) = 120 \text{ V}; \quad v_o(\infty) = -4(37.5) = -150 \text{ V}$

$$\tau = (37.5 + 12.5)10^3(0.04 \times 10^{-6}) = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$


$$\therefore v_o(t) = -150 + 270e^{-500t} \text{ V}, \quad t \geq 0^+$$

$$[b] \quad i_o(t) = -C \frac{dv_o}{dt} = -0.04 \times 10^{-6} (-135,000 e^{-500t}) = 5.4 e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$[c] \quad v_g(t) = v_o - 12.5 i_o(t) = -150 + 270 e^{-500t} - 67.5 e^{-500t} \\ = -150 + 202.5 e^{-500t} \text{ V}, \quad t \geq 0^+$$

$$[d] \quad v_g(0^+) = 52.50 \text{ V}$$

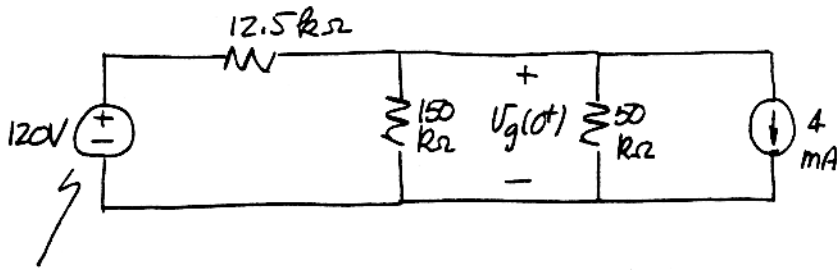We can check $v_g(0^+)$ as follows. At $t = 0^+$ we have:



Capacitor acts like a voltage source at $t = 0^+$.

$$\frac{v_g(0^+) - 120}{12.5} + \frac{v_g(0^+)}{150} + \frac{v_g(0^+)}{50} + 4 = 0 \\ 12v_g(0^+) - 1440 + v_g(0^+) + 3v_g(0^+) + 600 = 0 \\ 16v_g(0^+) = 840 \\ v_g(0^+) = 52.50 \text{ V (ok)}$$

3.

$$[a] \quad RC = 25(0.4) \times 10^{-3} = 10 \text{ ms}; \quad \frac{1}{RC} = 100; \quad v_o = 0, \quad t < 0$$

$$[b] \quad 0 \leq t \leq 250 \text{ ms:}$$

$$v_o = -100 \int_0^t -0.20 dx = 20t \text{ V}$$

$$[c] \quad 250 \text{ ms} \leq t \leq 500 \text{ ms:}$$


$$v_o(0.25) = 20(0.25) = 5 \text{ V}$$

$$v_o(t) = -100 \int_{0.25}^t 0.20 dx + 5 = -20(t - 0.25) + 5 = -20t + 10 \text{ V}$$

$$[d] \quad 500 \text{ ms} \leq t \leq \infty:$$

$$v_o(0.5) = -10 + 10 = 0 \text{ V}$$


$$v_o(t) = 0 \text{ V}$$

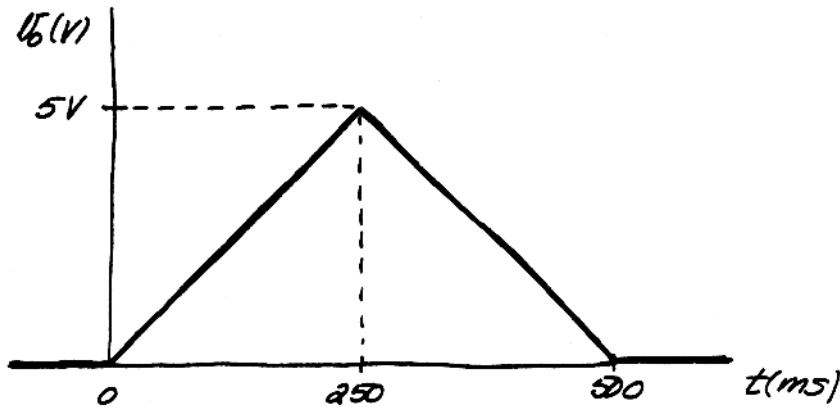

4.

[a] $v_a(0) = v_c(0) = 72 \text{ V}$

[b] $t > 0$:

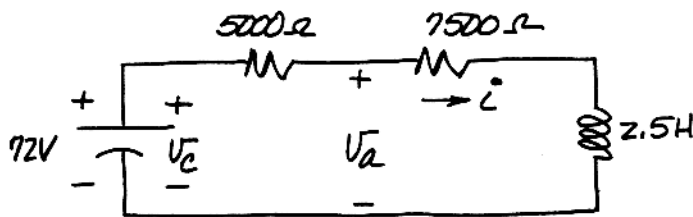

$$v_a = v_c - 5000i$$

$$\frac{dv_a}{dt} = \frac{dv_c}{dt} - 5000 \frac{di}{dt}$$

$$\frac{dv_c(0)}{dt} = 0 \quad \text{since } i(0) = 0; \quad \therefore \frac{dv_a(0)}{dt} = -5000 \frac{di(0)}{dt}$$

$$\frac{di(0)}{dt} = \frac{72}{2.5} = 28.80 \text{ A/s}; \quad \therefore \frac{dv_a(0)}{dt} = -144,000 \text{ V/s}$$

[c] $\alpha = \frac{R}{2L} = \frac{12,500}{5} = 2500 \text{ rad/s}; \quad \alpha^2 = 625 \times 10^4$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(0.1)(2.5)} = 4 \times 10^6 = 400 \times 10^4$$

$$\therefore \alpha^2 > \omega_o^2 \quad \text{overdamped}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2} = -2500 + \sqrt{225 \times 10^4} = -2500 + 1500 = -1000 \text{ rad/s}$$

$$s_2 = -2500 - 1500 = -4000 \text{ rad/s}$$

$$v_a = A_1 e^{-1000t} + A_2 e^{-4000t}; \quad v_a(0) = A_1 + A_2 = 72$$

$$\frac{dv_a(0)}{dt} = -1000A_1 - 4000A_2 = -144,000$$

$$\therefore A_1 + 4A_2 = 144; \quad \therefore 3A_2 = 72, \quad A_2 = 24, \quad A_1 = 48$$

$$\therefore v_a = 48e^{-1000t} + 24e^{-4000t} \text{ V}, \quad t \geq 0$$

5.

$$[a] \quad i_o(0) = \frac{80}{800} = 0.10 \text{ A}; \quad v_o(0) = 500(0.1) = 50 \text{ V}$$

$$L \frac{di_o(0)}{dt} = 0; \quad \therefore \frac{di_o}{dt}(0) = 0$$

$$\alpha = \frac{R}{2L} = \frac{500}{5} \times 10^3 = 10^5; \quad \alpha^2 = 10^{10}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^9)}{(2.5)(40)} = 10^{10}$$

$\therefore \omega_o^2 = \alpha^2$ critically damped

$$i_o(t) = D_1 t e^{-10^5 t} + D_2 e^{-10^5 t}$$

$$i_o(0) = D_2 = 0.10 \text{ A}$$

$$\frac{di_o}{dt}(0) = -\alpha D_2 + D_1 = 0; \quad D_1 = \alpha D_2 = 10^5(0.1) = 10^4$$

$$i_o(t) = 10^4 t e^{-10^5 t} + 0.1 e^{-10^5 t} \text{ A}, \quad t \geq 0$$

$$[b] \quad v_o(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$v_o(0) = 50 = D_2$$


$$C \frac{dv_o}{dt}(0) = -0.10; \quad \frac{dv_o}{dt} = -25 \times 10^5$$

$$\frac{dv_o}{dt}(0) = -\alpha D_2 + D_1 = -25 \times 10^5; \quad D_1 = -25 \times 10^5 + 10^5(50) = 25 \times 10^5$$

$$\therefore v_o(t) = 25 \times 10^5 t e^{-10^5 t} + 50 e^{-10^5 t} \text{ V}, \quad t \geq 0$$

6.


[a] $t < 0$:

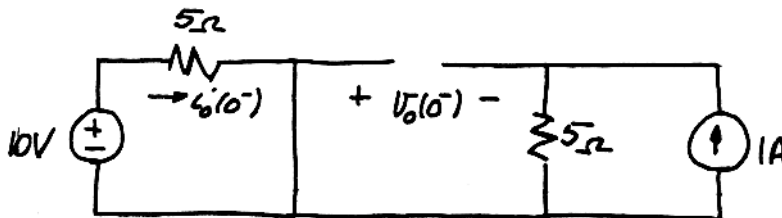

$$i_o(0^-) = 10/5 = 2 \text{ A} = i_o(0^+)$$

$$v_o(0^-) = -5(1) = -5 \text{ V} = v_o(0^+)$$

$t > 0^+$:

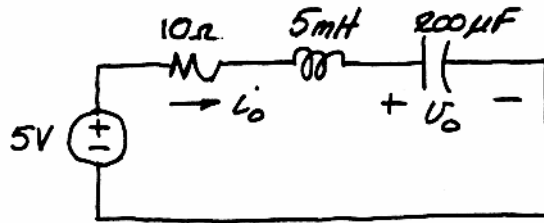


$$\alpha = \frac{R}{2L} = \frac{10}{10} \times 1000 = 1000 \text{ rad/s}; \quad \omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^6)}{(5)(200)} = 10^6$$

$$\alpha^2 = \omega^2 \quad \therefore \text{critically damped}$$

$$\therefore i_o = i_F + D'_1 t e^{-1000t} + D'_2 e^{-1000t}; \quad i_F = 0$$

$$\therefore i_o = D'_1 t e^{-1000t} + D'_2 e^{-1000t}; \quad i_o(0^+) = D'_2 = 2$$

At $t = 0^+$:

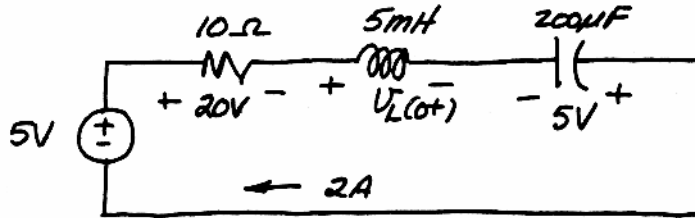

$$-5 + 20 + v_L(0^+) - 5 = 0, \quad v_L(0^+) = -10 \text{ V}$$

$$\therefore \frac{di}{dt}(0^+) = \frac{-10}{5} \times 10^3 = -2000 \text{ A/s}$$

$$\frac{di_o}{dt} = -1000e^{-1000t}(D'_1 t + D'_2) + e^{-1000t} D'_1$$

$$\frac{di_o}{dt}(0^+) = -1000D'_2 + D'_1 = -2000$$

$$-2000 + D'_1 = -2000; \quad D'_1 = 0$$

$$\therefore i_o(t) = 2e^{-1000t} \text{ A}, \quad t \geq 0$$

[b] $v_o = v_F + D'_3 t e^{-1000t} + D'_4 e^{-1000t}$

$$v_o(0^+) = v_F + D'_4 = -5$$

$$v_F = 5 \text{ V}; \quad \therefore D'_4 = -10 \text{ V}$$

$$v_o = 5 + D'_3 t e^{-1000t} - 10e^{-1000t}$$

$$\frac{dv_o}{dt} = -1000e^{-1000t}(D'_3 t - 10) + D'_3 e^{-1000t}$$

$$\frac{dv_o}{dt}(0^+) = 10,000 + D'_3$$

$$\frac{dv_o}{dt}(0^+) = \frac{2}{200} \times 10^6 = 10^4 = 10,000$$

$$\therefore D'_3 = 0$$

$$\therefore v_o = 5 - 10e^{-1000t} \text{ V}, \quad t \geq 0$$