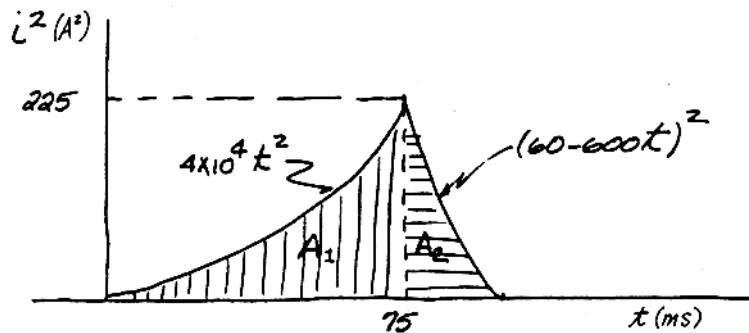


ENSC 220 – Assignment #7 Solutions (Fall 2005)

1.

P11.5



$$A_1 = \int_0^{0.075} 4 \times 10^4 t^2 dt = 4 \times 10^4 \frac{t^3}{3} \Big|_0^{0.075} = 5.625$$

$$\begin{aligned} A_2 &= \int_{0.075}^{0.1} (3600 - 72,000t + 36 \times 10^4 t^2) dt \\ &= 3600t \Big|_{0.075}^{0.10} - 36,000t^2 \Big|_{0.075}^{0.10} + 12 \times 10^4 t^3 \Big|_{0.075}^{0.10} = 90 - 157.50 + 69.375 = 1.875 \end{aligned}$$


$$A_1 + A_2 = 5.625 + 1.875 = 7.5$$

$$\frac{1}{T} = \frac{1}{0.10} = 10$$

$$\therefore I_{\text{rms}} = \sqrt{10(7.5)} = \sqrt{75} = 8.66 \text{ A (rms)}$$

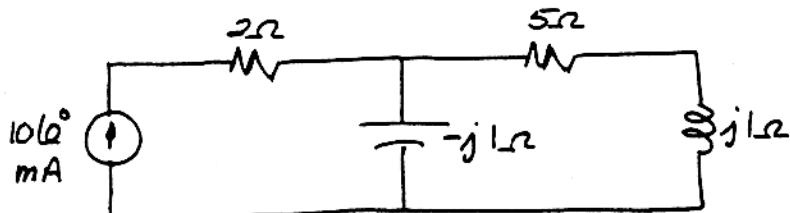2.

P11.12 $\frac{1}{j\omega C} = -j1 \Omega$; $j\omega L = j1 \Omega$



$$Z_1 = -j1/(5 + j1) = 0.2 - j1.0 \Omega; \quad Z_{\text{eq}} = 2 + 0.2 - j1 = 2.2 - j1 \Omega$$

$$P_{\text{del}} = P_{\text{diss}} = \left(\frac{10 \times 10^{-3}}{\sqrt{2}} \right)^2 (2.2) = 110 \mu\text{W}$$

3.

$$\mathbf{P11.17} \quad [\text{a}] \quad Z^* = \frac{|\mathbf{V}_{\text{eff}}|^2}{S}; \quad \mathbf{V}_{\text{eff}} = 480 \text{ V}$$

$$S = [25 + j25 + 15(0.8 - j0.6) + 11(1 + j0)] \text{ kVA} \\ = [25 + j25 + 12 - j9 + 11] \text{ kVA} = (48 + j16) \text{ kVA}$$

$$Z^* = \frac{(480)(480)}{48,000 + j16,000} = 4.32 - j1.44$$

$$Z = 4.32 + j1.44 = 4.55 / 18.43^\circ \Omega$$

$$[\text{b}] \quad \text{pf} = \cos(18.43^\circ) = 0.9487 \quad (\text{lagging})$$

4.


$$\mathbf{P17.29} \quad [\text{a}] \quad \frac{1}{sC} = \frac{20 \times 10^6}{s}; \quad sL = 0.05s$$

$$I_o = \frac{I_g(250 + 0.05s)}{[(20 \times 10^6)/s] + 250 + 0.05s}$$

$$\frac{I_o}{I_g} = \frac{s(250 + 0.05s)}{0.05s^2 + 250s + 20 \times 10^6}$$

$$H(s) = \frac{s(s + 5000)}{s^2 + 5000s + 4 \times 10^8}$$

[b]

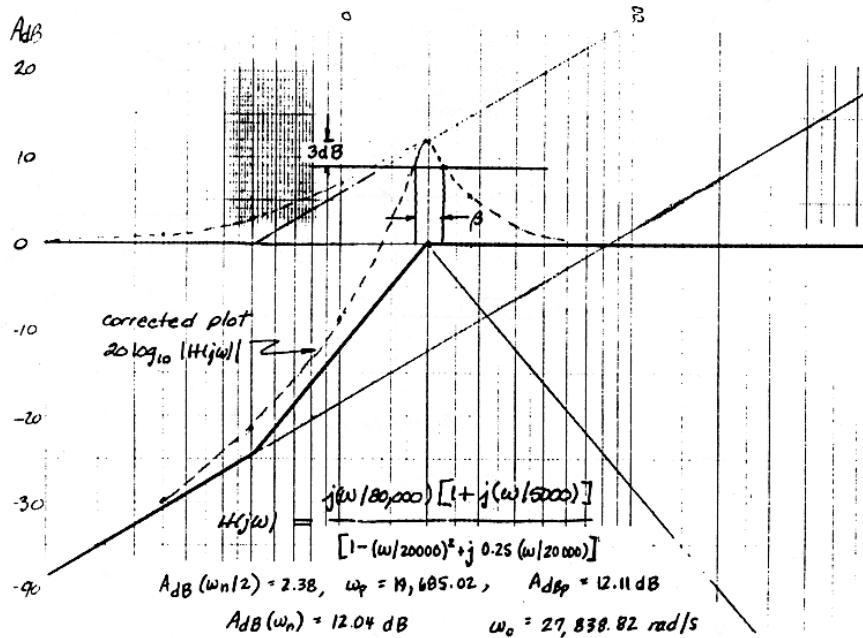

$$[\text{c}] \quad \omega_p = 19,685.02 \text{ rad/s}$$

$$[\text{d}] \quad A_{dB}(\text{max}) \cong 12.11 \text{ dB}$$

$$[\text{e}] \quad \omega_1 \cong 18,000 \text{ rad/s}; \quad \omega_2 \cong 23,500 \text{ rad/s}$$

$$[\text{f}] \quad \beta \cong 5,500 \text{ rad/s}$$

$$[\text{g}] \quad H(j\omega) = \frac{j(\omega/80,000)[1 + j(\omega/5000)]}{1 - (\omega/20,000)^2 + j0.25(\omega/20,000)}$$

$$20 \log_{10} |H(j18,000)| = 9.11 \text{ dB}$$

$$20 \log_{10} |H(j23,500)| = 9.35 \text{ dB}$$

5.

P17.31 [a] $H(j\omega) = \frac{10^8}{-\omega^2 + j3000\omega + 10^8} = \frac{1}{1 - (\omega/10^4)^2 + j(3000/10^4)(\omega/10^4)}$
 $\therefore 2\zeta = 0.30, \quad \zeta = 0.15$

$$\omega_o = \sqrt{2}\omega_p = \sqrt{2} [\omega_n \sqrt{1 - 2\zeta^2}] = \sqrt{2} [10^4 \sqrt{1 - 2(0.15)^2}] = 13,820.27 \text{ rad/s}$$

$\therefore \omega = 0 \text{ and } \omega = 13,820.27 \text{ rad/s}$

[b] $\omega_p = 10^4 \sqrt{1 - 2(0.15)^2} = 9772.41 \text{ rad/s}$

[c] $A_{dBp} = -10 \log_{10} [4\zeta^2(1 - \zeta^2)] = 10.56 \text{ dB}$
 $20 \log_{10} |H(j\omega)| = 10.56; \quad \log_{10} |H(j\omega)| = 0.53; \quad H(j\omega) = 3.37$
 $\therefore \text{Maximum ratio is 3.37.}$

6.

P17.34 $A_{dB} = 3 \text{ dB} @ 1 \text{ rad/s}$, therefore 1 rad/s looks like a corner frequency. Assume 1 rad/s is a corner, then a straight line plot would predict 20 dB @ 10 rad/sec. On the plot, $A_{dB} @ 10 \text{ rad/s}$ is 17 dB, i.e., down 3 dB. Therefore, we suspect a simple pole at 10 rad/s. At this point, we have $H(s)$ is of the form $K(s+1)/(s+10)$. A straight line plot of this function would approach a constant as s increases. However, we see from Fig. 18.34 that A_{dB} drops off and is down to 17 dB @ 100 rad/s. Therefore, the transfer function has another simple pole at 100 rad/s, thus $H(s)$ is of the form $K(s+1)/(s+10)(s+100)$. Because $H(j\omega) \rightarrow 0 \text{ dB}$ as $\omega \rightarrow 0$, K must equal 1000.