


ENSC 220 – Assignment #1 Solutions

P 2.15 [a] $v_o = 8i_a + 14i_a + 18i_a = 40(20) = 800 \text{ V}$
 $800 = 10i_o$
 $i_o = 800/10 = 80 \text{ A}$

[b] $i_g = i_a + i_o = 20 + 80 = 100 \text{ A}$

[c] $p_g(\text{delivered}) = (100)(800) = 80,000 \text{ W} = 80 \text{ kW}$

P 2.17 [a]

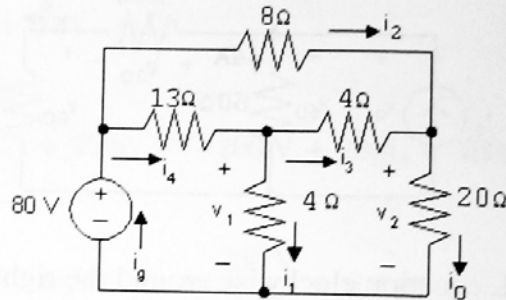

$$v_2 = 2(20) = 40 \text{ V}$$

$$v_{8\Omega} = 80 - 40 = 40 \text{ V}$$

$$i_2 = 40 \text{ V} / 8 \Omega = 5 \text{ A}$$

$$i_3 = i_o - i_2 = 2 - 5 = -3 \text{ A}$$

$$v_{4\Omega} = (-3)(4) = -12 \text{ V}$$

$$v_1 = 4i_3 + v_2 = -12 + 40 = 28 \text{ V}$$

$$i_1 = 28 \text{ V} / 4 \Omega = 7 \text{ A}$$

[b] $i_4 = i_1 + i_3 = 7 - 3 = 4 \text{ A}$

$$p_{13\Omega} = 4^2(13) = 208 \text{ W}$$

$$p_{8\Omega} = (5)^2(8) = 200 \text{ W}$$

$$p_{4\Omega} = 7^2(4) = 196 \text{ W}$$

$$p_{4\Omega} = (-3)^2(4) = 36 \text{ W}$$

$$p_{20\Omega} = 2^2(20) = 80 \text{ W}$$

[c] $\sum P_{\text{dis}} = 208 + 200 + 196 + 36 + 80 = 720 \text{ W}$

$$i_g = i_4 + i_2 = 4 + 5 = 9 \text{ A}$$

$$P_{\text{dev}} = (9)(80) = 720 \text{ W}$$

P 3.8 [a] $5 \parallel 20 = 100/25 = 4 \Omega$ $5 \parallel 20 + 9 \parallel 18 + 10 = 20 \Omega$
 $9 \parallel 18 = 162/27 = 6 \Omega$ $20 \parallel 30 = 600/50 = 12 \Omega$
 $R_{ab} = 5 + 12 + 3 = 20 \Omega$

[b] $5 + 15 = 20 \Omega$ $30 \parallel 20 = 600/50 = 12 \Omega$
 $20 \parallel 60 = 1200/80 = 15 \Omega$ $3 \parallel 6 = 18/9 = 2 \Omega$
 $15 + 10 = 25 \Omega$ $3 \parallel 6 + 30 \parallel 20 = 2 + 12 = 14 \Omega$
 $25 \parallel 75 = 1875/100 = 18.75 \Omega$ $26 \parallel 14 = 364/40 = 9.1 \Omega$
 $18.75 + 11.25 = 30 \Omega$ $R_{ab} = 2.5 + 9.1 + 3.4 = 15 \Omega$

[c] $3 + 5 = 8 \Omega$ $60 \parallel 40 = 2400/100 = 24 \Omega$
 $8 \parallel 12 = 96/20 = 4.8 \Omega$ $24 + 6 = 30 \Omega$
 $4.8 + 5.2 = 10 \Omega$ $30 \parallel 10 = 300/40 = 7.5 \Omega$
 $45 + 15 = 60 \Omega$ $R_{ab} = 1.5 + 7.5 + 1.0 = 10 \Omega$

P 3.13 [a] We can calculate the no-load voltage using voltage division to determine the voltage drop across the $500\ \Omega$ resistor:

$$v_o = \frac{500}{(2000 + 500)} \left(\frac{50}{10} \text{ V} \right) = 10 \text{ V}$$

[b] We can calculate the power if we know the current in each of the resistors. Under no-load conditions, the resistors are in series, so we can use Ohm's law to calculate the current they share:

$$i = \frac{10 \text{ V}}{2000\ \Omega + 500\ \Omega} = 0.002 \text{ A} = 2 \text{ mA}$$

Now use the formula $p = Ri^2$ to calculate the power dissipated by each resistor:

$$P_{R_1} = (2000)(0.002)^2 = 0.008 \text{ W} = 8 \text{ mW}$$

$$P_{R_2} = (500)(0.002)^2 = 0.002 \text{ W} = 2 \text{ mW}$$

[c] Since R_1 and R_2 carry the same current and $R_1 > R_2$ to satisfy the no-load voltage requirement, first pick R_1 to meet the 1 W specification

$$i_{R_1} = \frac{10}{R_1}, \quad \text{Therefore, } \left(\frac{10}{R_1} \right)^2 R_1 \leq 1$$

$$\text{Thus, } R_1 \geq \frac{100}{1} \quad \text{or} \quad R_1 \geq 100\ \Omega$$

Now use the voltage specification:

$$\frac{R_2}{R_2 + 100} \left(\frac{10}{10} \right) = 10$$

$$\text{Thus, } R_2 = 300\ \Omega$$

$R_1 = 100\ \Omega$ and $R_2 = 300\ \Omega$ are the smallest values of resistors that satisfy the 1 W specification.

P 3.21 Begin by using the relationships among the branch currents to express all branch currents in terms of i_4 :

$$i_1 = 2i_2 = 2(10i_3) = 20i_4$$

$$i_2 = 10i_3 = 10i_4$$

$$i_3 = i_4$$

Now use KCL at the top node to relate the branch currents to the current supplied by the source.

$$i_1 + i_2 + i_3 + i_4 = 8 \text{ mA}$$

Express the branch currents in terms of i_4 and solve for i_4 :

$$8 \text{ mA} = 20i_4 + 10i_4 + i_4 + i_4 = 32i_4 \quad \text{so} \quad i_4 = \frac{0.008}{32} = 0.00025 = 0.25 \text{ mA}$$

Since the resistors are in parallel, the same voltage, 4 V appears across each of them. We know the current and the voltage for R_4 so we can use Ohm's law to calculate R_4 :

$$R_4 = \frac{v_g}{i_4} = \frac{4 \text{ V}}{0.25 \text{ mA}} = 16 \text{ k}\Omega$$

Calculate i_3 from i_4 and use Ohm's law as above to find R_3 :

$$i_3 = i_4 = 0.25 \text{ mA} \quad \therefore R_3 = \frac{v_g}{i_3} = \frac{4 \text{ V}}{0.25 \text{ mA}} = 16 \text{ k}\Omega$$


Calculate i_2 from i_4 and use Ohm's law as above to find R_2 :

$$i_2 = 10i_4 = 10(0.25 \text{ mA}) = 2.5 \text{ mA} \quad \therefore R_2 = \frac{v_g}{i_2} = \frac{4 \text{ V}}{2.5 \text{ mA}} = 1.6 \text{ k}\Omega$$

Calculate i_1 from i_4 and use Ohm's law as above to find R_1 :

$$i_1 = 20i_4 = 20(0.25 \text{ mA}) = 5 \text{ mA} \quad \therefore R_1 = \frac{v_g}{i_1} = \frac{4 \text{ V}}{5 \text{ mA}} = 800 \Omega$$

The resulting circuit is shown below:

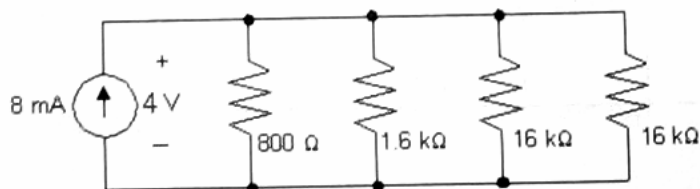

P 3.29 [a] $v_{9\Omega} = (1)(9) = 9 \text{ V}$

$$i_{2\Omega} = 9/(2 + 1) = 3 \text{ A}$$

$$i_{4\Omega} = 1 + 3 = 4 \text{ A};$$

$$v_{25\Omega} = (4)(4) + 9 = 25 \text{ V}$$

$$i_{25\Omega} = 25/25 = 1 \text{ A};$$

$$i_{3\Omega} = i_{25\Omega} + i_{9\Omega} + i_{2\Omega} = 1 + 1 + 3 = 5 \text{ A};$$

$$v_{40\Omega} = v_{25\Omega} + v_{3\Omega} = 25 + (5)(3) = 40 \text{ V}$$

$$i_{40\Omega} = 40/40 = 1 \text{ A}$$

$$i_{5\parallel 20\Omega} = i_{40\Omega} + i_{25\Omega} + i_{4\Omega} = 1 + 1 + 4 = 6 \text{ A}$$

$$v_{5\parallel 20\Omega} = (4)(6) = 24 \text{ V}$$

$$v_{32\Omega} = v_{40\Omega} + v_{5\parallel 20\Omega} = 40 + 24 = 64 \text{ V}$$

$$i_{32\Omega} = 64/32 = 2 \text{ A};$$

$$i_{10\Omega} = i_{32\Omega} + i_{5\parallel 20\Omega} = 2 + 6 = 8 \text{ A}$$

$$v_g = 10(8) + v_{32\Omega} = 80 + 64 = 144 \text{ V}.$$

[b] $P_{20\Omega} = \frac{(v_{5\parallel 20\Omega})^2}{20} = \frac{24^2}{20} = 28.8 \text{ W}$