

ENSC 220 Assignment 7 (Nov. 28, 2004, due Fri. Dec. 3, 2004)

From Electronic Circuits by Nilsson, 7th Ed.

Chapters 9, 10, 14

P9.65

P10.25

P14.15

Note for chapter 14 the text uses slightly different notation than the notes:

ω_{c1} as ω_1 in notes

ω_{c2} as ω_2 in notes

β as $\omega_2 - \omega_1$ in notes