

# ENSC 220 – Assignment #6 (Nov 21<sup>st</sup>, 2005; due Nov 28<sup>th</sup>, 2005)

1.

Find the impedance  $Z_{ab}$  in the circuit seen in Fig. **A**. Express  $Z_{ab}$  in both polar and rectangular form.

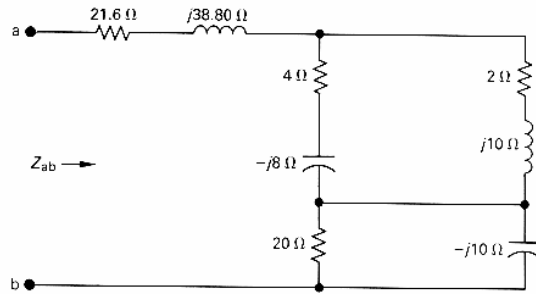


FIGURE A

2.

Find the admittance  $Y_{ab}$  in the circuit seen in Fig. **B**. Express  $Y_{ab}$  in both polar and rectangular form. Give the value of  $Y_{ab}$  in millimhos.

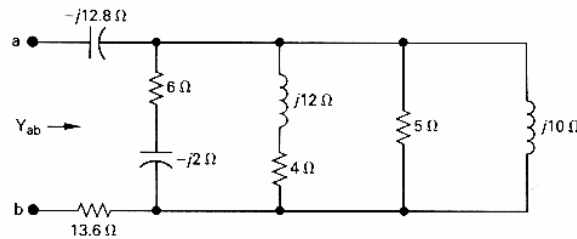


FIGURE B

3.

The current source in the circuit shown in Fig. **C** is generating a sinusoidal waveform such that  $i_g = 20 \cos(40,000t - 73.74^\circ)$  A. Find the steady-state expression for  $v_o(t)$ .

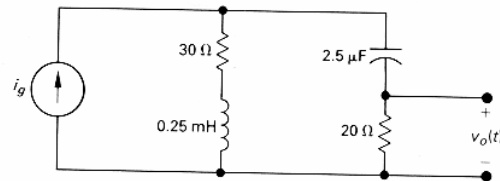


FIGURE C

4.

Find the steady-state expression for  $v_o(t)$  in the circuit seen in Fig. **D** by using the technique of source transformations. The sinusoidal voltage sources are

$$v_1 = 400 \cos(5000t + 36.87^\circ) \text{ V}$$

and

$$v_2 = 128 \sin 5000t \text{ V.}$$

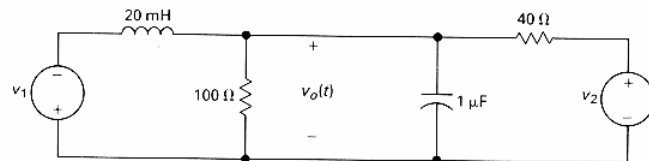


FIGURE D

5.

A resistor, denoted as  $R_t$ , is added in series with the inductor in the circuit in (N/A). The new low-pass filter circuit is shown in Fig. G.

- Derive the expression for  $H(s)$  where  $H(s) = V_o/V_i$ .
- At what frequency will the magnitude of  $H(j\omega)$  be maximum?
- What is the maximum value of the magnitude of  $H(j\omega)$ ?
- At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by  $\sqrt{2}$ ?

- Assume a resistance of  $75 \Omega$  is added in series with the 250 mH inductor in the circuit in Fig. G2. Find  $\omega_c$ ,  $H(j0)$ ,  $H(j\omega_c)$ ,  $H(j0.3\omega_c)$ , and  $H(j3\omega_c)$ .

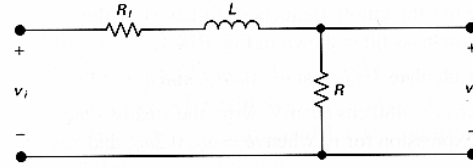


Figure G

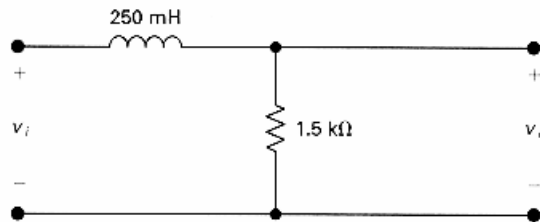


Figure G2

6.

A resistor, denoted as  $R_c$ , is connected in series with the capacitor in the circuit in Fig. H2. The new high-pass filter circuit is shown in Fig. H.

- Derive the expression for  $H(s)$  where  $H(s) = V_o/V_i$ .
- At what frequency will the magnitude of  $H(j\omega)$  be maximum?
- What is the maximum value of the magnitude of  $H(j\omega)$ ?
- At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by  $\sqrt{2}$ ?

- Assume a resistance of  $10 \text{ k}\Omega$  is connected in series with the 2.5 nF capacitor in the circuit in Fig. H3. Calculate  $\omega_c$ ,  $H(j\omega_c)$ ,  $H(j0.1\omega_c)$ , and  $H(j10\omega_c)$ .

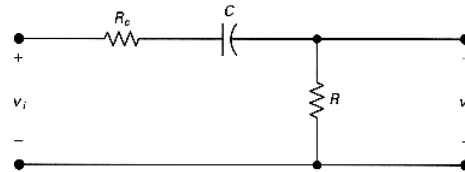


Figure H

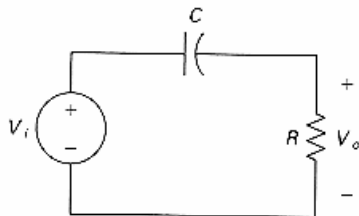


Figure H2

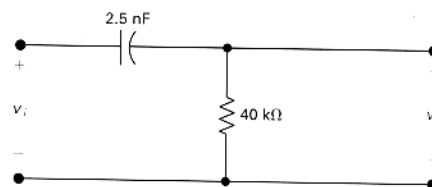


Figure H3

7.

The frequency of the sinusoidal voltage source in the circuit in Fig. E is adjusted until the amplitude of the sinusoidal output voltage is maximum. The maximum amplitude of the source voltage is 600 V.

- What is the frequency of  $v_s$  in hertz?
- What is the amplitude of  $v_o$  at the frequency given in part (a)?
- What is the bandwidth of the circuit?
- What is the  $Q$  of the circuit?
- At what frequencies will the amplitude of  $v_o$  be  $1/\sqrt{2}$  times its maximum value?

- If the 20-k $\Omega$  resistor represents the internal resistance of the source, how much does this source resistance lower the  $Q$  of the circuit?

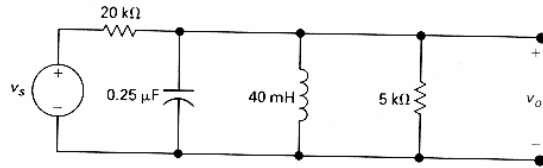


FIGURE E

8.

The sinusoidal voltage source in the circuit in Fig. F has a maximum amplitude of 50 V. The internal impedance of the source is negligible.

- At what frequency is the amplitude of  $v_o$  maximum?
- What is the maximum amplitude of  $v_o$ ?
- Over what range of frequencies will the amplitude of  $v_o$  be equal to or greater than 0.80 of its maximum value?

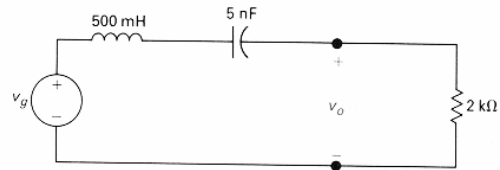


FIGURE F