

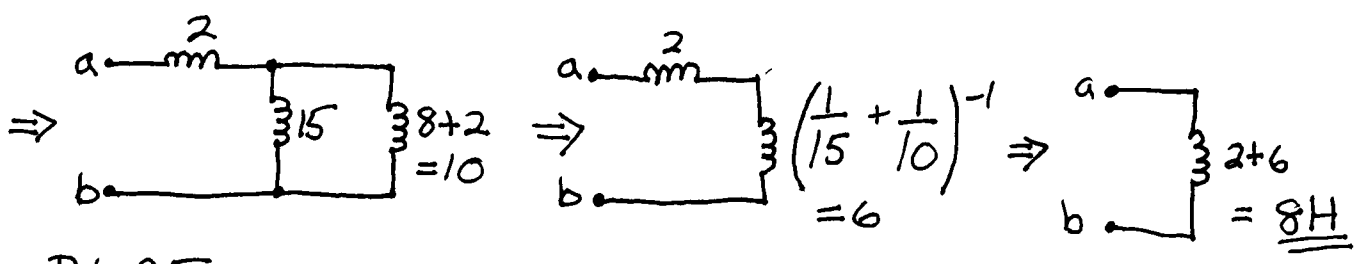
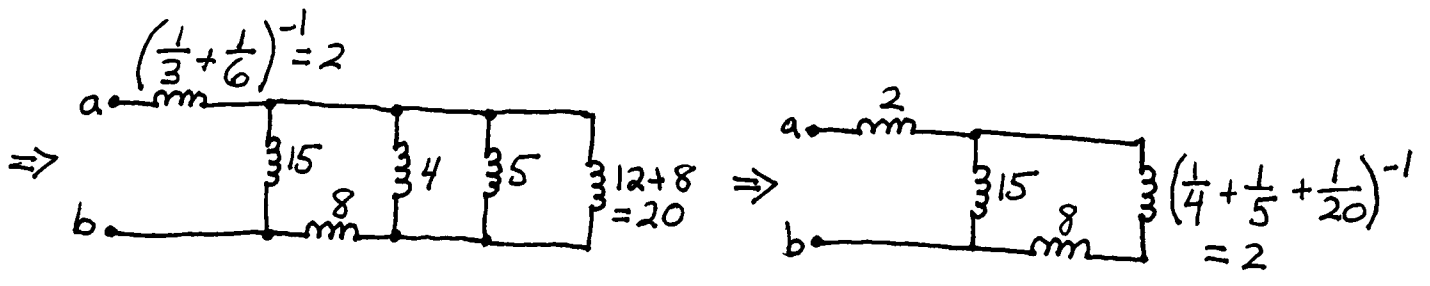
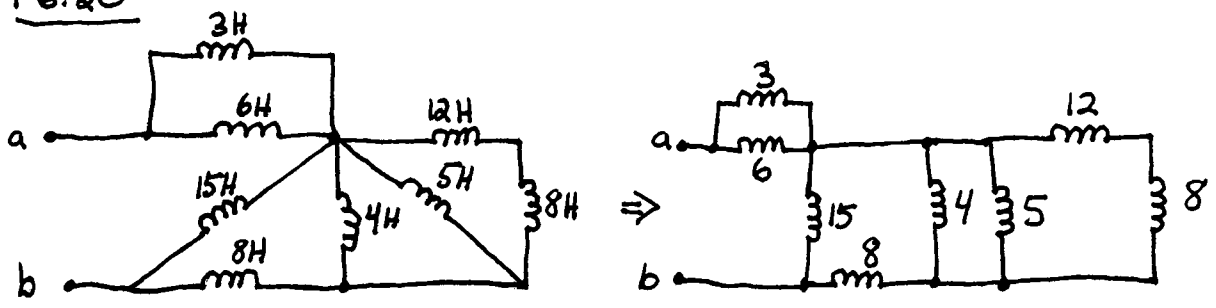
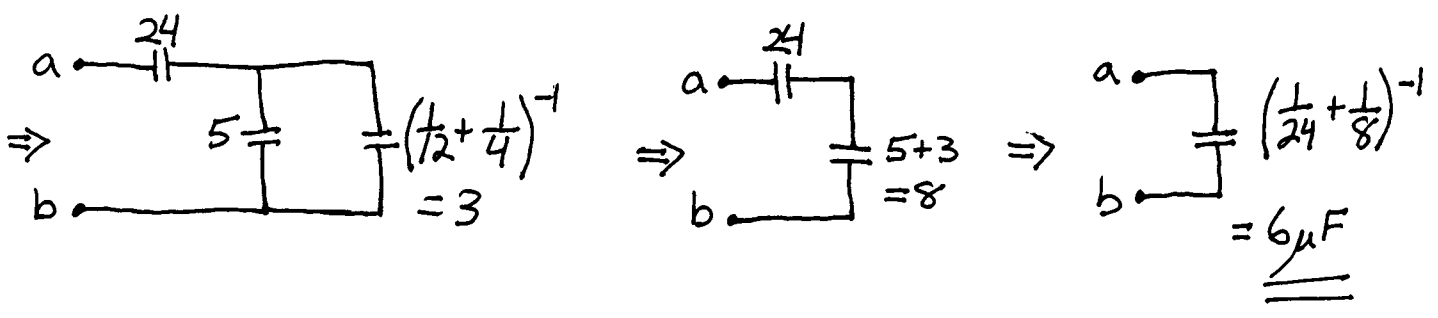



P6.20

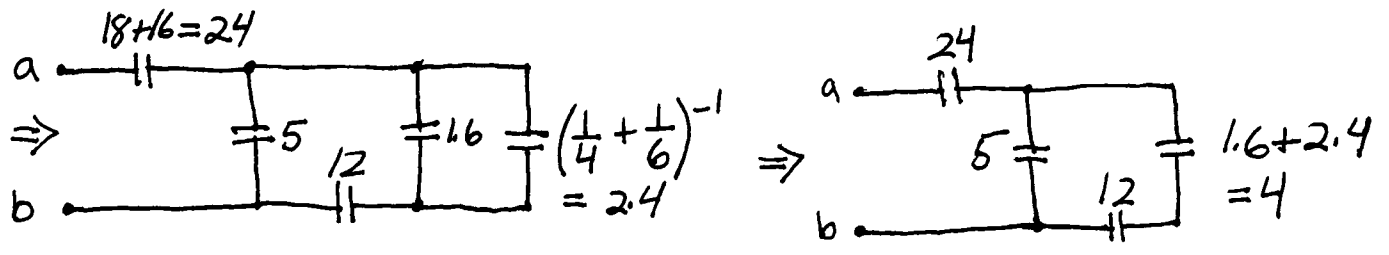

P6.25

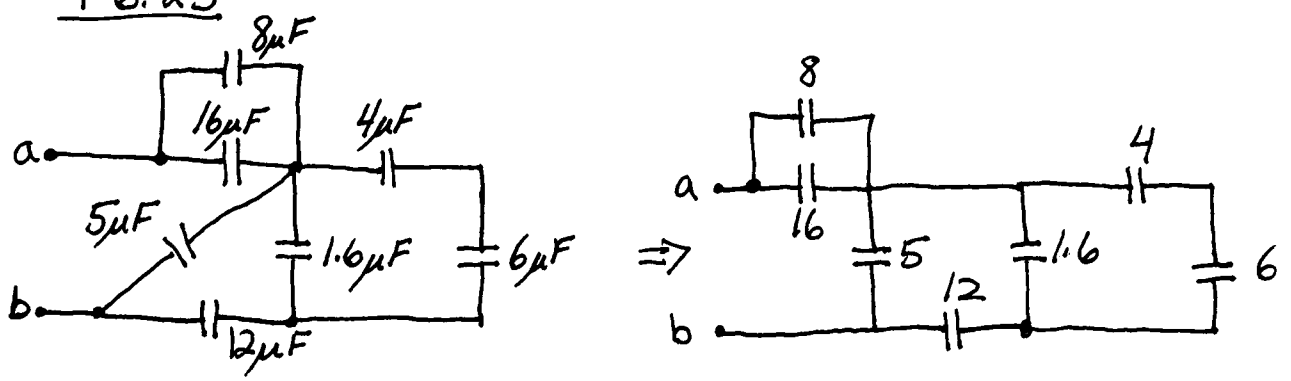


P 7.8

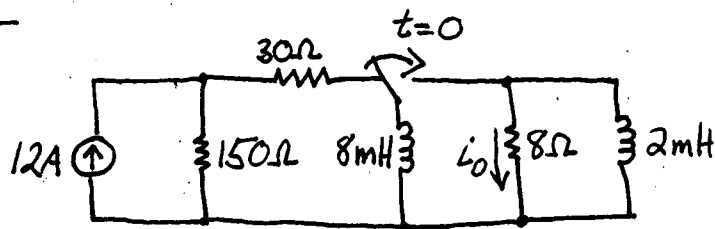

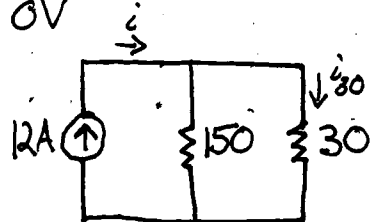
a) $i(t) = i(0)e^{-(R/L)t}$

- voltage across 8mH inductor just before switch is flipped is 0V



$$i_{30} = \frac{R_{eq}}{R_{30}} I = \left(\frac{1}{150} + \frac{1}{30} \right)^{-1} (12) = 10A$$

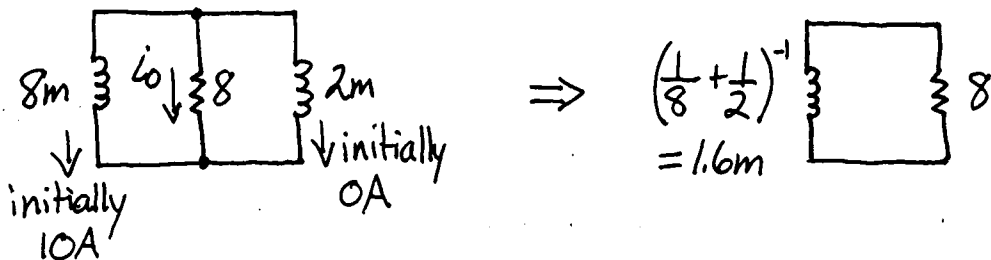- current in 8mH inductor just after switch is flipped is 10A



$$i_0(0) = -10A \text{ in } 8\Omega \text{ resistor} = I_0$$

$$i_0(t) = -10e^{-(8/1.6m)t} = -10e^{-5000t} A$$

b)
$$\begin{aligned} \omega &= \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}) \\ &= \frac{1}{2} (1.6m) (10)^2 (1 - e^{-2(5000)t}) \\ &= 0.08 (1 - e^{-10,000t}) \end{aligned}$$

$$\begin{aligned} W_{TOT} &= 0.08 (1 - e^{-10,000t}) \Big|_{t=\infty} \\ &= 0.08(1-0) \\ &= 0.08J \end{aligned}$$

$$c) .95 = \frac{0.08(1 - e^{-10,000t})}{0.08}$$

$$.95 = 1 - e^{-10,000t}$$

$$e^{-10,000t} = 0.05$$

$$-10,000t = \ln(0.05)$$



$$t = 2.995732274 \times 10^{-4} \text{ s}$$

$$\tau = \frac{L}{R} = \frac{1.6 \text{ m}}{8} = 2 \times 10^{-4}$$

$$\frac{2.995732274 \times 10^{-4}}{2 \times 10^{-4}} = 1.497866137$$

it takes $\sim 1.5\tau$ to deliver 95% of the energy


D 7.22

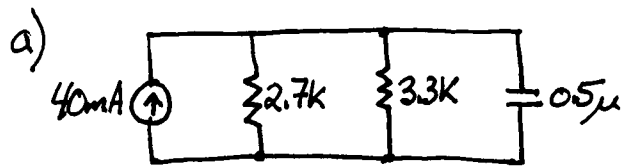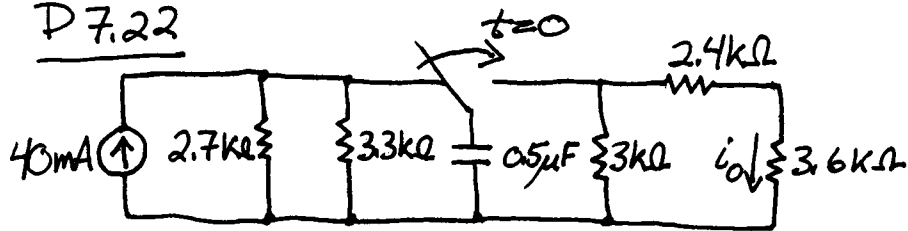

The capacitor acts like an open

$$\therefore \left(\frac{1}{2.7} + \frac{1}{3.3} \right)^{-1} = 1.485 \text{ k}\Omega$$
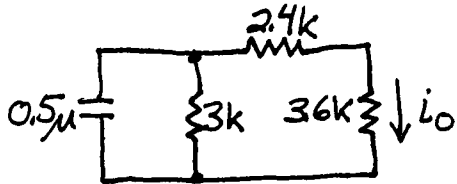
$$V_0 = 40 \text{ m} (1.485 \text{ k}) = 59.4 \text{ V} \quad \text{across the capacitor initially}$$



$$R_{eq} = \left(\frac{1}{3} + \frac{1}{2.4+3.6} \right)^{-1} = 2 \text{ k}\Omega$$

$$i_0 = \frac{V_0}{R} = \frac{59.4}{(2.4+3.6) \text{ k}} = 0.0099 \text{ A} = 9.9 \text{ mA}$$

$$i_0(t) = 9.9 e^{-t/(2 \text{ k} \cdot 0.5 \mu)} = 9.9 e^{-1000t} \text{ mA}$$

b) initial energy $w_i = \frac{1}{2} C V_0^2 = \frac{1}{2} (0.5 \mu) (59.4)^2 = 8.8209 \times 10^{-4} \text{ J}$

$$w = \int_0^t I_0^2 R e^{-2t/\tau} dt$$

I_0 through 3k resistor

$$I_0 = \frac{V_0}{R} = \frac{59.4}{3 \text{ k}} = 0.0198 \text{ A}$$

$$= \int_0^t (0.0198)^2 (3 \text{ k}) e^{-2t/\tau} dt$$

$$= 3.9204 \times 10^{-4} (3 \text{ k}) \int_0^t e^{-2t/\tau} dt$$

$$= 1.17612 \left(\frac{\tau}{2} \right) e^{-2t/\tau} \Big|_0^t$$


$$= -0.58806 \tau (e^{-2t/\tau} - 1)$$

$$w(t=500 \mu\text{s}) = -0.58806 (2 \text{ k} \cdot 0.5 \mu) (e^{-2(500 \mu)(1000)} - 1)$$


$$= -5.8806 \times 10^{-4} (e^{-1} - 1) = 3.717248158 \times 10^{-4} \text{ J}$$

$$\% \text{ energy delivered} = \frac{3.717248158 \times 10^{-4}}{8.8209 \times 10^{-4}} = 42.14137059 \%$$

P7.53

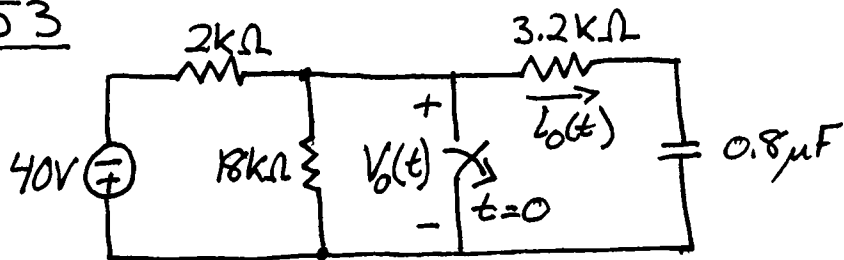

a) after switch is opened

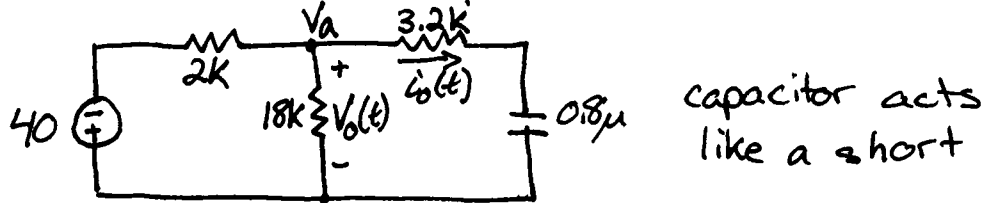

$$\frac{-40 - V_a}{2k} = \frac{V_a}{18k} + \frac{V_a}{3.2k}$$

$$-0.02 - \frac{V_a}{2k} = \frac{V_a}{18k} + \frac{V_a}{3.2k}$$


$$-0.02 = \frac{V_a}{18k} + \frac{V_a}{3.2k} + \frac{V_a}{2k}$$

$$-0.02 = 0.000868056 V_a$$

$$\Rightarrow V_a = -23.04V \quad \Rightarrow i_0(0) = \frac{-23.04}{3.2k} = -0.0072A = 7.2mA$$

b) $i_0(t=\infty) = 0A$

c) $\tau = RC$

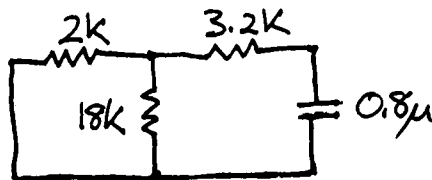

$$R_{th} = \left(\frac{1}{2k} + \frac{1}{18k} \right)^{-1} + 3.2k$$


$$= 1.8k + 3.2k$$

$$= 5k\Omega$$


$$\tau = 5k(0.8\mu)$$

$$= 0.004s^{-1}$$
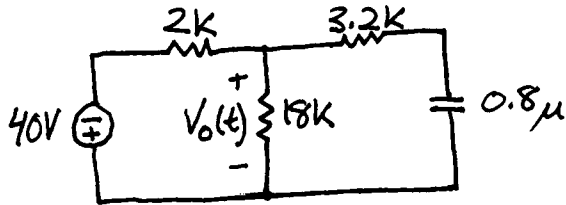
$$d) i_0(t) = \begin{pmatrix} V_f \\ \bar{R} \end{pmatrix} - \begin{pmatrix} V_0 \\ \bar{R} \end{pmatrix} e^{-t/\tau}$$



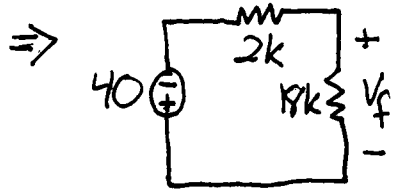capacitor acts like an open at $t = \infty$



$$V_f = \frac{18k}{2k+18k} \cdot (-40) = -36V$$

$$i_0(t) = \begin{pmatrix} -36 \\ \frac{5k}{5k} \end{pmatrix} e^{-t/0.004}$$



$$= -7.2 e^{-250t} \text{ mA}$$

$$e) V_0(t) = V_f + (V_0 - V_f) e^{-t/\tau}$$

$$= -36 + (0 - 36) e^{-250t}$$

$$= -36 + 36 e^{-250t} \text{ V}$$

P 7.96

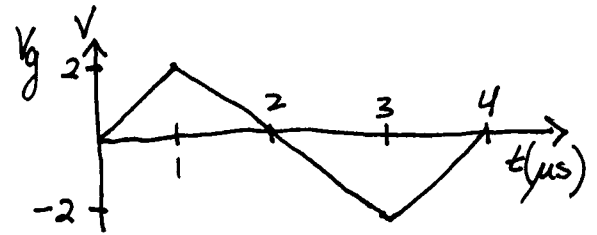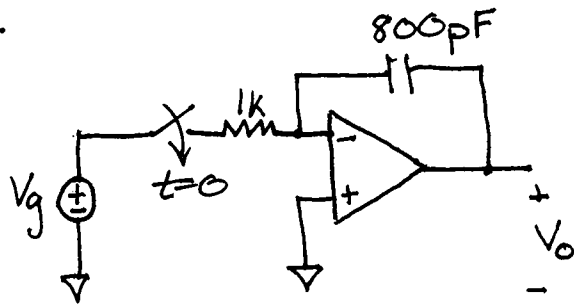

a) $0 \leq t \leq 1 \mu s$

$$V_o(t) = -\frac{1}{R_s C_f} \int_{t_0}^t V_s dt + V_o(t_0)$$

$$t_0 = 0, V_o(t_0) = 0, V_s = \frac{2t}{1\mu} = 2 \times 10^6 t$$

$$\begin{aligned} V_o(t) &= -\frac{1}{1k(800p)} \int_0^t 2 \times 10^6 t dt \\ &= -2.5 \times 10^{12} \frac{t^2}{2} \Big|_0^t \\ &= -1.25 \times 10^{12} t^2 V \end{aligned}$$

$1 \leq t \leq 3 \mu s$

$$t_0 = 1 \mu s, V_o(t_0) = -1.25V, V_s = \frac{-4}{2\mu} t + 4 = -2 \times 10^6 t + 4$$

$$\begin{aligned} V_o(t) &= \frac{-1}{1k(800p)} \int_{1\mu}^t (-2 \times 10^6 t + 4) dt - 1.25 \\ &= (1.25 \times 10^{12} t^2 - 5 \times 10^6 t) \Big|_{1\mu}^t - 1.25 \end{aligned}$$

$$= 1.25 \times 10^{12} t^2 - 5 \times 10^6 t - (1.25 \times 10^{12} (\mu)^2 - 5 \times 10^6 (\mu)) - 1.25$$

$$= 1.25 \times 10^{12} t^2 - 5 \times 10^6 t - (1.25 - 5) - 1.25$$

$$= 1.25 \times 10^{12} t^2 - 5 \times 10^6 t + 2.5V$$

$$3\mu\text{s} \leq t \leq 4\mu\text{s}$$

$$t_0 = 3\mu\text{s}, V_0(t=3\mu\text{s}) = -1.25\text{V}, V_s = \frac{2}{\mu}t - 8 = 2 \times 10^6 t - 8$$


$$V_0(t) = \frac{-1}{1\text{k}(800\text{p})} \int_{3\mu}^t (2 \times 10^6 t - 8) dt - 1.25$$

$$= (-1.25 \times 10^{12} t^2 + 10 \times 10^6 t) \Big|_{3\mu}^t - 1.25$$

$$= -1.25 \times 10^{12} t^2 + 1 \times 10^7 t - (-1.25 \times 10^{12} (3\mu)^2 + 1 \times 10^7 (3\mu)) - 1.25$$

$$= -1.25 \times 10^{12} t^2 + 1 \times 10^7 t - 18.75 - 1.25$$
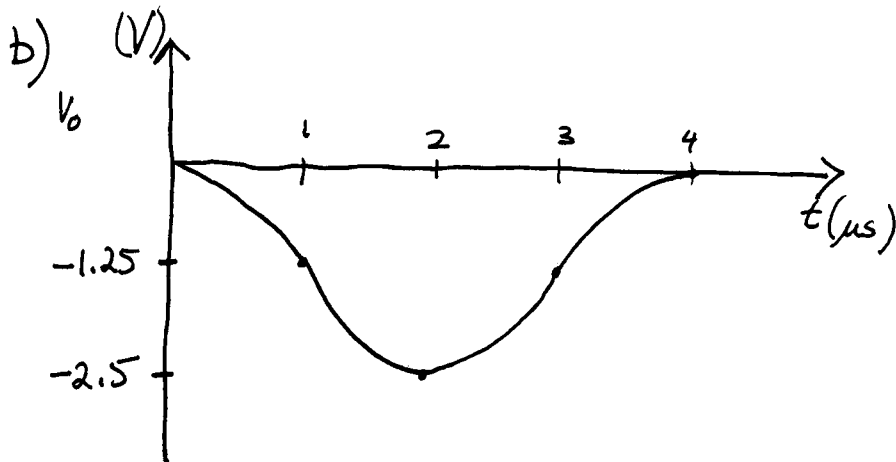
$$= -1.25 \times 10^{12} t^2 + 1 \times 10^7 t - 20\text{V}$$



$$V_0(0) = 0, V_0(1\mu\text{s}) = -1.25\text{V}, V_0(2\mu\text{s}) = -2.5\text{V}$$

$$V_0(3\mu\text{s}) = -1.25\text{V}, V_0(4\mu\text{s}) = 0\text{V}$$

c) repeats