

ENSC 220 – Fall 2005
ELECTRIC CIRCUITS I

Lab #1: Verification of KVL and KCL (Due: Oct 11, 2005)

OBJECTIVE:

Using the circuit below, you can verify KVL by showing that the sum of voltages around the loop $V_{in} \rightarrow R1 \rightarrow R2$ is zero. You can also verify KCL by showing that the currents entering node "a" sum to zero.

PREPARATION:

Read about power supply, DMM and breadboards to make sure you understand the operation of instruments and usage of the bread board. For example, you can read the Lab Handbook 2.2.2 (Lab Power Supplies), 2.2.3 (DMM), 2.3.3 (Resistors) and 2.4.1 (Breadboards). Derive equations for all circuit voltages and currents in terms of V_{in} , $R1$, $R2$, and $R3$.

EQUIPMENT:


Basic lab tools and breadboard, Digital multimeter (DMM-Fluke 8010A) and DC power supply

NOTES:

Set current limit and connect the power after verifying the circuit & connections thoroughly. Check the multimeter setup before making any measurement. Improper setup can give incorrect readings and/or damage the meter.

IMPORTANT: When constructing the circuit, select resistor values such that the power dissipated in each resistor in the circuit is well below its 1/4 watt rating.

METHOD:

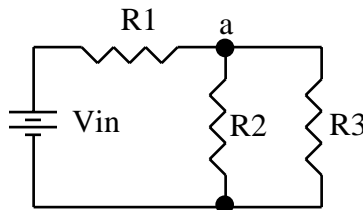

Schematic of the KCL/KVL verification circuit

Construct the circuit shown above. Choose appropriate $R1$, $R2$, and $R3$ (all three of them in few Kilo Ohms range), and measure their values using the DMM. Apply the power and adjust $V_{in}=1.0$ V (approximately), under load.

KVL: Calculate the expected voltages across $R1$ and $R2$, and then measure them.

KCL: Calculate the expected currents through $R1$, $R2$, and $R3$, and then measure them.

DISCUSSION:

- Find the DMM accuracy for measuring DC voltage, current, and resistance.
- Choose one example from your calculations and show how equipment accuracy and measurement errors propagate through equations to affect expected values.
- Explain how the measurement process itself affects the resistances, voltages and currents that you are measuring.
- Reconcile each measurement against the expected value. You should be able to explain any differences within a specified range of certainty.
- Can you think of a more effective method of confirming KCL?