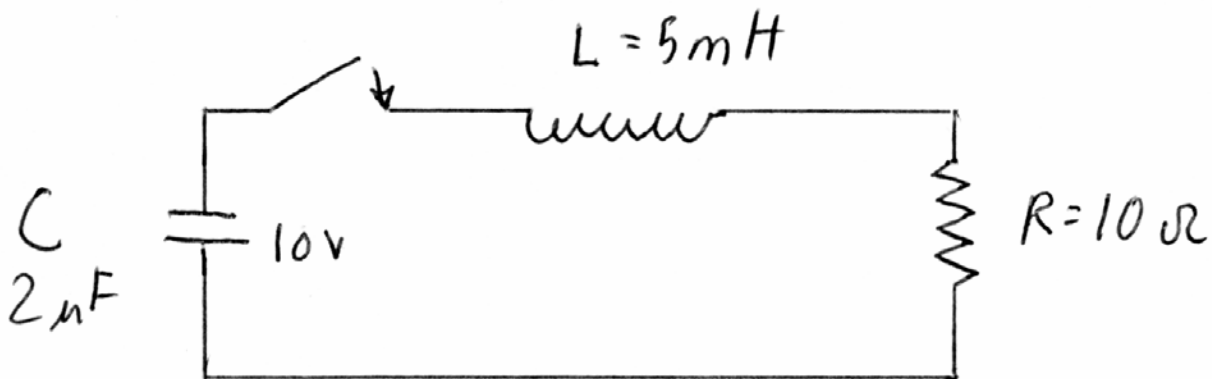



Underdamped Second Order Systems

- Underdamped case results in complex numbers
- This generates a decaying oscillating case.
- Consider a case of the RLC circuit below
- Assume the Capacitor is initially charged to 10 V
- What happens is C's voltage is creates current
- That current transfers energy in the inductor L
- Energy is lost by the resistors R
- Eventually C's voltage drops below L's
- Current flow changes direction
- Inductor now transfers energy back to C
- C and L exchange energy, R losses it
- This energy loss is called Damping



* Simple RLC circuit, underdamping, C charged initially
Date/Time run: 02/24/92 11:04:43 Temperature: 27.0

Energy flows

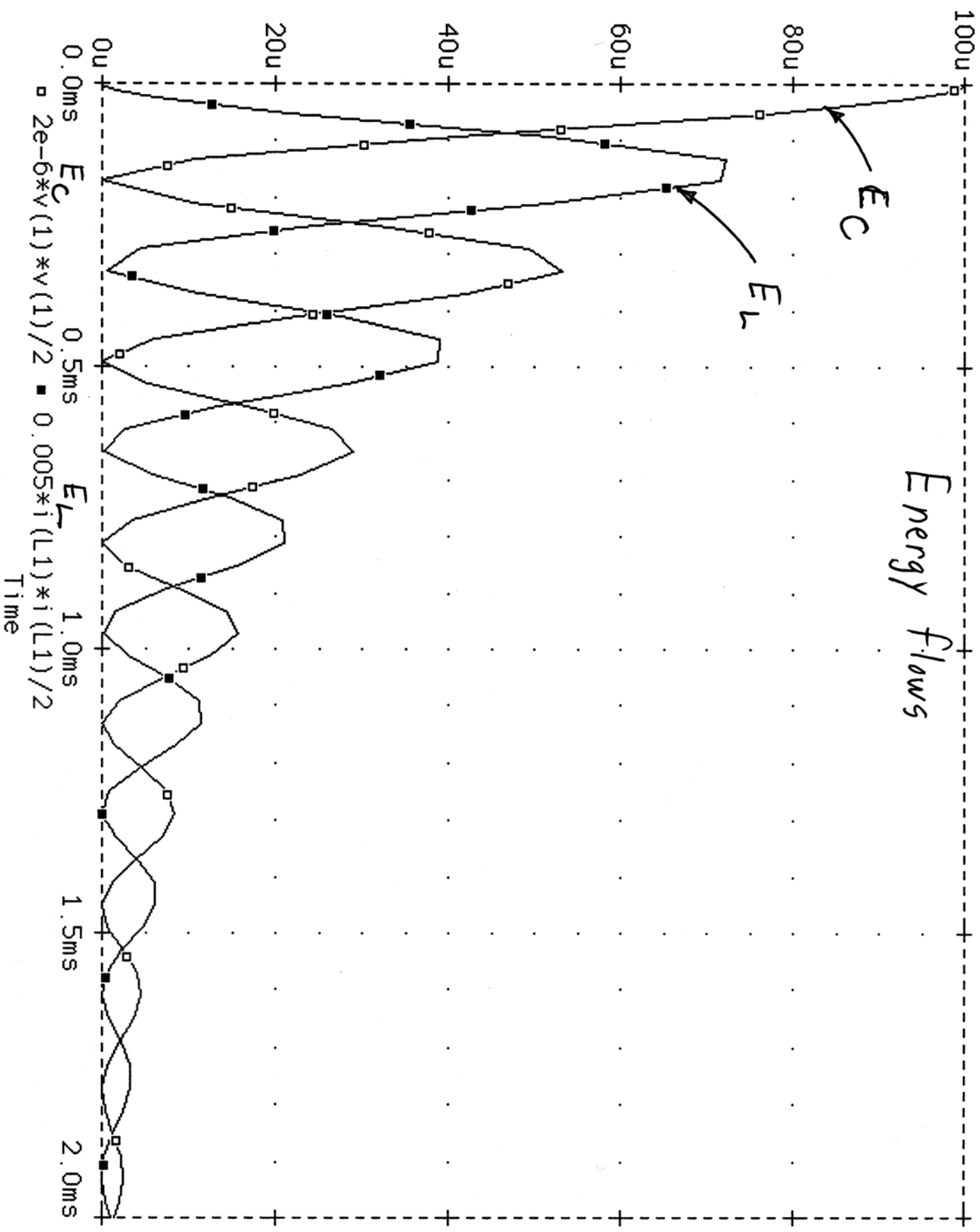

Underdamped RLC circuit Equations

- continuing with the simple RLC circuit
- Recall the differential equation
- also called the "homogeneous equation"


$$0 = L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i$$

- Thus for the characteristic equation

$$0 = s^2 + s \frac{R}{L} + \frac{1}{LC}$$

- for Natural Response want initial conditions
- but no driving voltage or current applied thereafter
- The general solution is:
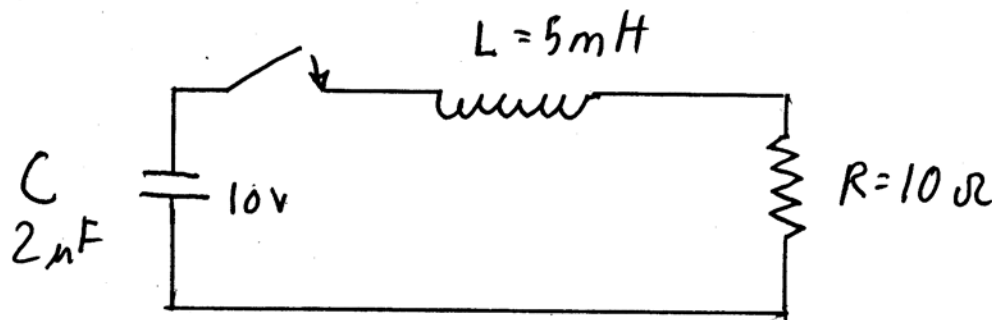
$$s = -\frac{R}{2L} \pm \left[\left(\frac{R}{2L} \right)^2 - \frac{1}{LC} \right]^{1/2}$$



Underdamped RLC circuit Equations Con'd

- For underdamped the discriminant < 0

$$D = \left[\left(\frac{R}{2L} \right)^2 - \frac{1}{LC} \right] = \left[\left(\frac{10}{2 \times 0.005} \right)^2 - \frac{1}{0.005 \times 2 \times 10^{-6}} \right]$$
$$= 10^6 - 10^8 = -9.9 \times 10^7$$

Underdamped Second Order Systems Con'd

- Define several terms from the equations
- the damping factor is:

$$\alpha = \frac{R}{2L}$$

- The Natural angular frequency of the circuit

$$\omega_n^2 = \frac{1}{LC}$$

- the Natural frequency is that when no damping
- the damped frequency is:

$$\omega^2 = \left[\left(\frac{R}{2L} \right)^2 - \frac{1}{LC} \right] = \omega_n^2 - \alpha^2$$

- Then can define the solutions

$$s_1 = -\alpha + j\omega \quad s_2 = -\alpha - j\omega$$

- The combined solution is

$$i(t) = A_1 \exp([- \alpha + j\omega]t) + A_2 \exp([- \alpha - j\omega]t)$$

- The A's are constants set by the initial conditions

Example Underdamped Second Order Circuit Con'd

- for the example case $L = 5 \text{ mH}$, $C = 2 \mu\text{F}$, $R = 10 \text{ ohms}$
- also assume C is charged to 10 V at $t = 0$
- the damping factor is:

$$\alpha = \frac{R}{2L} = \frac{10}{2 \times 0.005} = 10^3$$

- The Natural angular frequency of the circuit

$$\omega_n^2 = \frac{1}{LC} = \frac{1}{0.005 \times 2 \times 10^{-6}} = 10^8$$

- the damped frequency is:

$$\omega^2 = \omega_n^2 - \alpha^2 = 10^8 - 10^6 = 9.9 \times 10^7$$


$$\omega = 9.95 \times 10^3$$

- and the period is

$$T = \frac{2\pi}{\omega} = \frac{2\pi}{9.95 \times 10^3} = 6.31 \times 10^{-4} \text{ sec.}$$

- The combined solution is
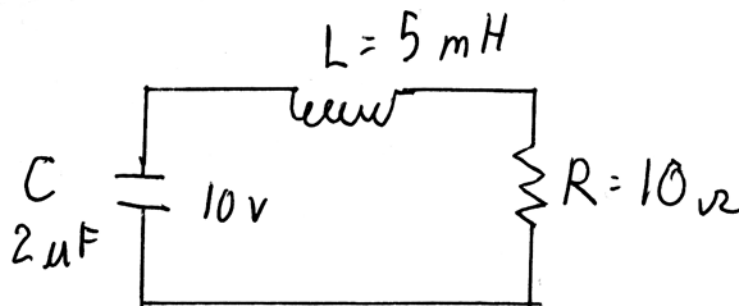
$$i(t) = A_1 \exp([- \alpha + j\omega]t) + A_2 \exp([- \alpha - j\omega]t)$$



Initial Underdamped Second Order Systems Con'd

- for the example case $L = 5 \text{ mH}$, $C = 2 \text{ mF}$, $R = 10 \text{ ohms}$
- Since L acts as an open initially then $i(0) = 0$, thus

$$i(0) = A_1 + A_2 = 0$$

- because $\exp(0) = 1$, thus

$$A_2 = -A_1$$

- Hence

$$\begin{aligned} i(t) &= A_1 \exp(-\alpha t) [\exp(j\omega t) - \exp(-j\omega t)] \\ &= A_1 \exp(-\alpha t) 2j \sin(\omega t) \end{aligned}$$

because

$$\sin(\theta) = \frac{1}{2j} [\exp(j\theta) - \exp(-j\theta)]$$

Initial Underdamped Second Order Systems Con'd

- since the inductor acts open at time zero

$$V_c = L \frac{di}{dt} = V_L$$

$$\begin{aligned} \frac{di(t=0)}{dt} &= A_1 2j [-\alpha \exp(-\alpha t) \sin(\omega t) + \omega \exp(-\alpha t) \cos(\omega t)] \\ &= 2\omega j A_1 = \frac{di(t=0)}{dt} \end{aligned}$$

because $\sin(0) = 0$ and $\cos(0) = 1$.


$$\frac{V_c}{L} = 2j\omega A_1$$

$$A_1 = \frac{V_c}{2j\omega L} = \frac{10}{2j \times 9.95 \times 10^3 \times 0.005} = \frac{0.201}{2j} \text{ A}$$


The $2j$ term is eliminated that from the sin function

$$i(t) = 0.201 \exp(-10^3 t) \sin(9.95 \times 10^3 t) \text{ A}$$

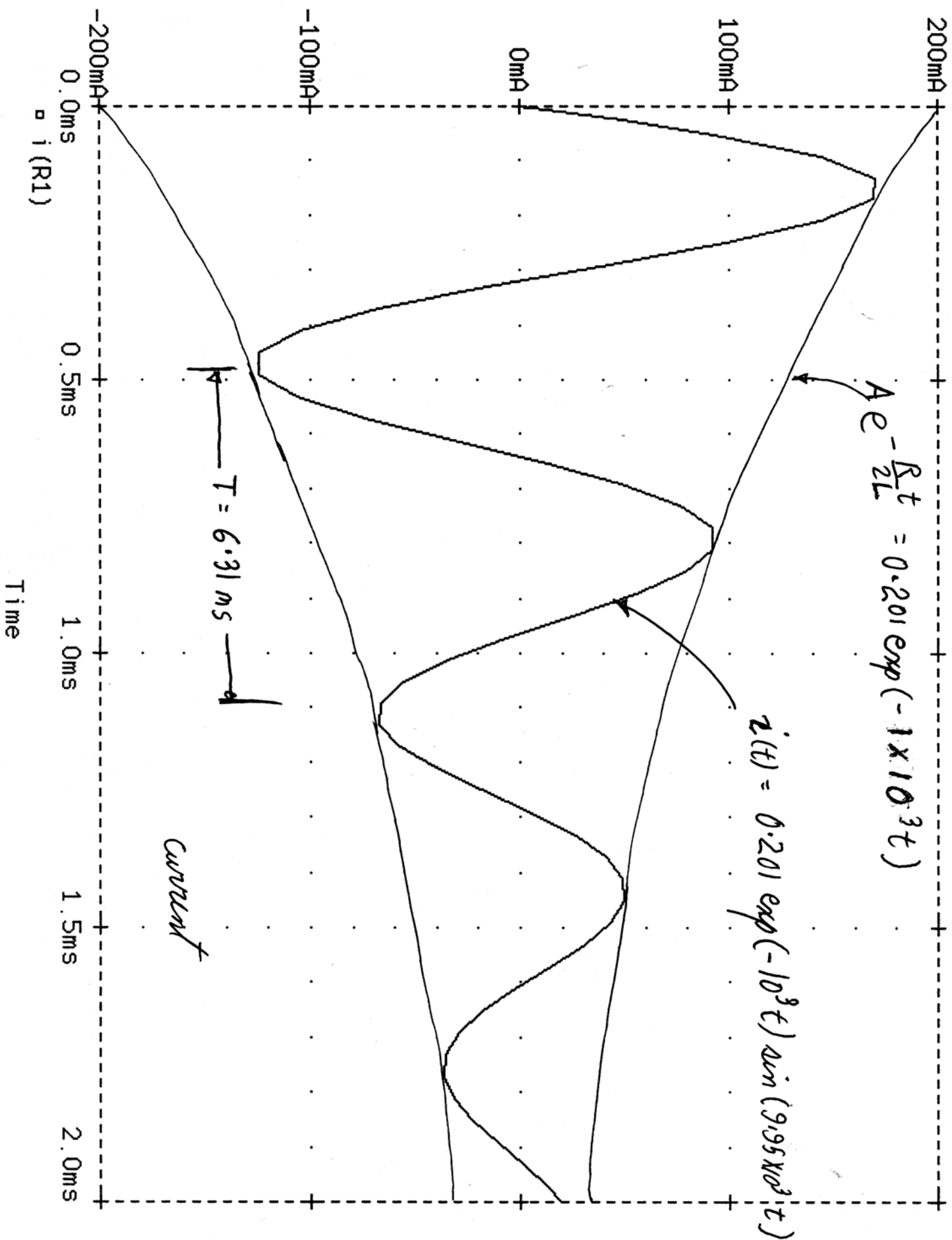* Simple RLC circuit, underdamping, C charged initially
 Date/Time run: 02/27/92 02:12:44 Temperature: 27.0



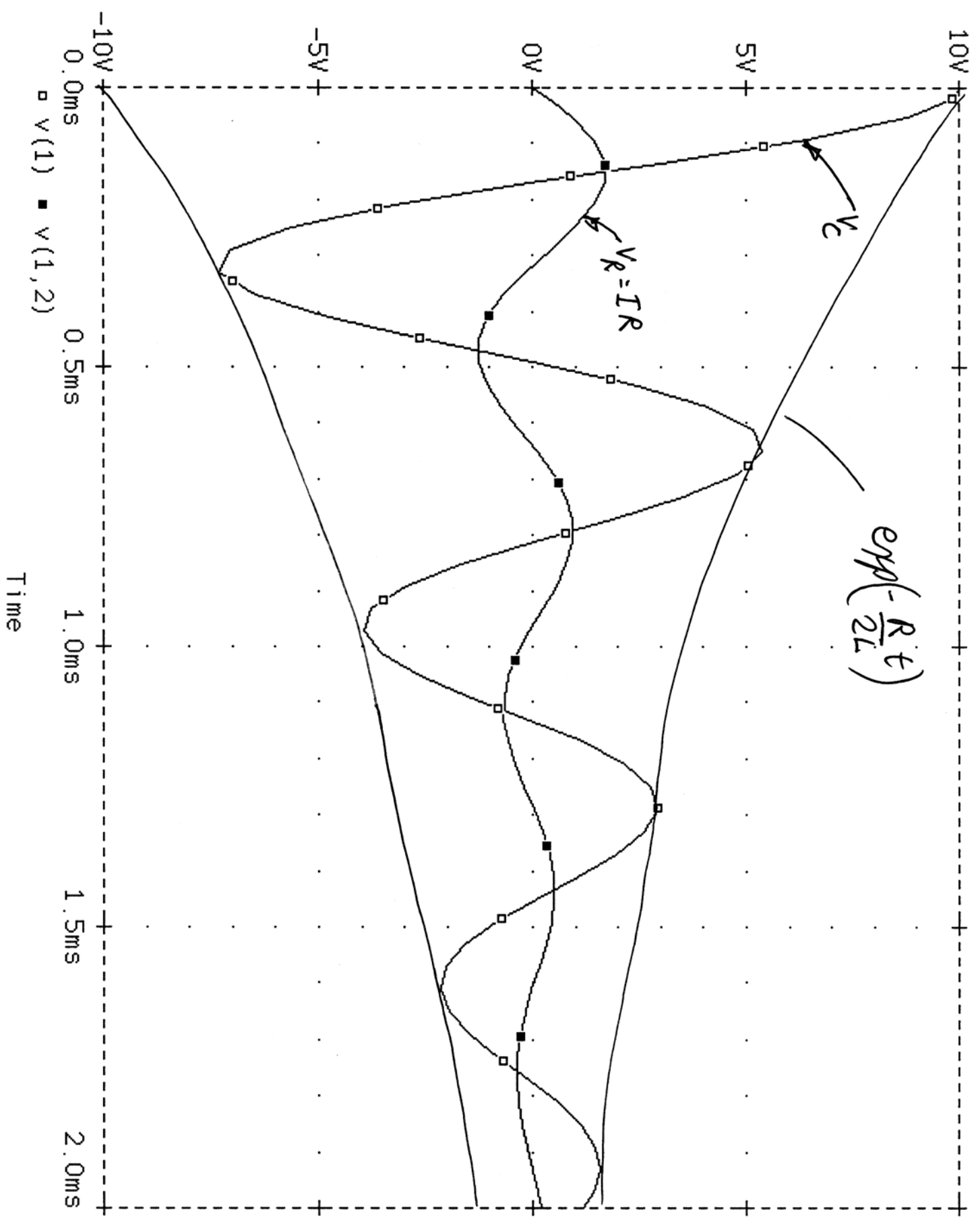* Simple RLC circuit, underdamping, C charged initially
Date/Time run: 02/24/92 11:04:43 Temperature: 27.0



* Simple RLC circuit, underdamping, C charged initially
Date/Time run: 02/24/92 11:04:43 Temperature: 27.0

