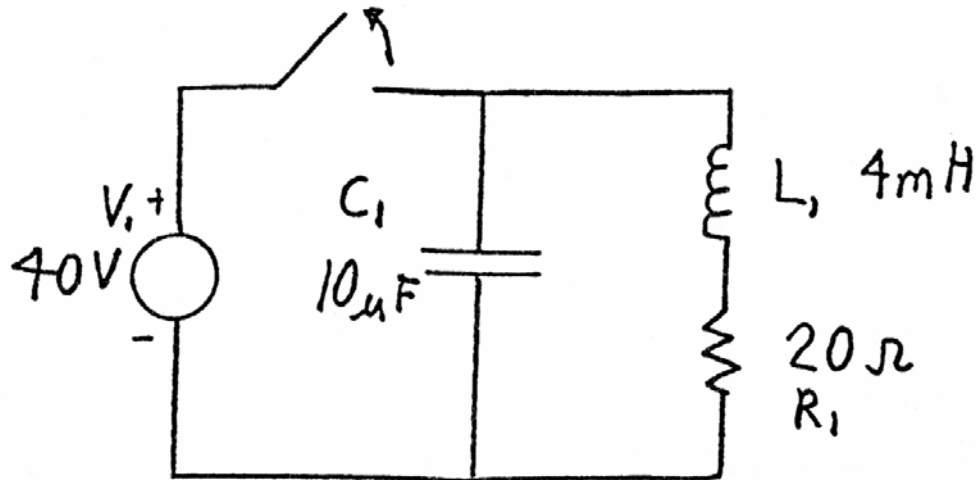


RLC Exam like Example

Consider this circuit where the switch has been closed long enough for the circuit to stabilize. Then open switch at $t=0$.



- (a) Write the DE for circuit & initial conditions (current or voltage across each element).
- (b) Solve DE for I through R_1
- (c) What type of damping does this have? What R_1 is needed for the other damping types?
- (d) For the (c) which is underdamped what is the 3 natural freq., damped freq. and damping factor?

(a) Using KVL

$$L \frac{di}{dt} + iR + \frac{1}{C} \int i \cdot dt = 0$$

• Differentiating

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

RLC Example Cont'd

- Initial conditions, C is fully charged, acts a V source

$$C \text{ has } V_C = 40V$$

- L acts as a short before switch opens (no change in I)
- Therefore, current controlled by R


$$I_L = I_R = \frac{V}{R} = \frac{40}{20} = 2A$$

$$V_L = 0, V_R = IR = 40V$$

- (b) Assuming an exponential solution then get the equations

$$I(t) = Ae^{st}$$

$$0 = s^2L + sR + \frac{1}{C}$$

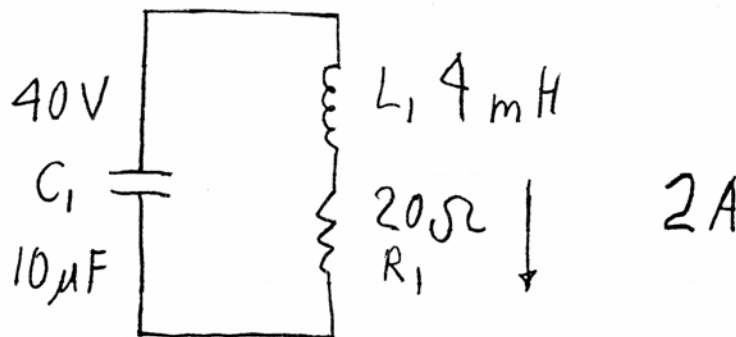

RLC Example Cont'd

- Solving this quadratic

$$0 = s^2 + s \frac{R}{L} + \frac{1}{CL}$$

- The roots are

$$s = \frac{R}{2L} \pm \left[\left(\frac{R}{2L} \right)^2 - \frac{1}{LC} \right]^{\frac{1}{2}}$$


$$\frac{R}{2L} = \frac{20}{2 \times 4 \times 10^{-3}} = 2.5 \times 10^3 \text{ sec}^{-1}$$

$$\frac{1}{LC} = \frac{1}{4 \times 10^{-3} \times 10^{-5}} = 2.5 \times 10^7 \text{ sec}^{-2}$$

- Thus the discriminant

$$\left[\left(\frac{R}{2L} \right)^2 - \frac{1}{LC} \right] = \left[(2.5 \times 10^3)^2 - 2.5 \times 10^7 \right] = -1.875 \times 10^7 \text{ sec}^{-2}$$

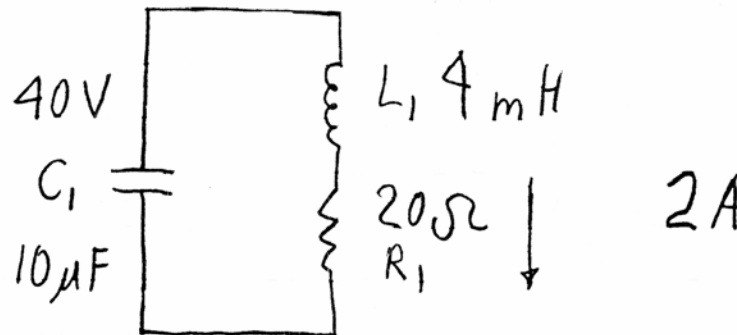- Because the discriminant is negative.
- This is an underdamped solution



RLC Example Cont'd

- Underdamped solved using ' α , ω ' form

$$\alpha = \frac{R}{2L} = 2.5 \times 10^3 \text{ sec}^{-1}$$

$$\omega_n^2 = \frac{1}{LC} = 2.5 \times 10^7 = 5000 \text{ rad} / \text{sec}$$

$$\therefore \omega^2 = \omega_n^2 - \alpha^2 = 2.5 \times 10^7 - 6.25 \times 10^6 = 1.875 \times 10^7$$

$$\omega = 4.33 \times 10^3$$

- Thus the solution will be of the form

$$i(t) = e^{-\alpha t} [A_1 e^{j\omega t} + A_2 e^{-j\omega t}]$$

- At $t = 0$, $I = 2A$

$$i(0) = e^0 [A_1 e^0 + A_2 e^0] = A_1 + A_2$$

$$A_1 + A_2 = 2A$$

RLC Example Cont'd

- As 2nd order also need the derivative at $t = 0$

$$L \frac{di}{dt} + I_0 R = V_C$$

$$L \frac{di}{dt} = V_C - I_0 R = 0$$

$$\frac{di}{dt} = 0$$

$$\therefore \frac{di(0)}{dt} = -\alpha e^{-\alpha t} [A_1 e^{j\omega t} + A_2 e^{-j\omega t}] + e^{\alpha t} [j\omega A_1 e^{j\omega t} - j\omega A_2 e^{-j\omega t}]$$

$$= -\alpha [A_1 + A_2] + j\omega [A_1 - A_2] = 0$$

$$\therefore j\omega [A_1 - A_2] = -\alpha [A_1 + A_2]$$

$$A_1 - A_2 = \frac{-\alpha}{j\omega} [A_1 + A_2] = j \frac{2.5 \times 10^3}{4.33 \times 10^3} [2]$$

- Thus

$$A_1 + A_2 = 2$$

$$A_1 - A_2 = j1.155$$

RLC Example Cont'd

- Adding

$$2A_1 = 2 + j1.155$$

$$A_1 = 1 + j0.577$$

- Subtracting

$$2A_2 = 2 - j1.155$$

$$A_2 = 1 - j0.577$$

$$\therefore i(t) = e^{-\alpha t} \left\{ \underbrace{\left[e^{j\omega t} + e^{-j\omega t} \right]}_{2 \cos \omega t} + 0.577j \underbrace{\left[e^{j\omega t} - e^{-j\omega t} \right]}_{2 \sin \omega t} \right\}$$

$$i(t) = e^{-2500t} [2 \cos \omega t + 1.155 \sin \omega t]$$

- Alternate solution - assume

$$i(t) = Ae^{-\alpha t} \cos(\omega t + \theta)$$

- At $t = 0$

$$A \cos \theta = 2$$

$$A = \frac{2}{\cos \theta}$$

RLC Example Cont'd

$$\frac{di}{dt} = -\alpha e^0 \cos \theta - \omega e^0 \sin \theta$$

$$= -\alpha \cos \theta - \omega \sin \theta = 0$$

$$\cos \theta = -\frac{\omega}{\alpha} \sin \theta$$

$$\frac{\sin \theta}{\cos \theta} = \tan \theta = -\frac{\alpha}{\omega}$$

$$\theta = \tan^{-1}(-0.577) = -30^\circ$$

$$A = \frac{2}{\cos(-30^\circ)} = 2.31$$

$$\therefore i(t) = 2.31e^{-2500t} \cos(\omega t - 30^\circ)$$

(c) This was underdamped, for critical damping

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$$

thus

$$R = \left(\frac{(2L)^2}{LC}\right)^{\frac{1}{2}} = \left(\frac{4L}{C}\right)^{\frac{1}{2}} = \left(\frac{8 \times 10^{-3}}{10^{-5}}\right)^{\frac{1}{2}}$$

$$R = 40\Omega$$

- For overdamped needs $R_1 > 40\Omega$ - say 60Ω
- Thus

$$\alpha = \frac{R}{2L} = 7.5 \times 10^3 \text{ sec}^{-1}$$

- Thus the discriminate

$$\left[\left(\frac{R}{2L} \right)^2 - \frac{1}{LC} \right] = \left[(7.5 \times 10^3)^2 - 2.5 \times 10^7 \right] = 3.125 \times 10^7$$

- Thus the solution is

$$s_1 = \alpha + \sqrt{3.125 \times 10^7} = 13090 \text{ sec}^{-1}$$
$$s_2 = \alpha - \sqrt{3.125 \times 10^7} = 1909 \text{ sec}^{-1}$$
$$i(t) = \left[A_1 e^{-13090 t} + A_2 e^{-1909 t} \right]$$