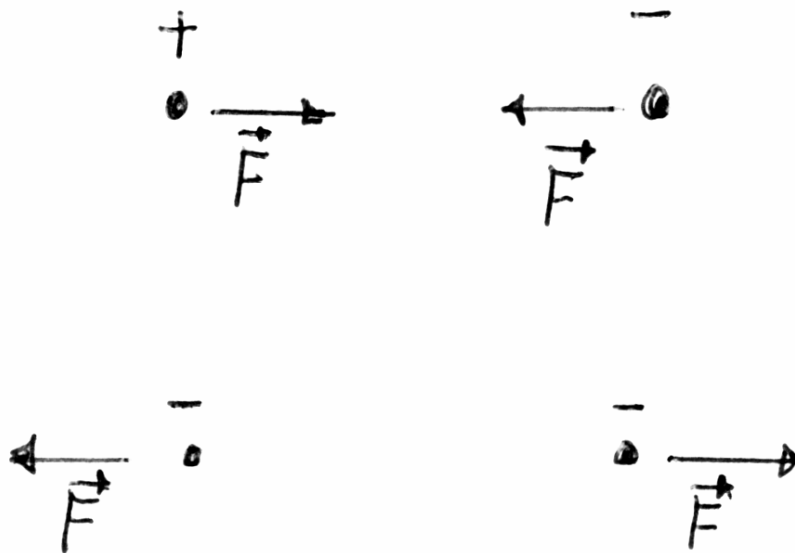


## Review of Current, Voltage & Resistance: Lesson 2

### Electrons and Charges (EC 1)

- Electricity is concerned with the flow of charged particles
- Basic particle: the Electron: negatively charged
- Electron charge:  $q = -e = 1.602 \times 10^{-19} \text{ C}$  (Coulombs)
- Mass of an electron  $m_e = 9.1 \times 10^{-31} \text{ kg}$
- Like charges repel each other
- Unlike charges attract
- Electrons attracted by Positive, repelled by Negative charges




## Electric Fields

- Electric Field ( $\vec{E}$ ): The Force applied to a unit charge
- E is a vector quantity: has a direction and magnitude
- Units are N/C (Newtons per Coulomb)
- Positive charges move in the same direction as the E field
- Negative charges move: opposite direction to the E field
- The force on a charge is:

$$\vec{F} = q\vec{E}$$

Where q = the charge

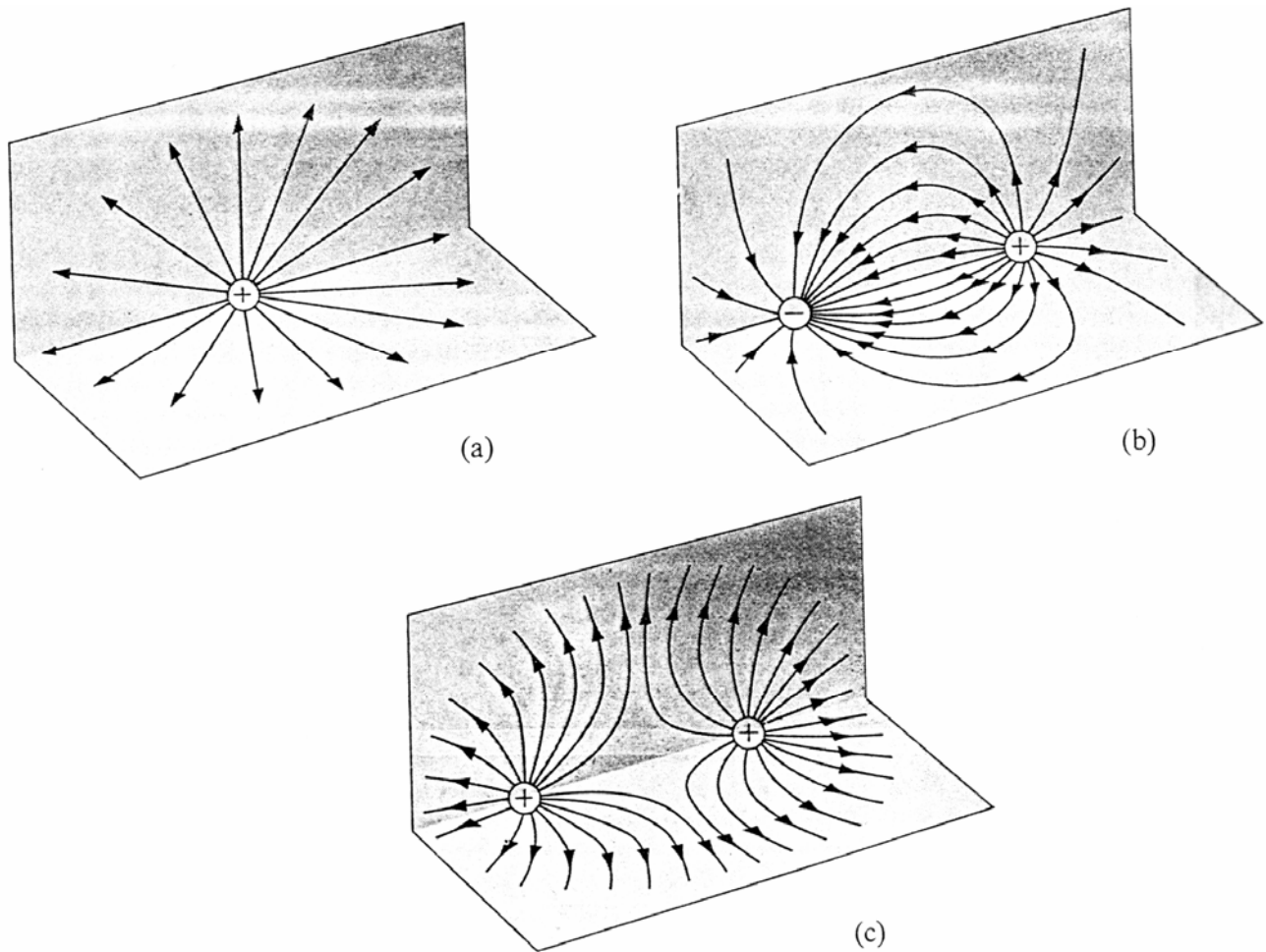

**Fig. 25-8.** The mapping of an electric field with the aid of lines of force.

## Charges and Current (EC 1)


- Electricity: the flow of charges within a confined volume
- Consider a wire with lots of free electrons
- An applied Electric field produces a flow of the electrons
- Electrons flow in the opposite direction of the E field
- Current (I): the rate of positive charge particle flow
- Units of Current: Amperes
- 1 Ampere = 1 Coulomb of charge passing a given point per second

$$I = \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$

where

q = charge in coulombs

t = time in seconds

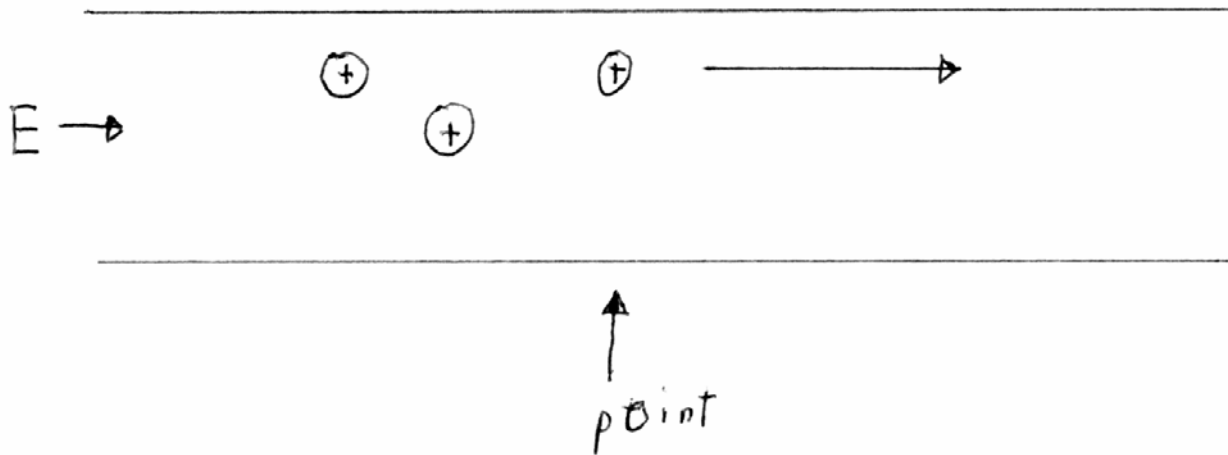

## Current in a Wire

- Often current is calculated using the charge density
- Then the current is:

$$I = nqA\mu$$


Where

$n$  = Charge density: charged particles per unit volume ( $\text{cm}^3$ )

$\mu$ : Velocity of the charges ( $\text{cm}/\text{sec.}$ )

$A$ : Area of the wire ( $\text{sq.cm}$ )

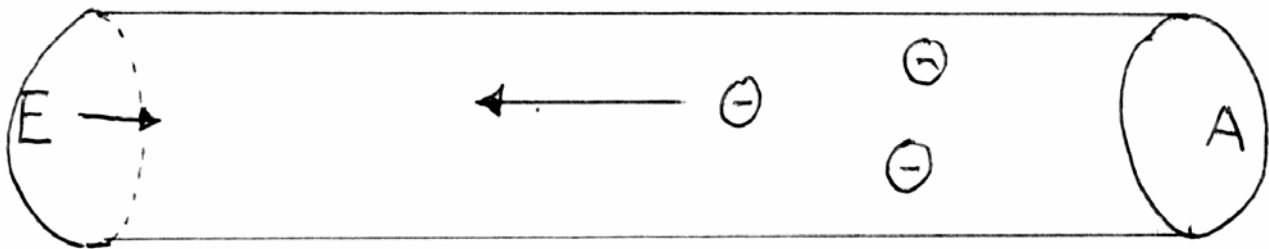- For copper  $n \sim 10^{22} \text{ cm}^{-3}$   
 $\mu \sim 9 \times 10^{-4} \text{ cm/s}$
- Takes 18.5 minutes for electrons to cross 1 cm in copper!
- Electron velocity is slow but signal travels near speed of light
- Reason: all the electrons move at same time
- Since  $q = -e$  (negative charge)
- Hence current direction is **OPPOSITE** the flow of electrons



## Positive & Negative Charge Currents

- Metals have only electron flow
- In Transistors/diodes (semiconductors) both positive and negative charges flow
- For both charge flow

$$I = (n_e e v_e + n_p e v_p) A$$

Where

$n_e$  = electron density ( $\text{cm}^{-3}$ )

$n_p$  = positive charge density ( $\text{cm}^{-3}$ )


$v_e$  = electron velocity ( $\text{cm/s}$ )

$v_p$  = positive charge velocity ( $\text{cm/s}$ )

$A$  = area of conductor ( $\text{cm}^2$ )

- NOTE: negative electron charge is cancelled by negative direction of current.
- The differential form is:
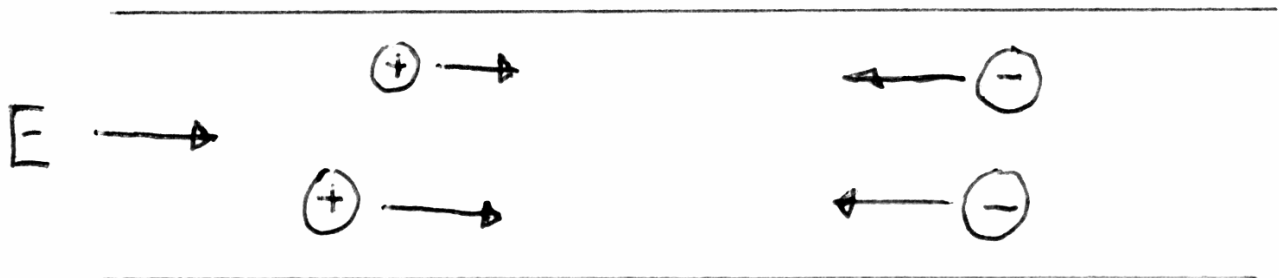
$$\frac{dI}{dx} = e \left( \frac{dn_e}{dt} + \frac{dn_p}{dt} \right) A$$



## Voltage

- Voltage: potential of an electric system to do work
- Voltage: is a "scalar" measured between two points
- Voltage: Work done moving a unit charge between 2 points

$$V_{AB} = \frac{\text{Work moving } e \text{ from } A \text{ to } B}{q} = \frac{dW}{dq}$$


where

$W$  = Work moving  $q$  from  $A$  to  $B$  in Joules

$q$  = charge in coulombs

- Work done on charge  $q$  accelerated through voltage  $V$ :

$$W = qV$$

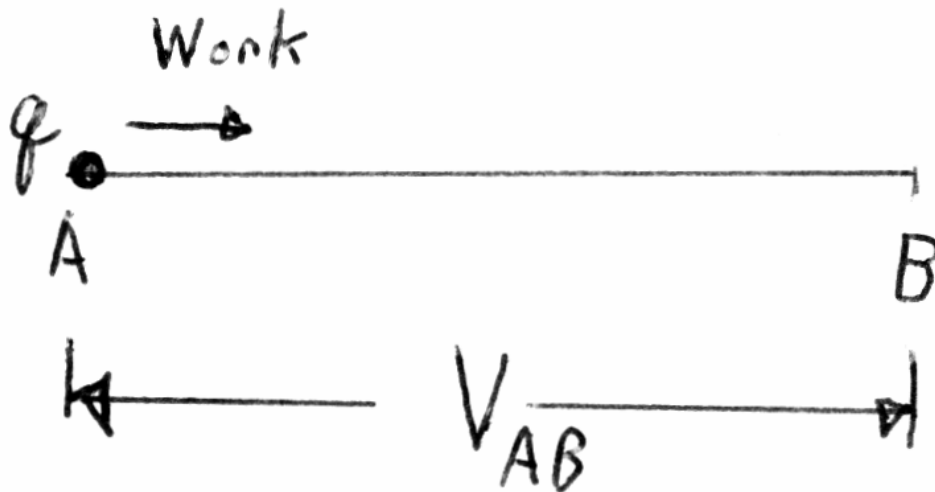

## Voltage and Electric Fields

- Electric fields are often given in Volts per metre (V/m)
- Derived from:

$$W = Fd = qEd = Vq$$

where


F = force in Newtons

d = distance in metres

E = Electric field (V/m)

Thus:

$$\vec{E} = \frac{V}{d}$$

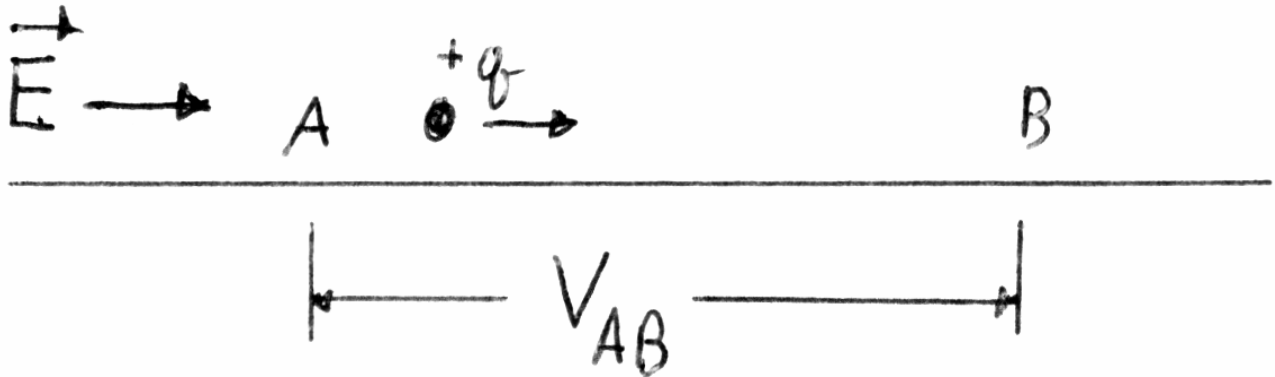

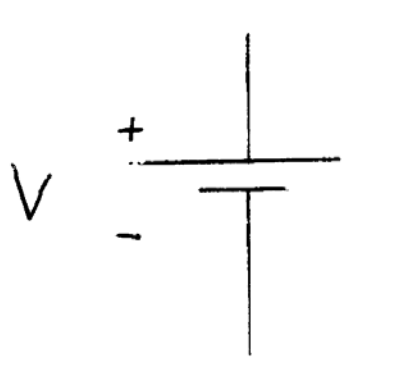
## Voltage Sources

- Voltage source has a positive & negative terminal
- Creates Electric Field in material between terminals
- Ideal Voltage source creates a specific, pure voltage
- Ideal source creates that voltage at all times



- Battery is a nearly a pure source (but not quite)
- Has finite internal resistance
- Hence batteries get hot when shorted




- Polarity: identification of which terminal is positive
- Long bar is positive terminal



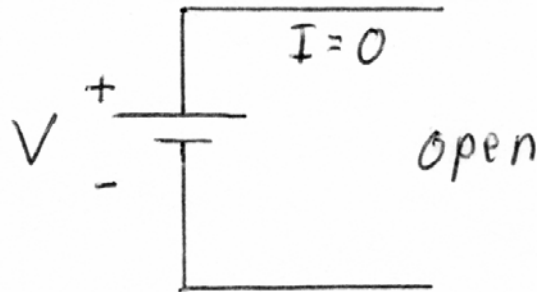
## Circuits & Current Directions

- Circuit: when the terminals of a voltage source are connected through some conducting element.
- Open circuit: when no current flows  
Infinite resistance path



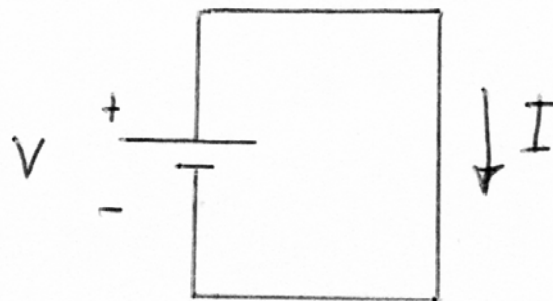- Short circuit: terminals directly connected to each other
- Perfect short circuit sets voltage to zero across it  
Zero resistance between paths
- Cannot have a perfect short on an ideal voltage source!



- Current  $\vec{I}$  is a vector quantity: has magnitude & direction
- Current shown coming out of positive terminal
- Original error (from 1700's):  
assumed current flow was positive charges
- Thus actual electron (neg charge) flow is into positive terminals

## Power

- Power loss: energy dissipated in a device per unit time


$$P = \frac{dW}{dt} = \frac{dW}{dq} \frac{dq}{dt} = VI$$

Since:

$$V = \frac{dW}{dq} \quad \text{and} \quad I = \frac{dq}{dt}$$



- Units of power = Watts (W) = Joules/sec
- Total work done is

$$W = \int P(t) dt = \int V(t) I(t) dt$$

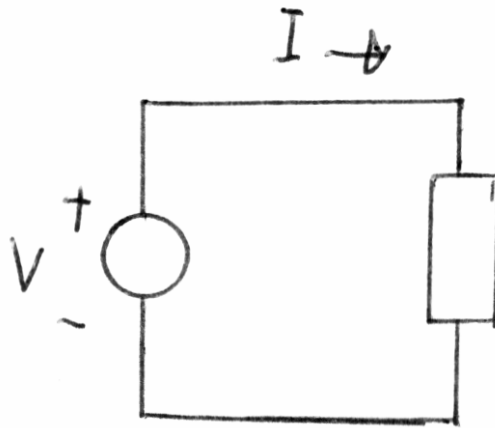
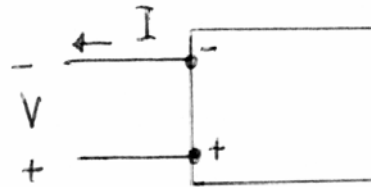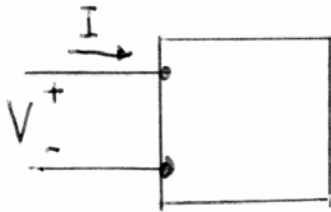
## Basic Circuit Elements

- Basic Circuit Element: has two lines entering it
- Terminals: places where circuit current/voltage applied
- Simple elements 2 terminal devices
- Complicated elements have 3 or more terminals: eg. Transistor
- Devices may be either: a load element or source element





- **Load element:** consumes power
- When voltage applied, get current flow
- When current applied, get voltage across it
- Current flows into positive terminal or out negative

**Active (source) element:** Power source: supplies energy

$$P = -VI$$

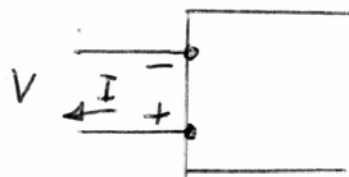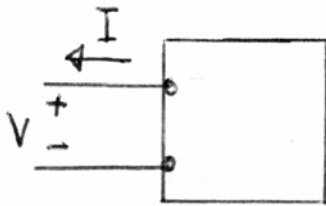- Power is negative: ie supplied
- Current flows out of the positive terminal
- or current flows into the negative terminal



## Unit Prefixes

- Standard Systems International (SI) prefixes
- Note: while SI units are meters usually use cm in electronics

**Table 1-3 Standard Decimal Prefixes**

Multiplier	Prefix	Abbreviation	Pronunciation
$10^{12}$	tera	T	těr' à
$10^9$	giga	G	ji' gá
$10^6$	mega	M	měg' à
$10^3$	kilo	k	kil' ò
$10^2$	hecto	h	hěk' tō
$10^1$	deka	da	děk' à
$10^{-1}$	deci	d	děs' ĭ
$10^{-2}$	centi	c	sěn' tĭ
$10^{-3}$	milli	m	mĭl' ĭ
$10^{-6}$	micro	$\mu$	mĭ' krō
$10^{-9}$	nano	n	nān' ò
$10^{-12}$	pico	p	pē' cō
$10^{-15}$	femto	f	fēm' tō
$10^{-18}$	atto	a	ăt' tō

## Constant Voltage and Current Sources & Nodes (EC2)

- There are two types of Ideal power source:
- Constant Current & Constant Voltage
- **Constant Voltage** always produces that voltage output  
When off acts like a short circuit




- **Constant Current** always produces that current output
- When off acts like an open circuit  $R \rightarrow \infty$



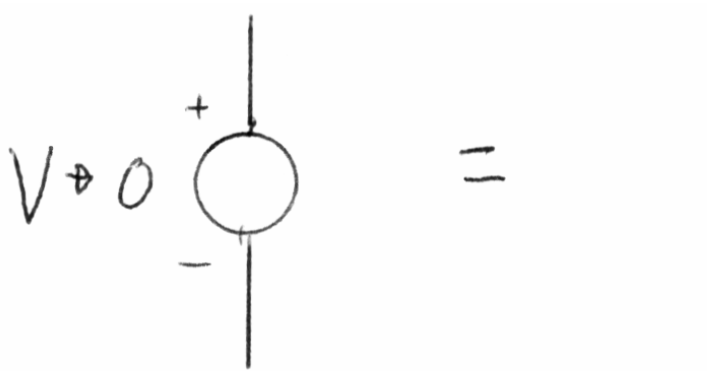
## Turning off Current & Voltage Sources

- Voltage source is turned off when output is 0 V
- This means it acts like a perfect short circuit
- Hence turn off voltage source: replaced by a short



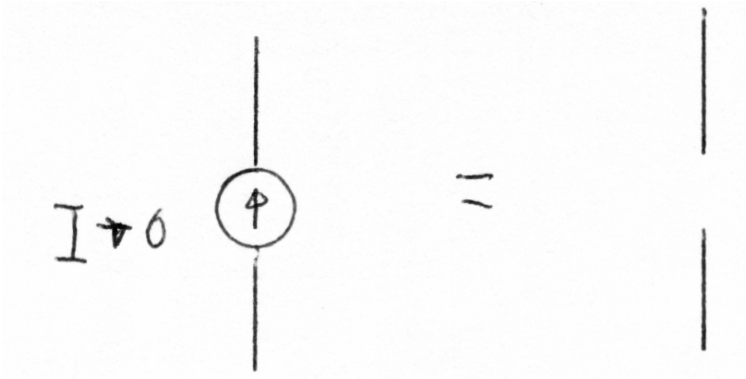- Current source is turned off when output = 0 A
- This means it acts like a perfect open circuit
- Hence turn off current: replaced by an open



## Ideal Dependent Current & Voltage Sources

- **Dependent Sources:**


V or I is a function of values across others devices

- Dependent voltage source follows a relationship
- Voltage dependent voltage source

$$v_s = \mu v_x$$

where:  $\mu$  = dimensionless multiplier


- MOS transistor behaves like this

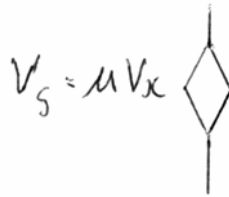


- Current dependent voltage source

$$v_s = \rho i_x$$

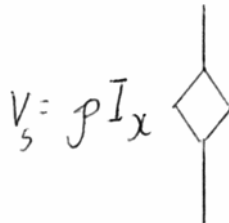where:  $\rho$  = multiplier: units Volt/Amp



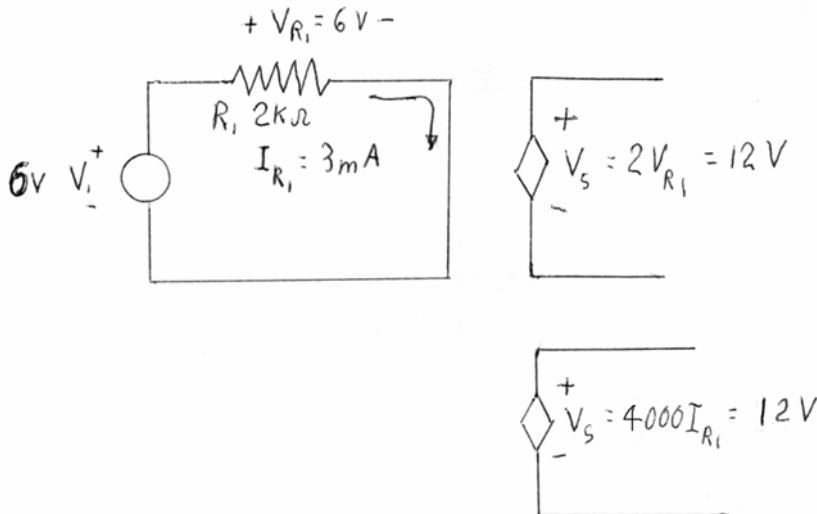- Eg. Dependent voltage source with  $V = 2$  times  $R_1$  voltage




## Ideal Dependent Current Sources

- Dependent current source follows the relationships
- Voltage dependent current source

$$i_s = \alpha v_x$$

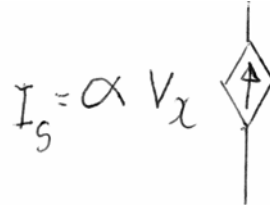where:  $\alpha$  = multiplier: units Amp/Volt




- Current dependent current source




$$i_s = \beta i_x$$

where:  $\beta$  = dimensionless multiplier

- Bipolar transistor acts like this

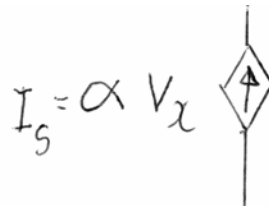

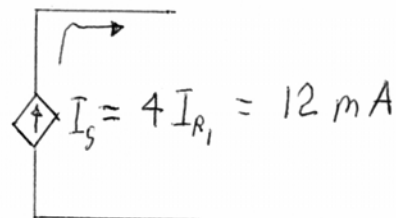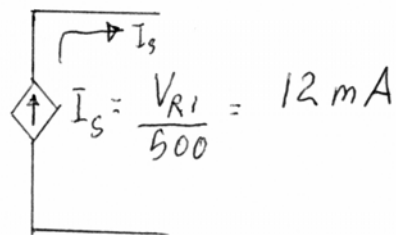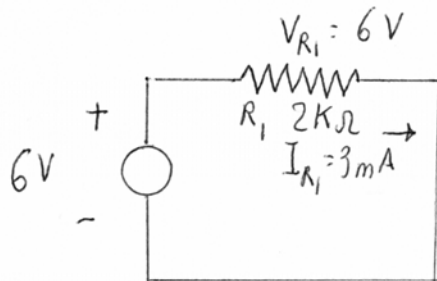
- Eg. Dependent current source with  $I = 4$  times  $R_1$  current




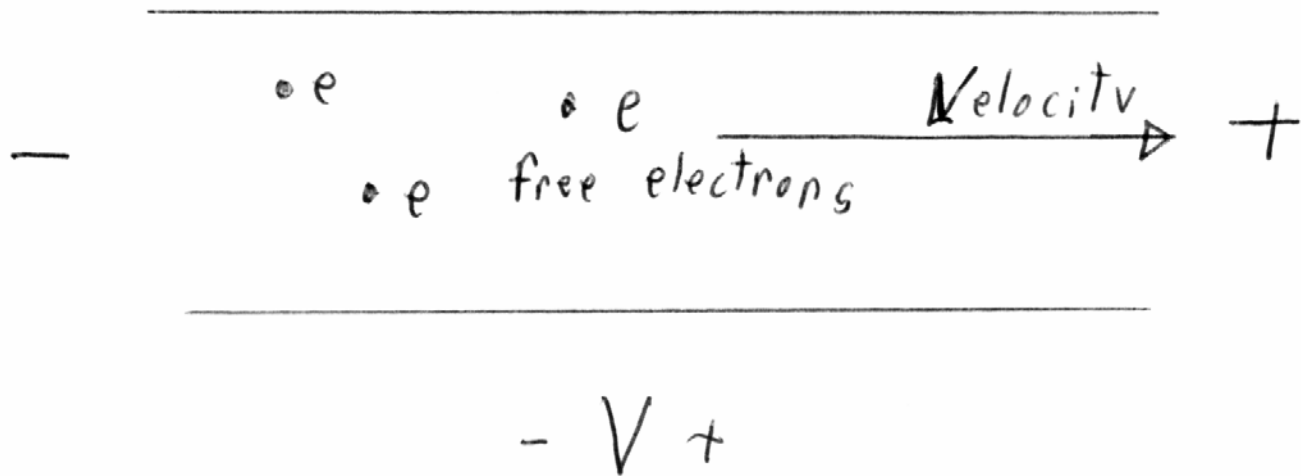
## Conductors, Insulators & Resistors (EC 2)

- Conductor has surplus of free charges, usually electrons
- Current flows:  
when an Electric field applied across a conductors
- Insulators have few free charges
- Typically  $10^{10}$ - $10^{20}$  higher resistance than conductors
- Almost no current flows when voltage applied
- But hard to get no current at all



## Insulators & Resistors

- Recall that the current is given by

$$I = nqA\mu$$

Where


$n$  = number of charges

$q$  = charge on the particle (electron)

$A$  = area of the conductor

$\mu$  = velocity of the charges

- Materials vary widely in the number of free charges
- Free charges are those not tied to atoms
- Metals have many free electrons  $\sim 10^{22} \text{ cm}^{-3}$
- Velocity of the charges is limited by the atoms
- Electrons "hit" an atom and are slowed down.
- Then reaccelerated by the electric field
- Collision with the atom cause a loss of energy
- Appears as heating of conductor
- Loss of energy creates a Resistance to current flow

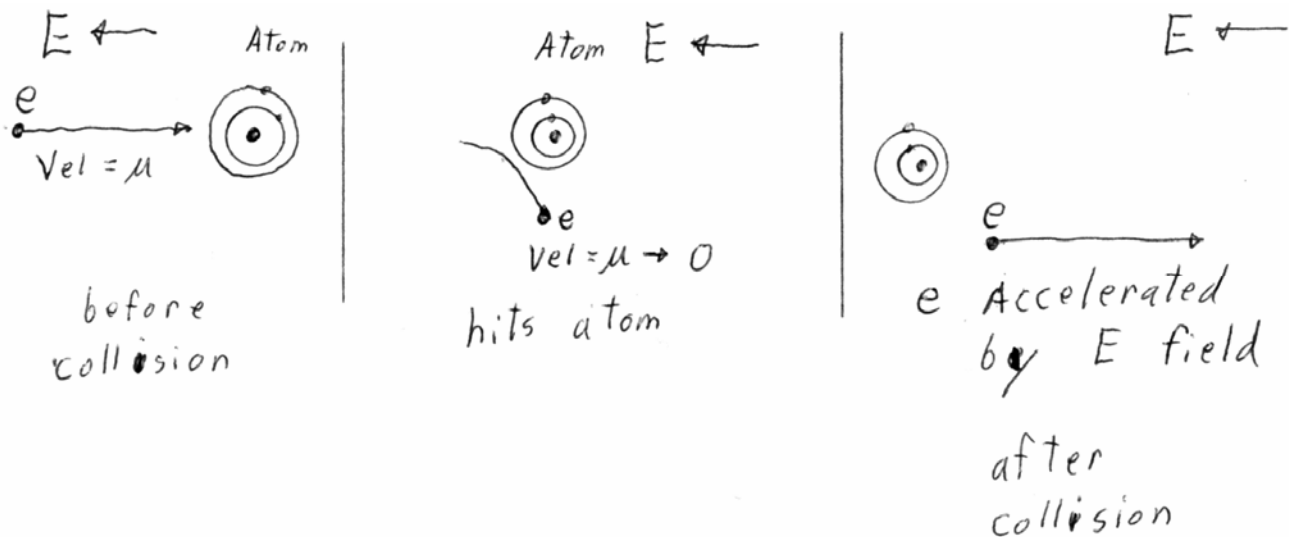

## Resistors (EC2)

- Resistors: cause energy loss from resistance to current flow
- Resistors are made up of materials that are poor conductors
- **Ohm's law**

$$R = \frac{dV}{dI}$$

where:

R = resistance in ohms  $\Omega$


I = current in Amperes A

V = voltage in volts V

or for simple resistors:

$$V = IR \quad \text{or} \quad R = \frac{V}{I} \quad \text{or} \quad I = \frac{V}{R}$$

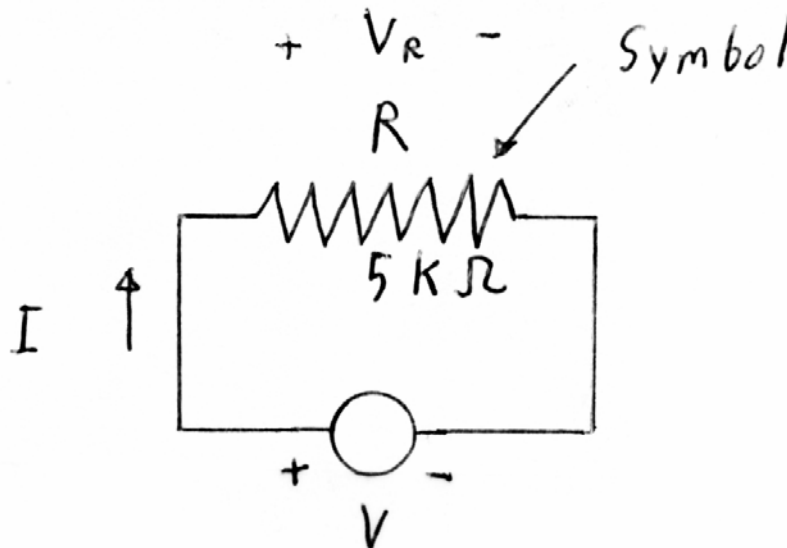- Thus resistors give a voltage drop across the device from current



## Power and Resistors

- Recall Power loss: energy dissipated in a device per unit time

$$P = \frac{dW}{dt} = \frac{dW}{dq} \frac{dq}{dt} = VI$$

- Recall Ohm's law


$$V = IR \quad \text{or} \quad R = \frac{V}{I} \quad \text{or} \quad I = \frac{V}{R}$$

- Thus power in loss in resistors is

$$P = VI = I^2 R = \frac{V^2}{R}$$

- NOTE: power alters as V, I or R changes instantaneously
- Example: a 1 Kohm resistor carries 20 mA of current.  
What is the power loss:
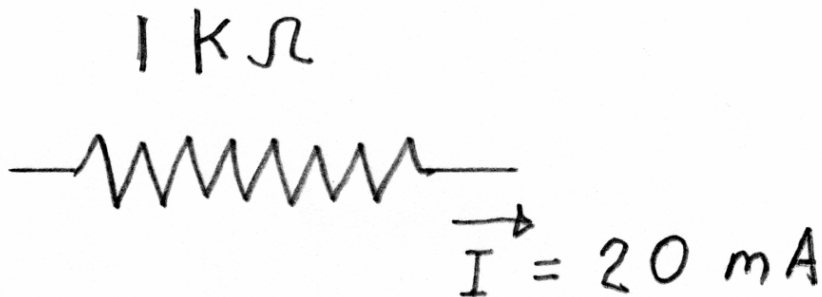
$$P = I^2 R = (0.02)^2 (1000) = 0.4W = 400mW$$



## Resistors and Resistivity

- Basic unit for resistive materials is their resistivity
- Resistivity  $\rho = \rho$  is related to resistance by

$$R = \frac{\rho L}{A}$$

where


$\rho$  = resistivity in ohm-cm =  $\Omega\text{cm}$

L = length of wire (cm)

A = cross-sectional area in  $\text{cm}^2$

- Typical values for copper is  $2 \times 10^{-6}$  ohm-cm =  $2 \mu\Omega\text{cm}$
- Typical insulators  $10^7$  to  $10^{22}$  ohm-cm
- Example a copper wire is 40 cm long by 1 sq mm cross section:  
what is the resistance?
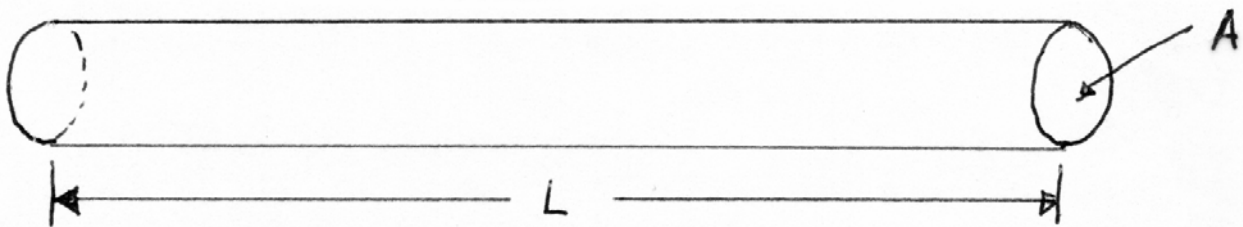
$$R = \frac{\rho L}{A} = \frac{2 \times 10^{-6} (40)}{(0.1)^2} = 0.008 \Omega$$



## Conductivity & Conductance

- For conductors often use the conductivity
- symbol sigma =  $\sigma$

$$\sigma = \frac{1}{\rho}$$



- Units are (ohm-cm)<sup>-1</sup>
- Conductance (G) is the inverse of resistance

$$G = \frac{1}{R}$$

- units are mhos (ohms spelled backwards) or Siemens

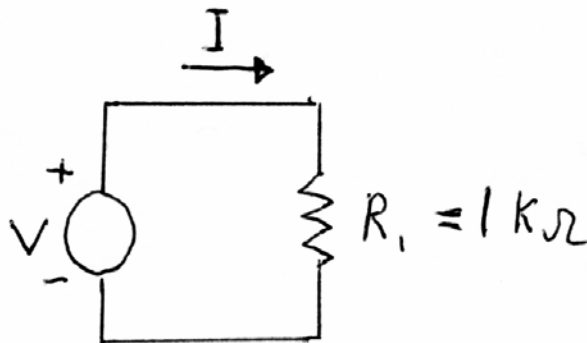
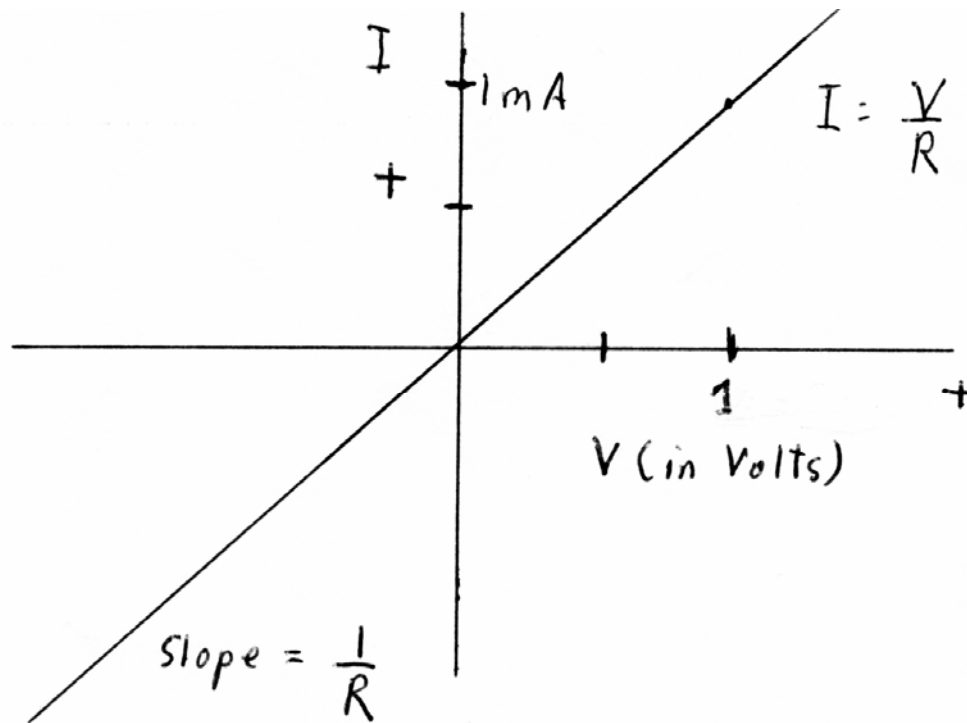
## I-V Characteristics of Resistors

- I-V curves characterize the operation of any electrical device.
- Also called V-I curves.
- Obtained by plotting current in device against the applied voltage between two terminals on the device
- In practice obtained using "curve tracers" or parametric analyzers


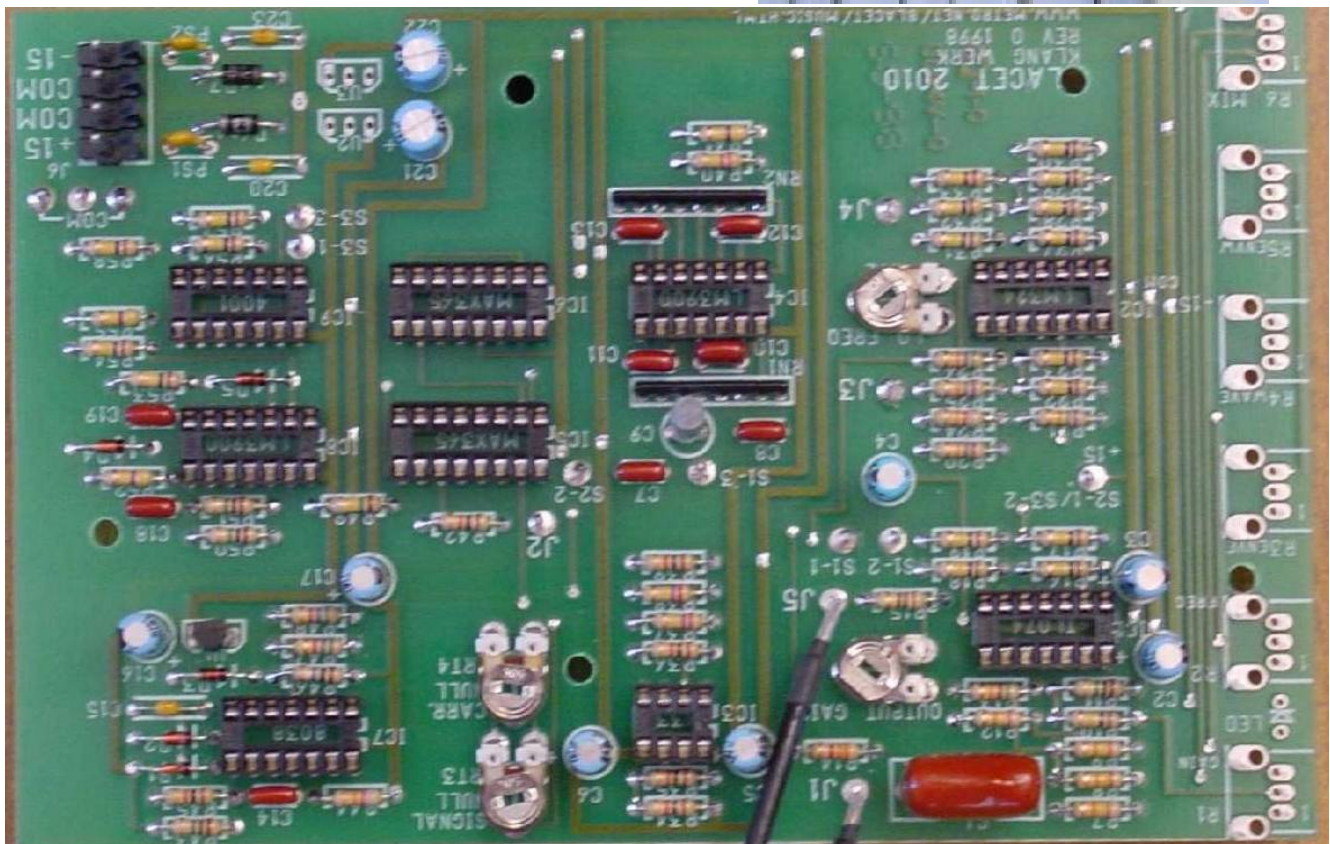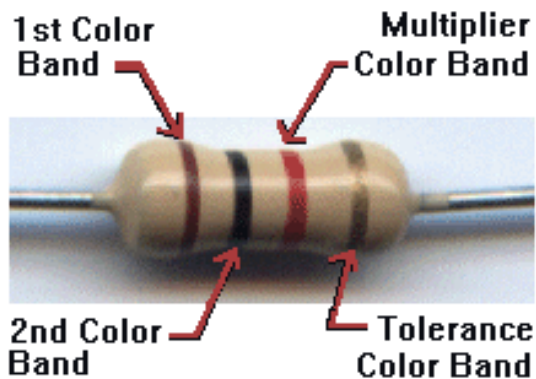
# Practical Resistors

- Resistor is the most widely used component
- Cost  $> \$0.01$  to  $> \$1$
- Provides way to control V or I values  
Feedback values in op-amp
- Low power resistors use a carbon film, plastic case
- High power are wire resistors
- Note hard to make high value resistors in microchips
- Often use external resistors
- Resistors are used created desired voltages or remove power





## Resistors and Power ratings

- Resistors are rated in terms of maximum power capability
- 1/4 W (most common), 1/2 W, 1 W, 2W, 5W are usual
- The larger surface area, the higher the power
- More surface area, faster heat loss
- Low power resistors have plastic surface
- High power resistors are ceramic
- Typically use a resistor rated for 2 times max power expected
- Thus less than 1/8 W power use 1/4 W resistors
  
- Example: a 1 Kohm resistor carries 20 mA of current.
- What is the size needed?
  
- As previously

$$P = I^2 R = 0.4W = 400mW$$

- Since max for 1/2 W resistor is 250 mW
- Thus want to use a 1 Watt resistor
- 1/2 W would work, but with very small safety range

