

ENSC 220 – Assignment #6 solution 2005

1.

$$\text{Let } Z_1 = 4 - j8 \Omega, \quad Z_2 = 2 + j10 \Omega$$

$$\text{Then } Z_1 // Z_2 = \frac{(4 - j8)(2 + j10)}{6 + j2} = \frac{88 + j24}{(6 + j2)} = \frac{(88 + j24)(6 - j2)}{40} = 14.4 - j0.8 \Omega$$

$$Z_3 = 20 \Omega, \quad Z_4 = -j10 \Omega$$

$$Z_3 // Z_4 = \frac{-j200}{20 - j10} = \frac{-j20}{2 - j1} = \frac{-j20(2 + j1)}{5} = 4 - j8 \Omega$$

$$Z_{ab} = 21.6 + j38.8 + 14.4 - j0.8 + 4 - j8 = 40 + j30 \Omega = 50/\underline{36.87^\circ} \Omega$$

2.

$$\begin{aligned} Y_1 &= \frac{1}{6 - j2} + \frac{1}{4 + j12} + \frac{1}{5} + \frac{1}{j10} = \frac{6 + j2}{40} + \frac{4 - j12}{160} + \frac{32}{160} - j\frac{16}{160} \\ &= \frac{24 + j8 + 4 - j12 + 32 - j16}{160} = \frac{60 - j20}{160} = \frac{3 - j1}{8} \end{aligned}$$

$$Z_1 = \frac{1}{Y_1} = \frac{8}{3 - j1} = 2.4 + j0.8$$

$$Z_{ab} = 13.6 - j12.8 + 2.4 + j0.8 = 16 - j12 = 20/\underline{-36.87^\circ}$$

$$Y_{ab} = \frac{1}{Z_{ab}} = 50/\underline{36.87^\circ} \text{ m}\mathcal{U} = 40 + j30 \text{ m}\mathcal{U}$$

3.

$$Z_1 = 30 + j0.25 \times 10^{-3}(40,000) = 30 + j10 \Omega$$

$$Z_2 = 20 - j\frac{10^6}{(40,000)(2.5)} = 20 - j10 \Omega$$

$$\mathbf{I}_g = 20/\underline{-73.74^\circ} \text{ A}$$

Let \mathbf{I}_C represent the current down through the capacitive branch. Then


$$\mathbf{I}_C = \frac{Z_1}{Z_1 + Z_2} \mathbf{I}_g = \frac{30 + j10}{50} (20/\underline{-73.74^\circ}) = 12.65/\underline{-55.31^\circ} \text{ A}$$

$$\mathbf{V}_o = 20\mathbf{I}_C = 252.98/\underline{-55.31^\circ} \text{ V}$$

$$v_o = 252.98 \cos(40,000t - 55.31^\circ) \text{ V}$$

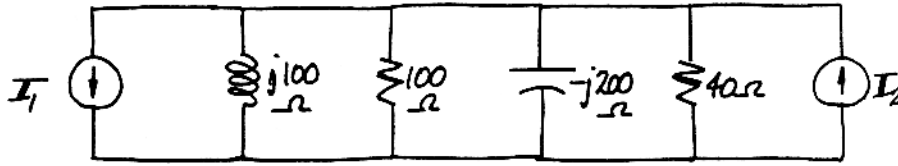4.

$$j\omega L = j5000(20 \times 10^{-3}) = j100 \Omega; \quad \frac{1}{j\omega C} = \frac{10^6}{j5000} = -j200 \Omega$$




$$I_1 = \frac{400/36.87^\circ}{j100} = 4/-53.13^\circ = 2.4 - j3.2 \text{ A}$$

$$I_2 = \frac{128/-90^\circ}{40} = 3.2/-90^\circ = -j3.2 \text{ A}$$

$$Y = \frac{1}{j100} + \frac{1}{100} + \frac{1}{-j200} + \frac{1}{40} = \frac{-j2 + 2 + j + 5}{200} = \frac{7 - j1}{200}$$
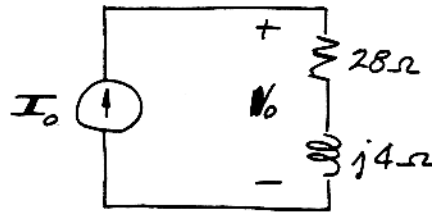
$$Z = \frac{200}{7 - j1} = \frac{200}{50}(7 + j1) = 28 + j4 \Omega$$



$$I_o = I_2 - I_1 = -j3.2 - 2.4 + j3.2 = -2.4 = 2.4/180^\circ$$

$$V_o = (28 + j4)I_o = (28.28/8.13^\circ)(2.4/180^\circ) = 67.88/188.13^\circ$$

$$v_o = 67.88 \cos(5000t + 188.13^\circ) \text{ V} \quad \text{or} \quad v_o = 67.88 \sin(5000t - 81.87^\circ) \text{ V}$$

5.

$$[a] H(s) = \frac{V_o}{V_i} = \frac{R}{sL + R + R_i} = \frac{(R/L)}{s + (R + R_i)/L}$$

$$[b] H(j\omega) = \frac{(R/L)}{\left(\frac{R+R_i}{L}\right) + j\omega}$$

$$|H(j\omega)| = \frac{(R/L)}{\sqrt{\left(\frac{R+R_i}{L}\right)^2 + \omega^2}}$$

$$|H(j\omega)|_{\max} \text{ occurs when } \omega = 0$$

$$[c] |H(j\omega)|_{\max} = \frac{R}{R + R_l}$$

$$[d] |H(j\omega_c)| = \frac{R}{\sqrt{2}(R + R_l)} = \frac{R/L}{\sqrt{\left(\frac{R+R_l}{L}\right)^2 + \omega_c^2}}$$

$$\therefore \omega_c^2 = \left(\frac{R + R_l}{L}\right)^2; \quad \therefore \omega_c = (R + R_l)/L$$

$$[e] \omega_c = \frac{1575}{0.25} = 6300 \text{ rad/s}$$

$$H(j\omega) = \frac{6000}{6300 + j\omega}$$

$$H(j0) = 0.9524$$

$$H(j6300) = \frac{0.9524}{\sqrt{2}} \angle -45^\circ = 0.6734 \angle -45^\circ$$

$$H(j1890) = \frac{6000}{6300 + j1890} = 0.9122 \angle -16.70^\circ$$

$$H(j18,900) = \frac{6000}{6300 + j18,900} = 0.3012 \angle -71.57^\circ$$

6.

$$[a] H(s) = \frac{V_o}{V_i} = \frac{R}{R + R_c + (1/sC)}$$

$$= \frac{R}{R + R_c} \cdot \frac{s}{[s + (1/(R + R_c)C)]}$$

$$[b] H(j\omega) = \frac{R}{R + R_c} \cdot \frac{j\omega}{j\omega + (1/(R + R_c)C)}$$

$$|H(j\omega)| = \frac{R}{R + R_c} \cdot \frac{\omega}{\sqrt{\omega^2 + \frac{1}{(R+R_c)^2 C^2}}}$$

The magnitude will be maximum when $\omega = \infty$

$$[c] |H(j\omega)|_{\max} = \frac{R}{R + R_c}$$

$$[d] |H(j\omega_c)| = \frac{R\omega_c}{(R + R_c)\sqrt{\omega_c^2 + [1/(R + R_c)C]^2}}$$

$$\therefore |H(j\omega)| = \frac{R}{\sqrt{2}(R + R_c)} \quad \text{when}$$

$$\therefore \omega_c^2 = \frac{1}{(R + R_c)^2 C^2}$$

$$\text{or } \omega_c = \frac{1}{(R + R_c)C}$$

$$[e] \omega_c = \frac{1}{(R + R_c)C} = \frac{10^9}{(50 \times 10^3)(2.5)} = 8000 \text{ rad/s}$$

$$H(j\omega_c) = \left(\frac{40}{50}\right) \frac{j8000}{8000 + j8000} = 0.5657/45^\circ$$

$$H(j0.1\omega_c) = \frac{(0.8)j800}{8000 + j800} = 0.0796/84.29^\circ$$

$$H(j10\omega_c) = \frac{(0.8)j80,000}{8000 + j80,000} = 0.7960/5.71^\circ$$

7.

$$[a] \omega_o^2 = \frac{10^3 \times 10^6}{(40)(0.25)} = 10^8, \quad \omega_o = 10^4 \text{ rad/s}$$

$$f_o = \frac{\omega_o}{2\pi} = \frac{5000}{\pi} = 1591.55 \text{ Hz}$$

$$[b] V_m = \frac{600}{25} \times 5 = 120 \text{ V}$$

$$[c] R_e = \frac{(20)(5)}{25} = 4 \text{ k}\Omega$$

$$Q = (10^4)(4 \times 10^3)(0.25 \times 10^{-6}) = 10$$

$$\beta = \frac{\omega_o}{Q} = \frac{10^4}{10} = 1000 \text{ rad/s}$$

$$[d] Q = 10$$

$$[e] \omega_1 = \omega_o \left[-\frac{1}{20} + \sqrt{\frac{1}{400} + 1} \right] = 9,512.49 \text{ rad/s}$$

$$\omega_2 = \omega_o \left[\frac{1}{20} + \sqrt{\frac{1}{400} + 1} \right] = 10,512.49 \text{ rad/s}$$

$$[f] Q(\text{with}) = 10$$

$$Q(\text{without}) = (10^4)(5000)(0.25 \times 10^{-6}) = 12.5$$

$$\therefore Q(\text{with}) = 0.80Q(\text{without})$$

8.

$$[a] \quad \omega_o^2 = \frac{10^3 \times 10^9}{(500)(5)} = \frac{10^{12}}{2500} = \frac{10^{10}}{25}$$

$$\omega_o = 20,000 \text{ rad/s} = 20 \text{ krad/s}$$

$$[b] \quad V_{m_o} = 50 \text{ V}$$

$$[c] \quad \mathbf{V}_o = \frac{\mathbf{V}_g(2000)}{Z} = \frac{(50/0^\circ)(2000)}{Z}$$

$$|\mathbf{V}_o| = \frac{(2000)(50)}{|Z|} = 0.80(50); \quad \therefore |Z| = 2500$$

$$2000 \left| 1 + jQ \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right) \right| = 2500$$

$$Q = \frac{\omega_o L}{R} = \frac{20 \times 10^3 (500 \times 10^{-3})}{2000} = 5$$

$$1 + 25 \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right)^2 = (1.25)^2$$

$$25 \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right)^2 = 0.5625$$

$$5 \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right) = \pm 0.75$$

$$\omega^2 - \omega_o^2 = \pm 0.15\omega\omega_o \quad \text{or} \quad \omega^2 \mp 3000\omega - 4 \times 10^8 = 0$$

$$\omega = \pm 1500 \pm \sqrt{2,250,000 + 4 \times 10^8} = \pm 1500 \pm 10^4 \sqrt{4.0225}$$
$$= \pm 1500 \pm 20,056.17$$

$$\omega_1 = 18,556.17 \text{ rad/s}; \quad \omega_2 = 21,556.17 \text{ rad/s}$$

$$\therefore 18,556.17 \leq \omega \leq 21,556.17 \text{ rad/s}$$