

Digital System Design

by

Dr. Lesley Shannon

Email: Ishannon@ensc.sfu.ca

Course Website: <http://www.ensc.sfu.ca/~Ishannon/courses/ensc350>



Simon Fraser University

Slide Set: 10

Date: March 4, 2009

Slide Set Overview

- Midterm
 - Results
 - Answers


What your marks mean in terms of your final mark

- 53.5 18%
- 47.5 16%
- 41.5 14%
- 35.5 12%
- 29.5 10%
- 24 8%
- 18 6%
- 12 4%
- 6 2%

How did everyone do

- The “bad” questions:
 - 1. & 4. were the worst
 - 2. & 3. weren't great =(
- Average
 - Mean: 38.22 (Std Dev: 11.53)
 - Median: 40
 - Mode: 41
 - Maximum: 60.5
 - Minimum: 15

How did everyone do

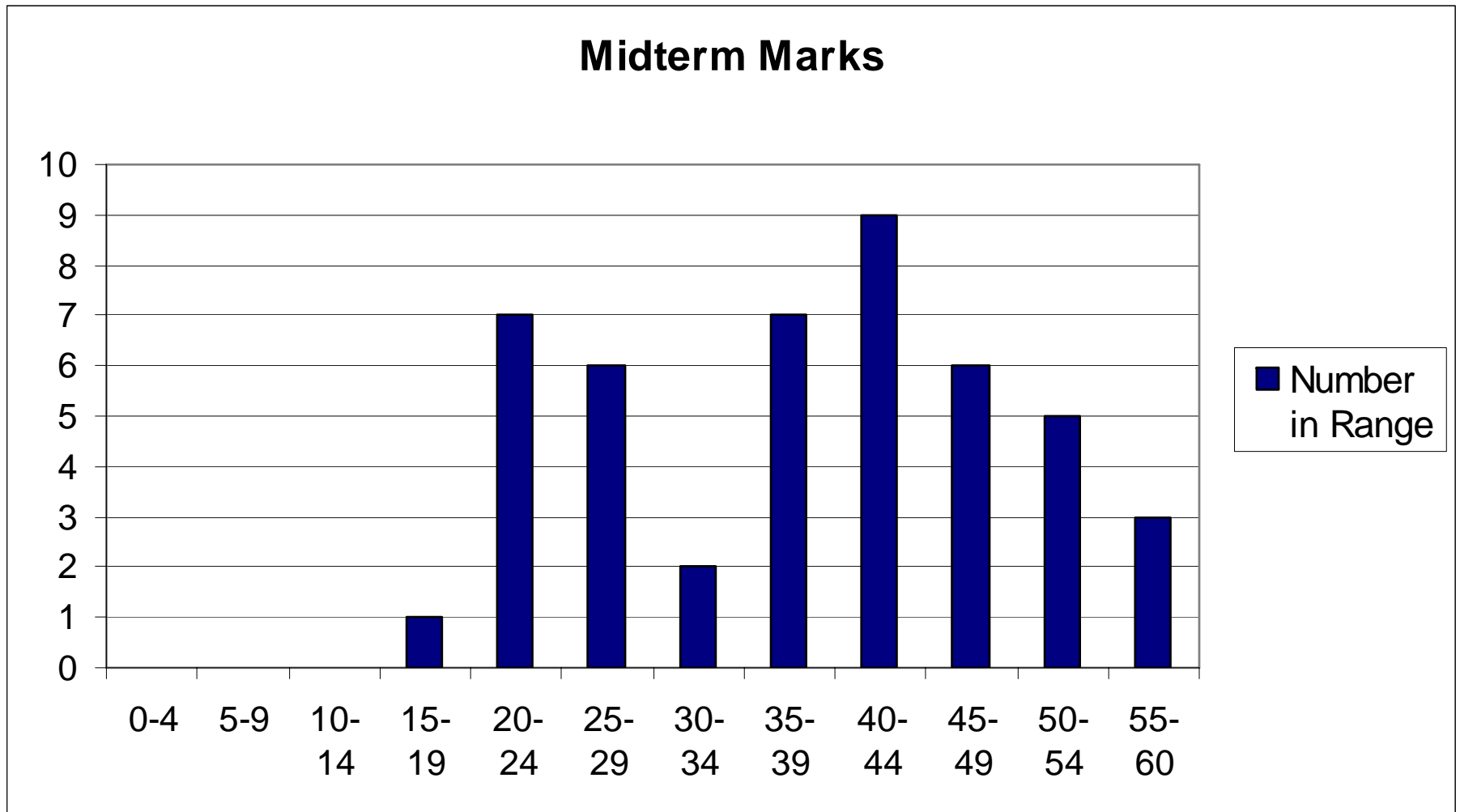


Answers 1.

- Simulated Annealing:
 - A Placement algorithm
 - Minimizes: WIRE LENGTH (accepted cost and area this time only)
 - A Heuristic; Completes in non-polynomial time
- Flowmap:
 - A Technology Mapping algorithm
 - Minimizes: DELAY
 - An Optimal Algorithm; Completes in polynomial time
- Pathfinder:
 - A Routing algorithm

Answers 2.

- A: Routing Channel
- B: Switch Block
 - Enables between vertical and horizontal tracks
- C: CLB/ I/O Pad
 - Implements circuit logic (LUTs and Flipflops)
 - Provides connection with off-chip I/O supporting different transmission standards
- D: Connection Block
 - Enables I/O connections with CLBs to routing tracks

 

Answers 2. (cont'd)

- Other FPGA components
 - Embedded memory, Multipliers/DSP, Dedicated Clock circuitry/DCMs/PLLs, CPUs, High Speed I/Os
- Specific Component consuming the most silicon area
 - Switch Blocks: 31% of Area

Answers 3.

- When do processes execute?
 - Processes don't 'execute' in hardware: they are only a behavioural description of the circuit to be implemented on the chip

OR

- Processes execute in a simulator when an event occurs on one of the signals in the sensitivity list; if there is no sensitivity list, a process executes continuously
- Different statements that specify a rising clock edge
 - (clk = 1) and (clk'event)
 - (clk = 1) and (not (clk'stable))
 - rising_edge(clk) *** This may not be synthesizable depending on the tools***

Answers 3.

- The difference between combinational and sequential logic:
 - Combinational logic: Has no memory; Outputs are only a function of the current inputs
 - Sequential logic: Has memory (aka “state”) such that the outputs are a function of historical information

Answers 4.(i)

entity adder_subtractor is

```
port(in1, in2:      IN      STD_LOGIC_VECTOR (3 DOWNTO 0);
      sub_not_add: IN      STD_LOGIC;
      result:       OUT     STD_LOGIC_VECTOR (4 DOWNTO 0));
```

end unknown;

architecture structural of adder_subtractor is

```
signal cin:      STD_LOGIC_VECTOR (4 DOWNTO 0); -- ripple carry
                                                         -- signal
in2_m:          STD_LOGIC_VECTOR (3 DOWNTO 0); -- "muxed"
                                                         -- in2/in2_bar
```

component full_adder is

```
port(a, b, cin:   IN      STD_LOGIC;
      cout, sum:  OUT     STD_LOGIC);
```

end component;

Answers 4.(i)

begin

```
in2_m(0) <= in2(0) xor sub_not_add; --Use sub_not_add signal to  
in2_m(1) <= in2(1) xor sub_not_add; --decide whether the in2 vector  
in2_m(2) <= in2(2) xor sub_not_add; --should or should not be inverted  
in2_m(3) <= in2(3) xor sub_not_add; --Invert when sub_not_add = 1
```

--Generate the Full Adder chain using your Full Adder component:

```
FA0: full_adder port map (in1(0), in2_m(0), cin(0), cin(1), result(0));
```

```
FA1: full_adder port map (in1(1), in2_m(1), cin(1), cin(2), result(1));
```

```
FA2: full_adder port map (in1(2), in2_m(2), cin(2), cin(3), result(2));
```

```
FA3: full_adder port map (in1(3), in2_m(3), cin(3), cin(4), result(3));
```

-- Initialize the cin to the adder/subtractor; provides the additional “plus one”

-- required for twos complement

```
cin(0) <= sub_not_add;
```

-- The final carry out bit provides the “sign bit” for the 2’s complement

-- number:

```
result <= cin(4);
```

end architecture;

Answers 4.(i)

entity full_adder is

```
port(a, b, cin:    IN    STD_LOGIC;  
      cout, sum:  OUT    STD_LOGIC);
```

end full_adder;

architecture structural of adder_subtractor is

begin

```
sum <= a xor b xor cin; --sum is high for an odd number of '1's  
cout <= (a and b) or (a and cin) or (b and cin); -- carry is high when  
-- more than 1 (>1)  
-- input is high
```

end structural;

Answers 4.(i) Marking Scheme

- 1 adder entity**
- 1 sum**
- 1 carry**
- 1 architecture**
- 1 COMMENTS**

- 1 component**
- 1 cin assignment for bit 0**
- 4 Full Adder instantiations**
- 1 in2 inversion**
- 1 in2 multiplexing**
- 2 comments**

Answers 4.(ii) Marking Scheme

- 1 sum
- 2 carry
- 1 a's connection
- 1 b's connection

- 1 in1
- 1 invert in2
- 2 mux in2/inv_in2
- 1 mux select
- 1 cin(0) = sub_not_add
- 1 result
- 1 cout = cin chain
- 1 replication
- 1 labels

- +1 result(4) = cout(3)

Answers 4.(ii)

SEE BOARD WORK FOR CIRCUIT SOLUTION